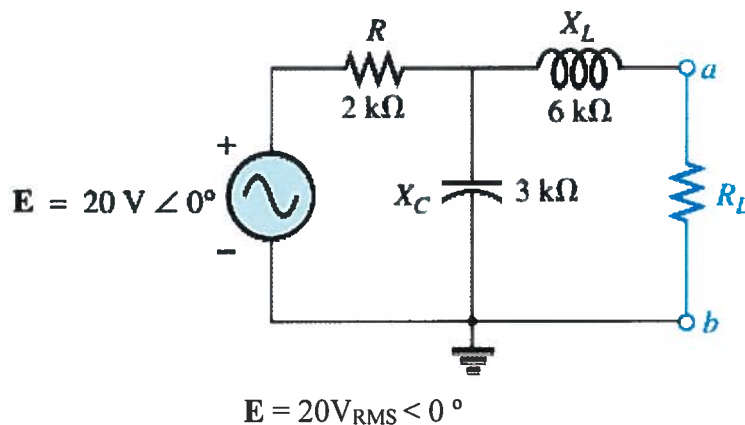


NAME (printed): * SOLUTIONS * Program: _____

You have 50 minutes to complete this examination. You are allowed your calculator, a 3x5" card and the provided formulas/tables from the text.


- M/C Questions
 - Circle the best alternative that answers the question
 - NO partial credit will be awarded
- Work the Problem Questions
 - SHOW ALL your work in the space provided
 - BOX-IN your final answer
 - Partial credit may be awarded



For the circuit shown above, answer the following questions:

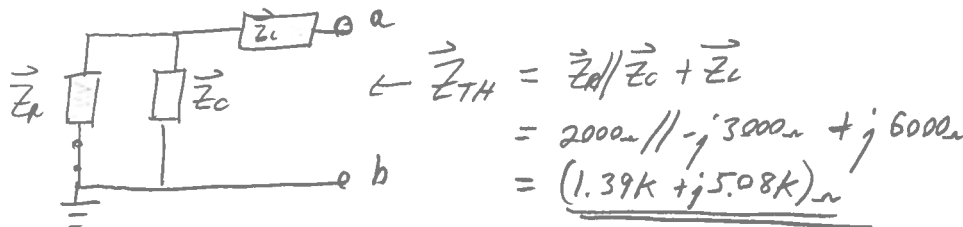
1. Calculate Z_{TH} :


- ☒ A) $(1.39k + j5.08k) \Omega$
☐ B) $5.26 k\Omega \angle -74.7^\circ$
☐ C) $(2k - j3k) \Omega$
☐ D) $(2k + j3k) \Omega$



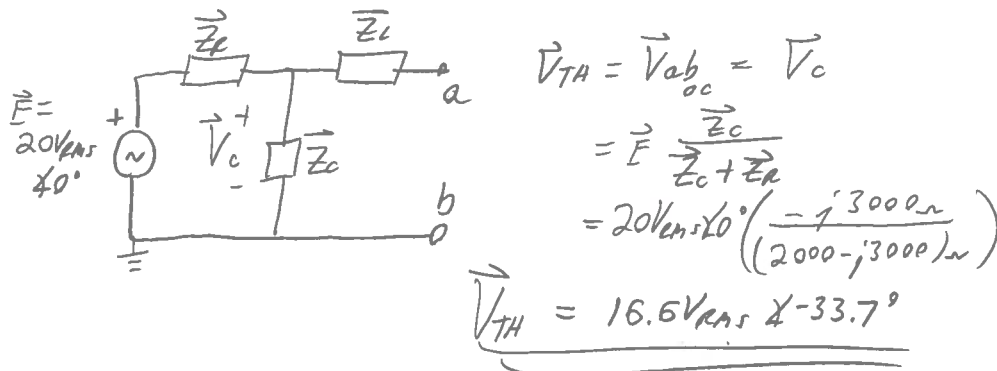2. Determine V_{TH} :

- ☐ A) $16.6 V_{rms} \angle +33.7^\circ$
☐ B) $8.3 V_{rms} \angle +33.7^\circ$
☐ C) $20 V_{rms} \angle 0^\circ$
☒ D) $16.6 V_{rms} \angle -33.7^\circ$



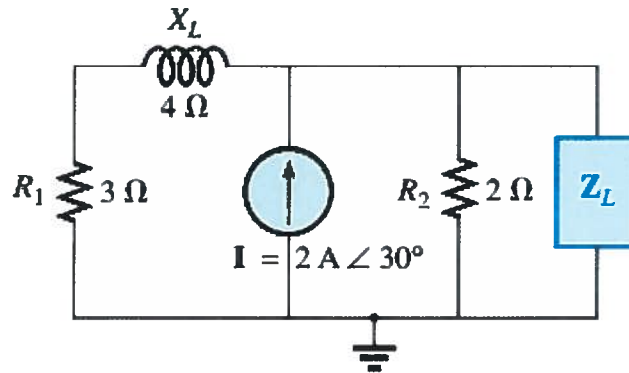


$$I = 2A_{RMS} \angle 30^\circ$$

For the circuit shown above, answer the following questions:

3. Find Z_L for maximum power transfer to the load:

- A) $(1.51 + j0.39) \Omega$
- B) $5\Omega \angle 53.1^\circ$
- C) $(1.51 - j0.39) \Omega$
- D) $(3 - j4) \Omega$


\hat{Z}_{TH}^*

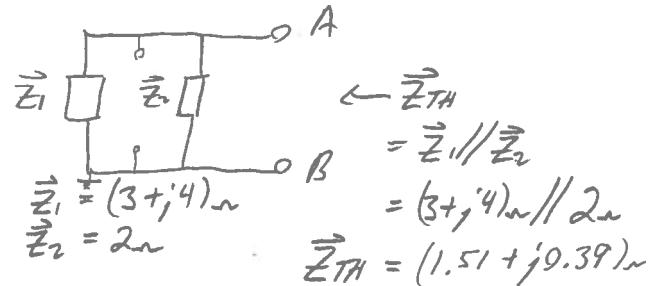


4. Find the power transferred to the load assuming $Z_L = Z_{TH}^*$:

- A) 1.93 W
- B) 1.61 W
- C) 3.12 W
- D) 1.31 W


\vec{V}_{TH} :

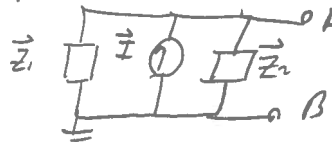
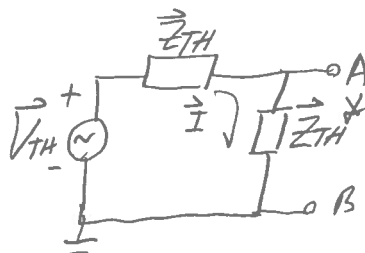
$$\begin{aligned}
 \vec{V}_{TH} &= \vec{V}_{AB\text{oc}} \\
 &= \vec{I} (\vec{Z}_1 \parallel \vec{Z}_2) \\
 &= (2A_{RMS} \angle 30^\circ) (1.51 + j0.39)\Omega \\
 &= 3.13V_{RMS} \angle 44.5^\circ
 \end{aligned}$$


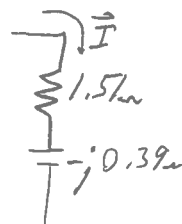
$$\begin{aligned}
 \vec{I} &= \frac{\vec{V}_{TH}}{\vec{Z}_{TH} + \vec{Z}_{TH}^*} \\
 &= 1.03A_{RMS} \angle 44.5^\circ
 \end{aligned}$$



$$\begin{aligned}
 P_{LOAD} &= |\vec{I}|^2 (1.5\Omega) \\
 &= 1.61W
 \end{aligned}$$

5. A power level of 50 W is 6 dB above what power level?

- A) 3.98 W
- B) 25.1 W
- C) 35.4 W
- ☒ D) 12.6 W

$$6 \text{ dB} = 10 \log_{10} \left(\frac{50 \text{ W}}{P_i} \right)$$

$$P_i = \underline{\underline{12.56 \text{ W}}}$$

6. Determine the power level in dBm corresponding to a power of 20 mW:

- A) 7.07 dBm
- ☒ B) 13.0 dBm
- C) 20.0 dBm
- D) 26.0 dBm

$$P_{\text{dBm}} = 10 \log_{10} \left(\frac{20 \text{ mW}}{1 \text{ mW}} \right)$$


$$= \underline{\underline{13.01 \text{ dBm}}}$$

7. Find the output voltage for an amplifier with an input voltage of 10 mV and voltage gain of 22 dB:

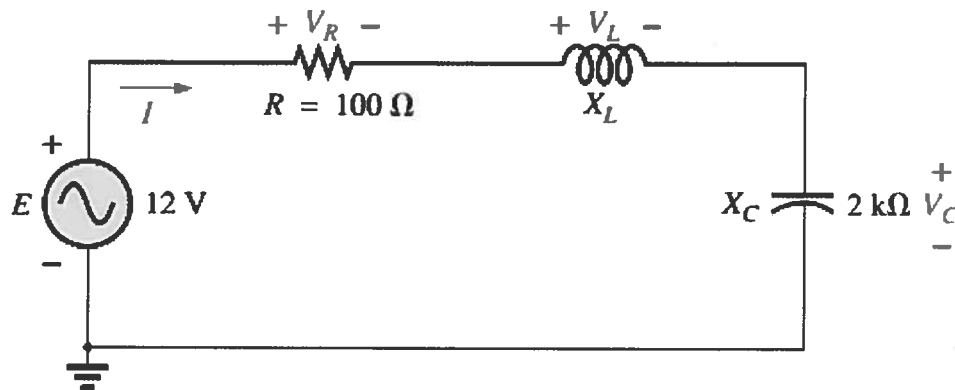- A) 252 mV
- B) 330 mV
- C) 12.6 mV
- ☒ D) 126 mV

$$22 \text{ dB} = 20 \log_{10} \left(\frac{P_o}{P_i} \right)$$

$$P_o = \underline{\underline{126 \text{ mV}}}$$



$$E = 12V_{RMS} \angle 0^\circ$$

For the circuit shown above, answer the following questions:

8. Determine the quality factor of the circuit:

A) 8.3

☒ B) 20

C) $Q_s = \infty$, as there is no R_L

D) 0.05

(at f_s)

$$Q_s = \frac{X_L}{R_L} = \frac{X_C}{R} = \frac{2000\Omega}{100\Omega} = \underline{\underline{20}}$$

$X_L = X_C$ at RESONANCE

9. If the resonant frequency is 5 kHz, find the value of L:

A) 31.9 mH

B) 200 μ H

C) 628 μ H

☒ D) 63.7 mH

$$\begin{aligned} X_L &= 2\pi fL \\ 2000 &= 2\pi (5\text{kHz})L \\ L &= \underline{\underline{63.66\text{ mH}}} \end{aligned}$$

10. Find the bandwidth of the circuit if the resonant frequency is 5 kHz:

A) 1204 Hz

B) 602 Hz

☒ C) 250 Hz

D) 302 Hz

$$\begin{aligned} BW &= \frac{f_s}{Q_s} = \frac{5\text{kHz}}{20} \\ &= \underline{\underline{250\text{ Hz}}} \end{aligned}$$

The load on a 240 VRMS, 60 Hz supply is 5kW (resistive), 8 kVAR (inductive) and 2kVAR (capacitive). Determine the following:

11. The total apparent power


$$\begin{aligned}
 P &= 5 \text{ kW} \\
 Q &= +j8000 - j2000 = +j6000 \text{ VAR} \\
 \therefore \vec{S} &= 5000 \text{ W} + j6000 \text{ VAR} \\
 &\text{OR} \\
 &\boxed{7,810 \text{ VA} \angle 50.19^\circ}
 \end{aligned}$$

12. The power factor of the system

$$\begin{aligned}
 \text{PF} &= \cos(\theta) = \cos(50.19^\circ) = \boxed{0.64} \\
 &\quad \text{LAGGING} \\
 &\quad \text{INDUCTIVE} \therefore I \text{ lags } V
 \end{aligned}$$

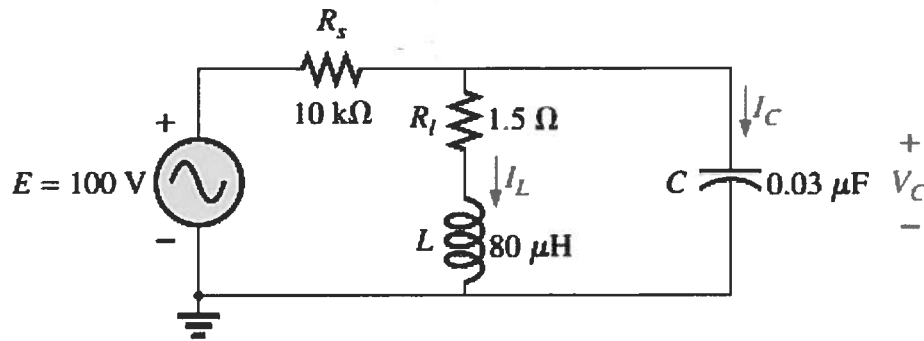13. Find the amount of current drawn from the supply

$$\begin{aligned}
 \vec{S} &= \vec{V} \vec{I}^* \\
 \vec{I}^* &= \frac{\vec{S}}{\vec{V}} = \frac{7810 \text{ VA} \angle 50.19^\circ}{240 \text{ V}_{\text{RMS}} \angle 0^\circ} \\
 &= 32.54 \text{ A}_{\text{RMS}} \angle 50.19^\circ \\
 \text{HENCE } \boxed{\vec{I} &= 32.54 \text{ A}_{\text{RMS}} \angle -50.19^\circ}
 \end{aligned}$$



$$E = 100V_{pk} < 0^\circ$$

For the circuit shown above, answer the following questions:


14. Find the resonant frequency (in Hz):

$$f_p \sim f_s = \frac{1}{2\pi\sqrt{LC}} = \boxed{102.73 \text{ kHz}}$$

$$Q_L \geq 10? \quad Q_L = \frac{X_L}{R_L} = \frac{2\pi fL}{R_L} = \boxed{34.4} \quad \checkmark Q_L \geq 10$$

15. Find the quality factor of the inductor, Q_L :

16. Find the peak voltage across the capacitor at resonance, $|V_C|$:

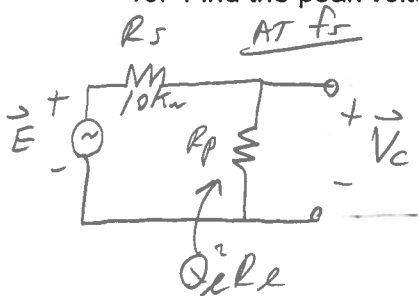

$$\begin{aligned} \vec{V}_C &= \vec{E} \frac{R_p}{R_p + R_s} \\ &= 100V_{pk} \angle 0^\circ \frac{(34.4)^2 (1.5\Omega)}{(34.4)^2 (1.5\Omega) + 10k\Omega} \\ &= 15.1V_{pk} \angle 0^\circ \end{aligned}$$

$$\boxed{|\vec{V}_C| = 15.1V_{pk}}$$