

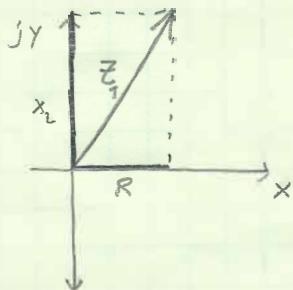
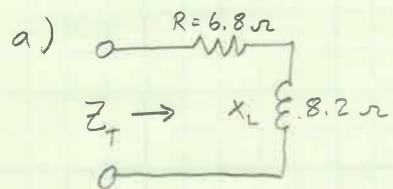


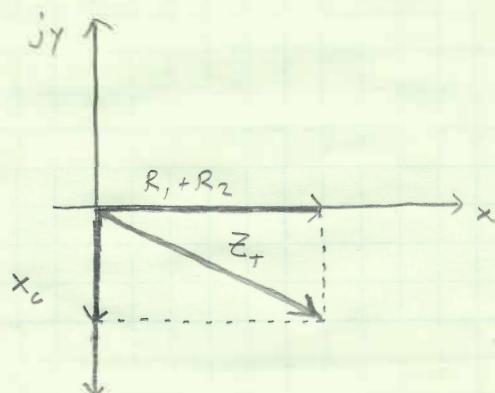(12) Calculate the total impedance of the circuit shown. Express your answer in both polar and rectangular form, and draw the impedance diagram.



$$Z_T = \boxed{(6.8 + j 8.2) \Omega}$$



$$= \boxed{10.65 \angle 50.3^\circ}$$

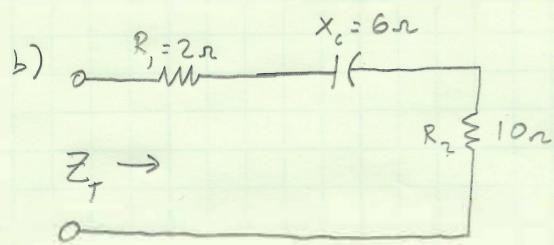



$$Z_T = \boxed{(12 - j 6) \Omega} = \boxed{13.42 \angle -26.6^\circ}$$

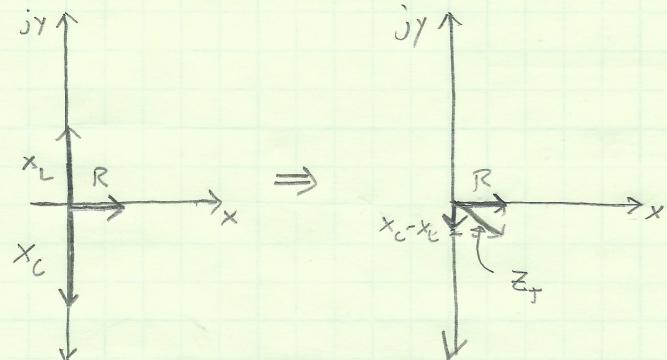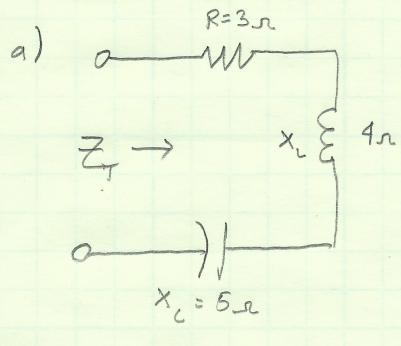(13) Calculate the total impedance of the circuit shown.

Express your answer in both rectangular and polar form, and draw the impedance diagram.


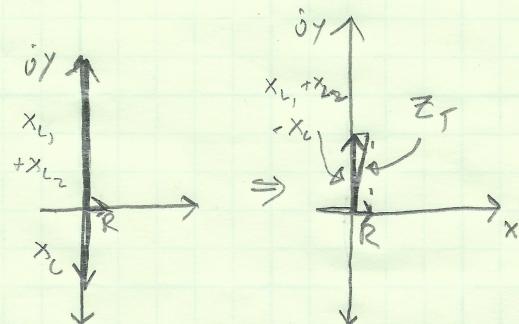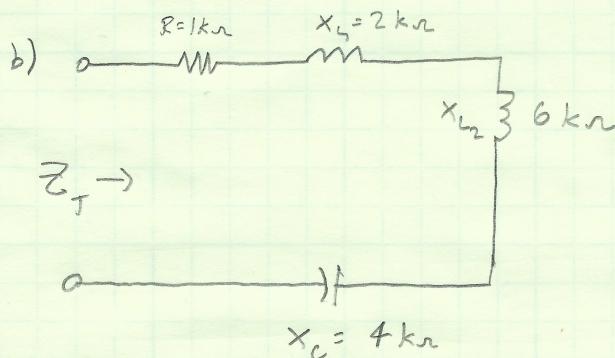
$$Z_T = 3 \Omega + (j4 \Omega) + (-j5 \Omega) = \boxed{(3-j1) \Omega = 3.162 \Omega \angle -18.4^\circ}$$



$$Z_T = 1 k\Omega + (j2 k\Omega) + (j6 k\Omega) + (-j4 k\Omega) = \boxed{(1k+j4k) \Omega = 4123 \Omega \angle 76.0^\circ}$$

(14) Find the type and impedance in ohms of the circuit in the closed container (Voltage and current phasors are in RMS)

$$a) E = 120V \angle 0^\circ$$

$$I = 6A \angle 45^\circ$$

$$Z = \frac{E}{I} = \frac{120V \angle 0^\circ}{6A \angle 45^\circ} = 20\Omega \angle -45^\circ$$

$$= (14.14 - j14.14)\Omega$$

$$R = 14.14\Omega$$

$$X_c = j14.14\Omega$$

Capacitive Load

* Check: We calculated that the load is capacitive. If this is correct, input current must lead input voltage, which it does.

$$b) E = 80V \angle 130^\circ$$


$$I = 20mA \angle 40^\circ$$

$$Z = \frac{E}{I} = \frac{80V \angle 130^\circ}{20mA \angle 40^\circ} = 4000\Omega \angle 90^\circ$$

$$= (0 + j4000)\Omega$$

Purely inductive load

(15) For the circuit:

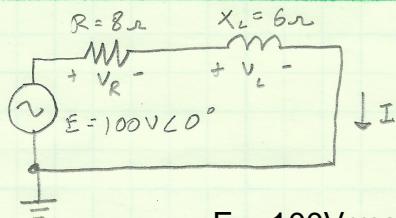


$$E = 100\text{Vrms} < 0 \text{ Deg}$$

a) Find Z_T in polar form

$$Z_T = (8 + j6)\Omega = \boxed{10\Omega \angle 36.9^\circ}$$

b) Draw the impedance diagram

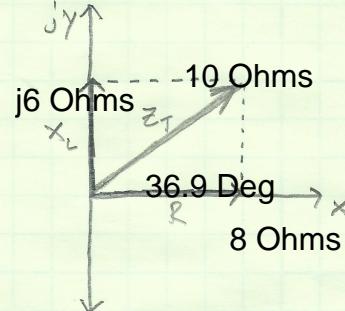


c) Find the current I and voltages V_R and V_L in phasor form

$$I = \frac{E}{Z_T} = \frac{100\text{V} \angle 0^\circ}{10\Omega \angle 36.9^\circ} = \boxed{10\text{A} \angle -36.9^\circ}$$

$$V_R = I \cdot R = (10\text{A} \angle -36.9^\circ)(8 + j0)\Omega = \boxed{80\text{V} \angle -36.9^\circ}$$

$$V_L = I \cdot X_L = (10\text{A} \angle -36.9^\circ)(0 + j6)\Omega = \boxed{60\text{V} \angle 53.1^\circ}$$

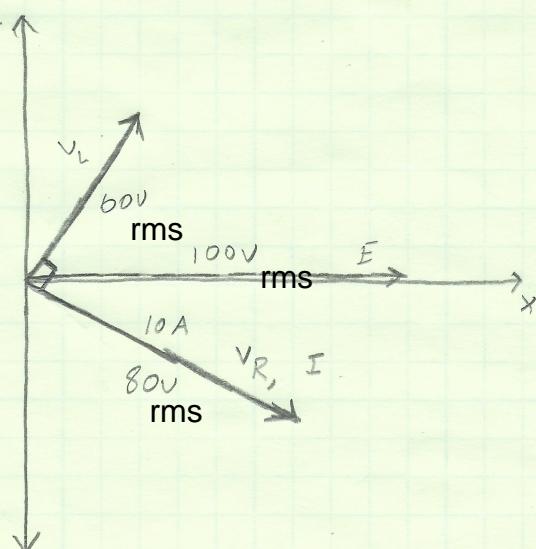d) Draw the phasor diagram of the voltages E , V_R , V_L , and the current I .



e) Verify KVL around the closed loop

$$E = V_R + V_L = \frac{100V}{\text{rms}} \angle 0^\circ = \frac{80V}{\text{rms}} \angle -36.9^\circ + \frac{60V}{\text{rms}} \angle 53.1^\circ$$
$$= (63.97 - j48.03)V + (36.03 + j47.98)V \approx \frac{100V}{\text{rms}} \angle 20^\circ$$

f) Find the average power delivered to the circuit

* Remember that reactive components do not dissipate power

$$P = I^2 R = \left(\frac{10A}{\text{rms}}\right)^2 (8\Omega) = \boxed{800W}$$

g) Find the power factor of the circuit

$$F_p = \cos(\theta_T) = \frac{R}{Z_T} = \frac{8\Omega}{10\Omega} = \boxed{0.8}$$

* I_T has a negative angle, which by definition means F_p is lagging


h) Find sinusoidal expressions for voltage and current if $f = 60\text{Hz}$

$$E = 141.4V_p \sin(60t) \quad I = 14.14A_p \sin(60t - 36.9^\circ)$$


$$V_R = 113.1V_p \sin(60t - 36.9^\circ) \quad V_L = 84.85V_p \sin(60t + 53.1^\circ)$$

* No need for the "p" designation here, by definition the number in front of a sinusoid is the peak value *

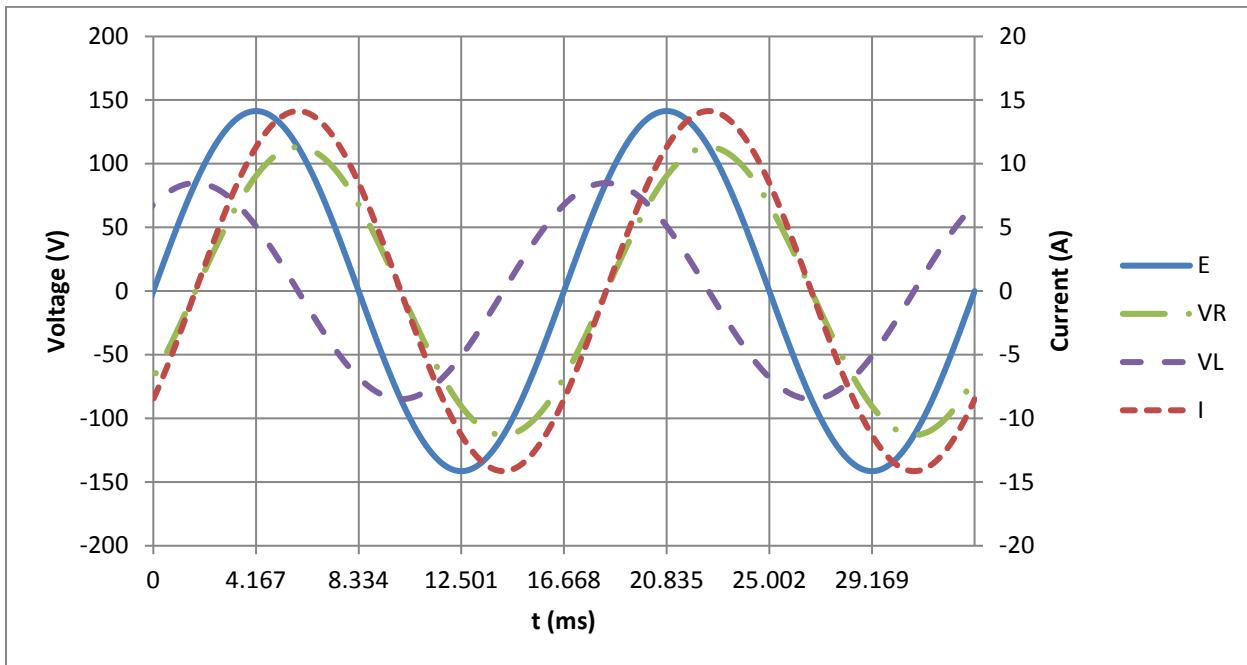i) Plot the waveforms for the voltage and current on the same set of axes.



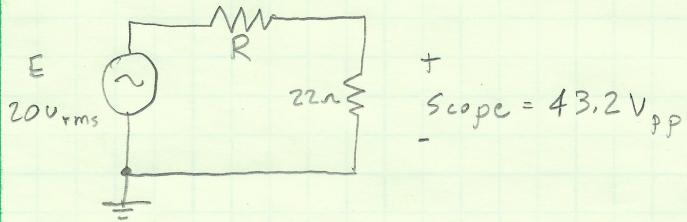(22) Using the oscilloscope reading in Fig. 15.99, determine the resistance R (closest standard value).




$$\text{Scope} = 43.2 \text{ V}_{\text{pp}}$$

$$20 \text{ V}_{\text{rms}} = 28.28 \text{ V}_p \quad 43.2 \text{ V}_{\text{pp}} = 21.6 \text{ V}_p$$

$$V_R = E - \text{Scope} = 28.28 \text{ V}_p - 21.6 \text{ V}_p = 6.684 \text{ V}_p$$

$$\frac{R}{22 \text{ n}} = \frac{6.684 \text{ V}_p}{21.6 \text{ V}_p} \quad R = 6.808 \text{ n} \approx \boxed{6.8 \text{ n}}$$

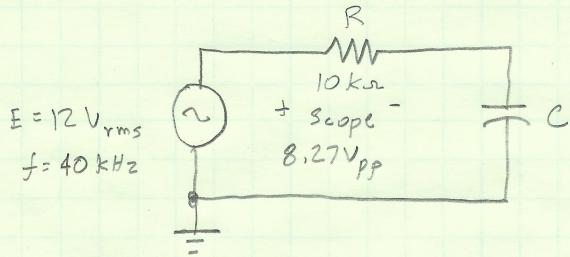(24) Using the oscilloscope reading in Fig. 15.101



a) Find the rms value of the current

$$I = \frac{\text{Scope}}{R} = \frac{8.27 \text{ V}_{\text{pp}}}{10 \text{ k}\Omega} = 827 \mu\text{A}_{\text{pp}} = \boxed{292.4 \mu\text{A}_{\text{rms}}}$$

b) Determine the capacitance C


$$\begin{aligned} E^2 &= V_R^2 + V_C^2 \rightarrow V_C = \sqrt{E^2 - V_R^2} \\ &= \sqrt{(12 \text{ V}_{\text{rms}})^2 + (292.4 \mu\text{A}_{\text{rms}})^2} \\ &= 11.64 \text{ V}_{\text{rms}} \end{aligned}$$

$$X_C = \frac{V_C(\text{rms})}{I_{\text{rms}}} = \frac{11.64 \text{ V}_{\text{rms}}}{292.4 \mu\text{A}_{\text{rms}}} = 39.81 \text{ k}\Omega = \frac{1}{2\pi f C}$$


$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi(40 \text{ k})(39.81 \text{ k})} = \boxed{100 \text{ pF}}$$

P15.24

GIVEN :

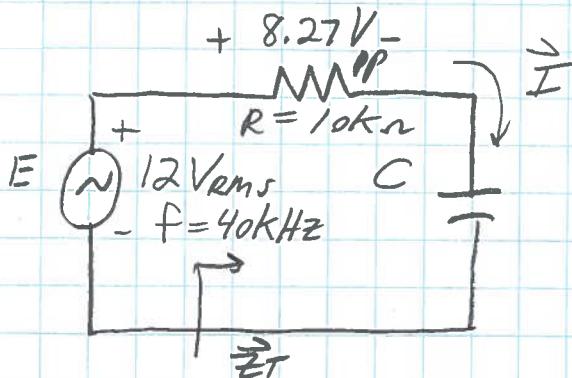

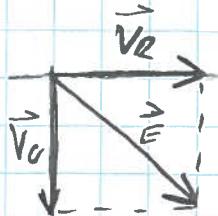ALTERNATE TO VOLTAGE PHASOR SOCN THAT STARTS:



$$|E| = \sqrt{|V_R|^2 + |V_C|^2}$$

$$E^2 = V_R^2 + V_C^2 \dots$$

FIND : (a) I_{RMS}

(b) C

$$(a) |\vec{I}| = \frac{|\vec{V}_R|}{R} = \frac{8.27 V_{pp}}{10 \text{ k}\Omega} = 827 \mu\text{A}_{pp}$$

$$= 413.5 \mu\text{A}_{pk} = \boxed{292.4 \mu\text{A}_{\text{RMS}}}$$

$$\frac{I_{pk}}{pk}/2 \quad \frac{I_{pk}}{\sqrt{2}}$$

$$(b) \vec{Z}_T = R - jX_C$$

$$= (10,000 - jX_C) \text{ } \Omega, \text{ NEED } X_C \text{ TO FIND } C$$

$$|\vec{Z}_T| = \sqrt{(10,000 \Omega)^2 + (X_C \Omega)^2} \quad (1)$$

$$\text{BUT } \vec{Z}_T = \frac{\vec{E}}{\vec{I}} = \frac{16.97 V_{pk} \angle 0^\circ}{413.5 \mu\text{A}_{pk} \angle X^\circ} \leftarrow \text{UNKNOWN PHASE}$$

$$\therefore \vec{Z}_T = 41,041 \Omega \angle (0^\circ - X^\circ)$$

$$\text{OR } |\vec{Z}_T| = 41,041$$

$$\text{INTO (1)}: 41,041 \Omega = \sqrt{(10,000 \Omega)^2 + (X_C \Omega)^2} \quad (2)$$

$$\text{SOLVING YIELDS } X_C = 39,804 \Omega = \frac{1}{2\pi f C} \approx 40 \text{ kHz}$$

$$\text{HENCE } \boxed{C = 99.96 \mu\text{F}}$$

28. Calculate the voltages V_1 and V_2 for the circuits in Fig. 15.104 in phasor form using the voltage divider rule.

a.)

The voltage divider rule is given by:

$$E = 20V_{\text{rms}} < 70 \text{ Deg}$$

$$V_x = \frac{Z_x E}{Z_T}$$

The total impedance of the circuit Z_T is:

$$Z_T = Z_R + Z_L + Z_C = (20 + j0) + (0 + j20) + (0 - j40) = (20 - j20)\Omega$$

Therefore, the voltage drop over the inductor is given by:

$$\begin{aligned} V_1 &= \frac{Z_L E}{Z_T} = \frac{(20\angle 90^\circ) \cdot (20\angle 70^\circ)}{(20 - j20)} \\ V_1 &= \frac{(400\angle 160^\circ)}{(20 - j20)} = \frac{(400\angle 160^\circ)}{28.28\angle \tan^{-1}(\frac{-20}{20})} \\ V_1 &= \frac{(400\angle 160^\circ)}{28.28\angle -45^\circ} = \boxed{(14.14\angle 205^\circ)V_{\text{rms}}} \\ V_1 &= \boxed{(14.14\angle -155^\circ)V_{\text{rms}}} \end{aligned}$$

$$\begin{aligned} V_2 &= \frac{Z_C E}{Z_T} = \frac{(40\angle -90^\circ) \cdot (20\angle 70^\circ)}{(20 - j20)} \\ V_2 &= \frac{(800\angle -20^\circ)}{(20 - j20)} = \frac{(800\angle -20^\circ)}{28.28\angle \tan^{-1}(\frac{-20}{20})} \\ V_2 &= \frac{(800\angle -20^\circ)}{28.28\angle -45^\circ} = \boxed{(28.28\angle 25^\circ)V_{\text{rms}}} \end{aligned}$$

b.)

$$E = 120V_{\text{rms}} < 0 \text{ Deg}$$

$$\begin{aligned} V_1 &= \frac{(Z_L + Z_R + Z_C) \cdot E}{Z_T} = \frac{[(0 + j30 \cdot 10^3)\Omega + (3.3 \cdot 10^3 + j0)\Omega + (0 - j10 \cdot 10^3)\Omega] \cdot (120\angle 0^\circ)}{(Z_R + Z_L + Z_R + Z_C)} \\ V_1 &= \frac{(3.3 \cdot 10^3 + j20 \cdot 10^3)\Omega \cdot (120\angle 0^\circ)}{(4.7 \cdot 10^3 + j0)\Omega + (0 + j30 \cdot 10^3)\Omega + (3.3 \cdot 10^3 + j0)\Omega + (0 - j10 \cdot 10^3)\Omega} \\ V_1 &= \frac{(2.43 \cdot 10^6 \angle 80.63)}{(8 \cdot 10^3 + j20 \cdot 10^3)\Omega} = \boxed{(112.92\angle 12.43^\circ)V_{\text{rms}}} \end{aligned}$$

$$V_2 = \frac{(Z_R + Z_C) \cdot E}{Z_T} = \frac{[(3.3 \cdot 10^3 + j0)\Omega + (0 - j10 \cdot 10^3)\Omega] \cdot (120\angle 0^\circ)}{(Z_R + Z_L + Z_R + Z_C)}$$

$$V_2 = \frac{(3.3 \cdot 10^3 - j10 \cdot 10^3)\Omega \cdot (120\angle 0^\circ)}{(4.7 \cdot 10^3 + j0)\Omega + (0 + j30 \cdot 10^3)\Omega + (3.3 \cdot 10^3 + j0)\Omega + (0 - j10 \cdot 10^3)\Omega}$$

$$V_2 = \frac{(1.26 \cdot 10^6 \angle -71^\circ)}{(8 \cdot 10^3 + j20 \cdot 10^3)\Omega} = \boxed{(58.66\angle -139.94^\circ)V_{\text{rms}}}$$

29. For the circuit in Fig.105:

a. Determine I , V_R and V_C in phasor form.

The source frequency is:

$$w = 2\pi \cdot f = 1000$$

$$Z_L = jwL = j \cdot 1000 \cdot 20 \cdot 10^{-3} = 20\Omega$$

$$Z_C = \frac{1}{jwC} = \frac{1}{j1000 \cdot 39 \cdot 10^{-6}} = 25.64\Omega \angle -90^\circ$$

$$Z_T = Z_R + Z_L + Z_C = (30 + j0) + (0 + j20) + (0 - j25.64) = (30 - j5.64)\Omega$$

$$I = \frac{E}{Z_T} = \frac{20\angle 40^\circ V_{\text{rms}}}{(30 - j5.64)\Omega} = \boxed{655\text{mA}\angle 50.65^\circ} \text{ rms}$$

$$V_R = IZ_R = (655\text{mA}\angle 50.65^\circ) \cdot (30\Omega) = \boxed{19.66V_{\text{rms}}\angle 50.65^\circ}$$

$$V_C = IZ_C = (655\text{mA}\angle 50.65^\circ) \cdot (25.64\Omega \angle -90^\circ) = \boxed{16.80V_{\text{rms}}\angle -39.35^\circ}$$


b. Calculate the total power factor, and indicate whether it is leading or lagging.

$$F_P = \cos(\phi_I - \phi_E) = \cos(50.65 - 40) = 0.983 \text{ leading}$$


c. Calculate the average power delivered to the circuit.

$$P_{ave} = V_{\text{rms}} \cdot I_{\text{rms}} \cos(\phi_I - \phi_E) = 20 \cdot 655 \cdot 10^{-3} \cdot \cos(50.65 - 40) = \boxed{12.87\text{W}}$$

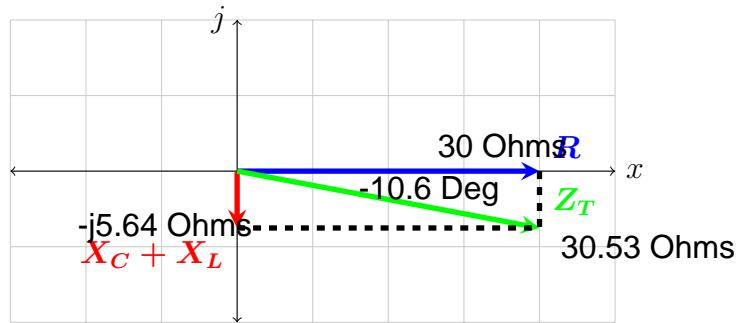d. Draw the impedance diagram. **Note:** Not drawn to scale.



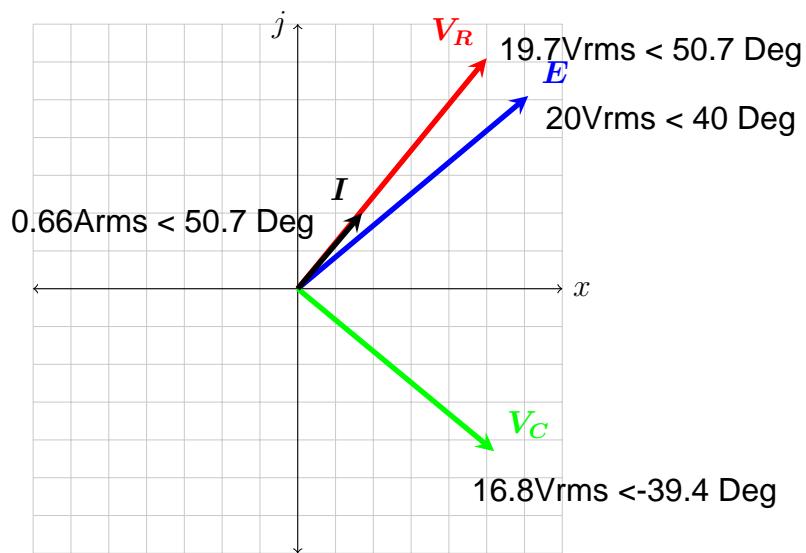- e. Draw the phasor diagram of the voltages E , V_R and V_C and the current I . **Note:** The phasors are not drawn to scale (especially current)



- f. Find the voltages V_R and V_C using the voltage divider rule, and compare them with the results of part (a).

$$V_R = \frac{R \cdot E}{Z_T} = \frac{30 \cdot 20 \angle 40^\circ \text{V}_{\text{rms}}}{(30 - j5.64)} = \boxed{19.66 \text{V}_{\text{rms}} \angle 50.65^\circ}$$

$$V_C = \frac{Z_C \cdot E}{Z_T} = \frac{(25.64 \text{V}_{\text{rms}} \angle -90^\circ) \cdot (20 \angle 40^\circ \text{V}_{\text{rms}})}{(30 - j5.64)} = \boxed{16.80 \text{V}_{\text{rms}} \angle -39.35^\circ}$$

- g. Draw the equivalent series circuit of the above as far as the total impedance and the current i are concerned.

The series circuit will contain the following parameters:

Source voltage, E : $20 \angle 40^\circ \text{V}_{\text{rms}}$

Impedance, Z_T : $(30 - j5.64)\Omega$

Current, I : $655 \text{mA} \angle 50.65^\circ$


rms

30. For the circuit in Fig.106:

- a. Plot Z_T and ϕ_T versus frequency for a frequency range of zero to 20kHz

$$Z_T = \sqrt{R^2 + X_L^2} \angle \tan^{-1} X_L/R$$

f	Z_T	θ_T
0 Hz	1.0 kΩ	0.0°
1 kHz	1.008 kΩ	7.16°
5 kHz	1.181 kΩ	32.14°
10 kHz	1.606 kΩ	51.49°
15 kHz	2.134 kΩ	62.05°
20 kHz	2.705 kΩ	68.3°

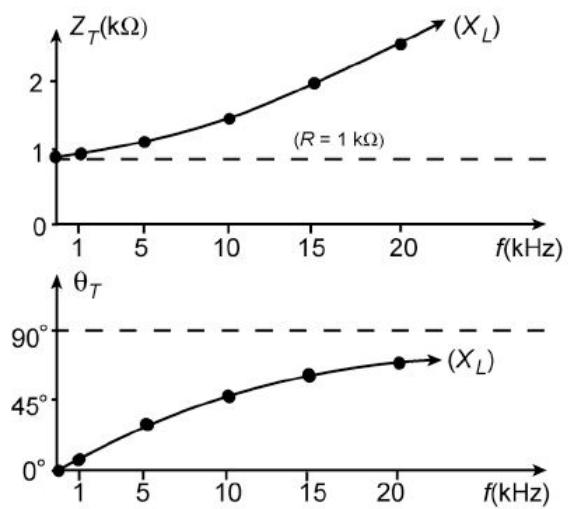


- b. Plot V_L versus frequency for the frequency range of part (a)

$$b. V_L = \frac{X_L E}{Z_T}$$

f	V_L
0 Hz	0.0 V
1 kHz	0.623 V
5 kHz	2.66 V
10 kHz	3.888 V
15 kHz	4.416 V
20 kHz	4.646 V


(Vrms)

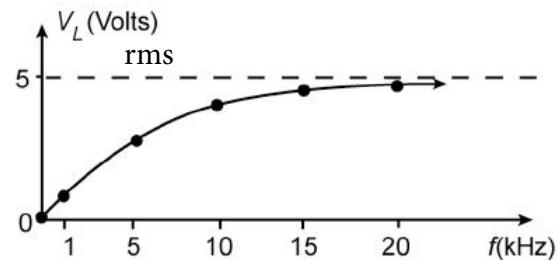

- c. Plot ϕ_L versus frequency for the frequency range of part (a)

$$c. \theta_L = 90^\circ - \tan^{-1} X_L/R$$

f	$\theta_L = 90^\circ - \tan^{-1} X_L/R$
0 Hz	90.0°
1 kHz	82.84°
5 kHz	57.85°
10 kHz	38.5°
15 kHz	27.96°
20 kHz	21.7°

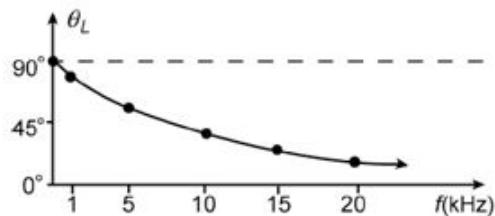

d. Plot V_R versus frequency for the frequency range of part (a)

d.

f	$V_R = RE/Z_T$	(Vrms)
0 Hz	5.0 V	
1 kHz	4.96 V	
5 kHz	4.23 V	
10 kHz	3.11 V	
15 kHz	2.34 V	
20 kHz	1.848 V	

