

Name (printed): * SOLUTIONS * Program: _____

All 5 questions are equally weighted, no partial credit. Circle the correct answer for each question.

- An ideal transformer has 200 primary turns and 20 secondary turns. What is the secondary voltage if the primary voltage is 120 V?
 a. 1.2 V
 b. 12 V
 c. 120 V
 d. 1200 V
 e. 12,000 V

$$120V \frac{20}{200} = 12V$$

$$200:20$$

$$10:1$$

$$N_p:N_s$$
- Which of the following terms describes the impedance appearing at the primary of a transformer due to a load connected to the secondary?
 a. Load impedance
 b. Mutual impedance
 c. Reflected impedance
 d. Resonant impedance

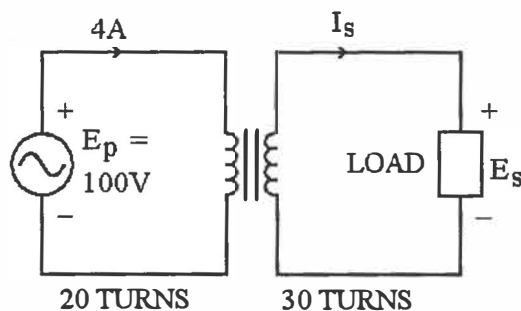


Figure 21.3

Note: Voltages and Currents shown are in RMS

- See Figure 21.3. What is the transformation ratio "a" for this transformer?

a. 0.667
 b. 1.5
 c. 20
 d. 30

- See Figure 21.3. What is the voltage magnitude, E_s across the load?

a. 66.7 V
 b. 100 V
 c. 120 V
 d. 150 V

$$E_s = \frac{E_p}{a} = \underline{150V}$$

- See Figure 21.3. If this transformer is ideal, how much power is transferred to the load?

a. 0 W
 b. 266.7 W
 c. 400 W
 d. 600 W

$$P_{\text{primary}} = (100V_{\text{RMS}})(4A_{\text{RMS}}) = \underline{400W}$$

$$P_{\text{load}} = P_p = \underline{400W}$$