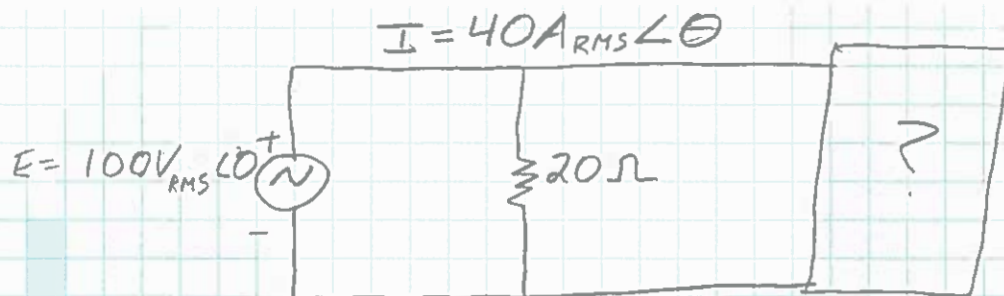


16-23



Find the element or elements that must be in the closed container to satisfy the following conditions (Find the simplest parallel circuit)

- Average Power to the circuit =  $3000W$
- Circuit has a lagging power factor

$$P = V_{RMS} I_{RMS} \cos \theta = (100V)(40A) \cos \theta = 3000W$$

$$\theta = \cos^{-1} \left( \frac{3000W}{100V \cdot 40A} \right)$$

$$= 41.41^\circ$$


Since parallel, use admittance:

$$Y = \frac{1}{Z_T} = \frac{I}{E} = \frac{40A_{RMS} \angle -41.41^\circ}{100V_{RMS} \angle 0^\circ} = .4S \angle -41.41^\circ = .3S - j.265S$$


Resistive
Inductive

Resistive:  $.3S = \frac{1}{R_T} = \frac{1}{20\Omega} + \frac{1}{R_2}$        $R_2 = 4\Omega$

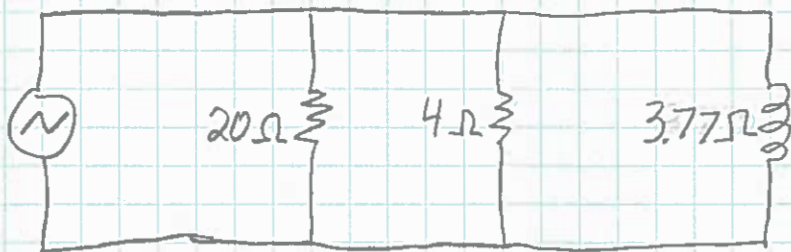
Inductive:  $.265S = \frac{1}{X_L}$        $X_L = 3.774\Omega$




## Question 16-26

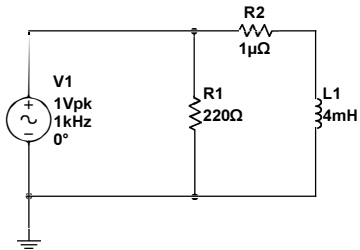


## 16.26 a - ZT vs Freq.

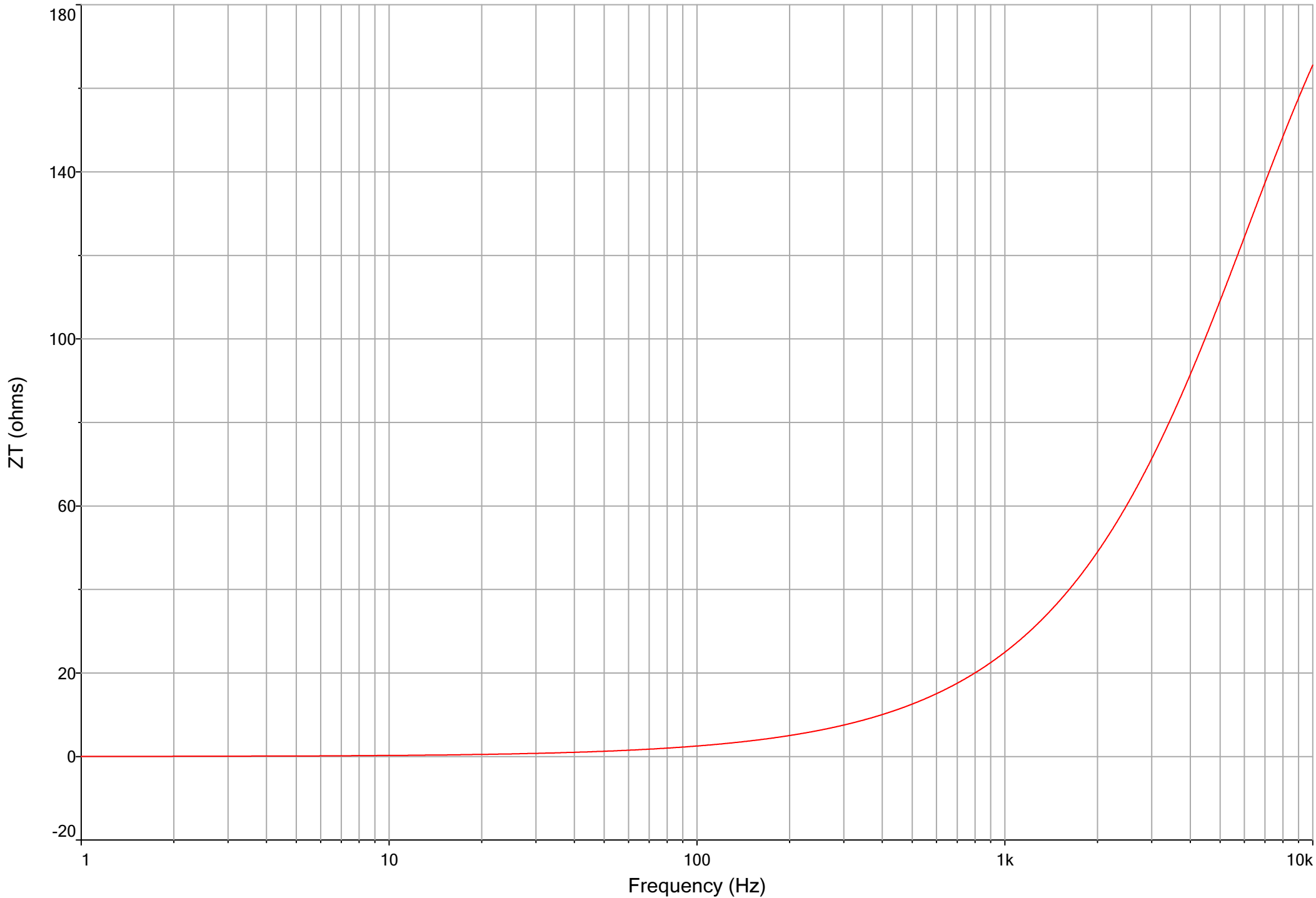

16.26 b -  $i_T$  vs Freq.

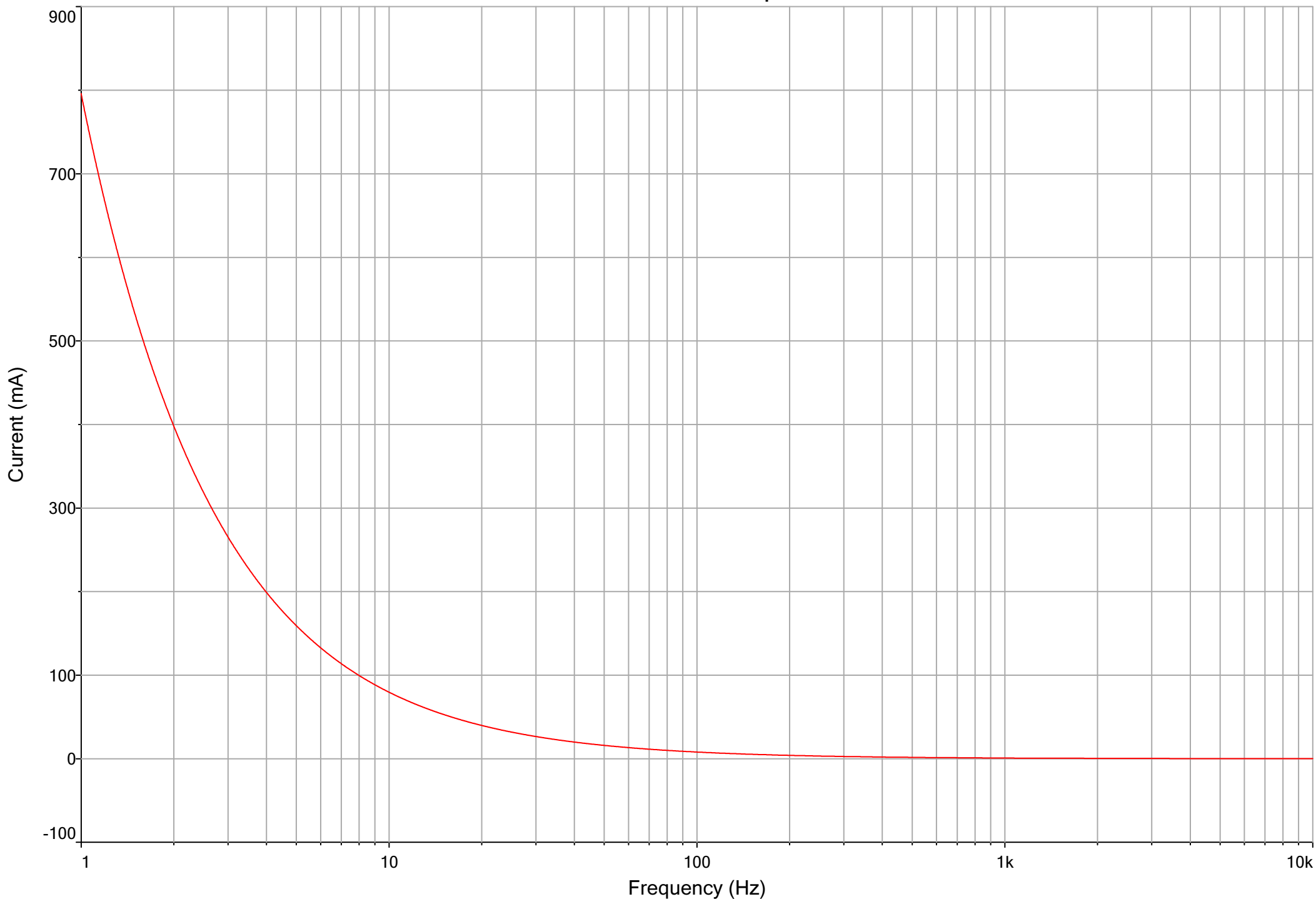

17-1) For the series-parallel network:

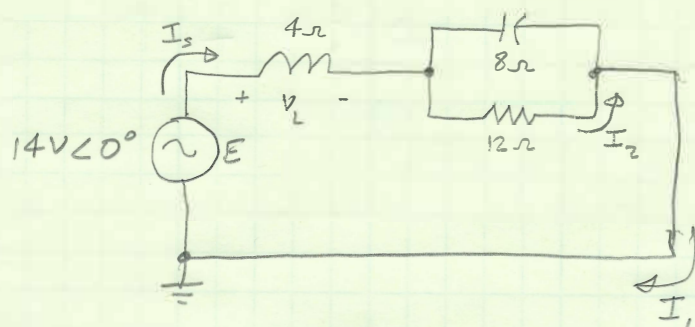

a) Calculate  $Z_T$

$$Z_T = (4\Omega \angle 90^\circ) + [(8\Omega \angle -90^\circ) \parallel (12\Omega \angle 0^\circ)] = \boxed{(4\Omega \angle -22.6^\circ)}$$

b) Determine  $I_s$

$$I_s = \frac{E}{Z_T} = \frac{14V \angle 0^\circ}{4\Omega \angle -22.6^\circ} = \boxed{(3.5A \angle 22.6^\circ)}$$

c) Determine  $I_1$

$$I_1 = I_s = \boxed{(3.5A \angle 22.6^\circ)}$$

d) Find  $I_2$


$$I_2 = I_s \frac{(8\Omega \angle -90^\circ)}{(8\Omega \angle -90^\circ) + (12\Omega \angle 0^\circ)} = \boxed{(1.94A \angle -33.7^\circ)}$$

e) Find  $V_L$

$$V_L = X_L \cdot I_s = (4\Omega \angle 90^\circ)(3.5A \angle 22.6^\circ) = \boxed{(14V \angle 112.6^\circ)}$$



17-2

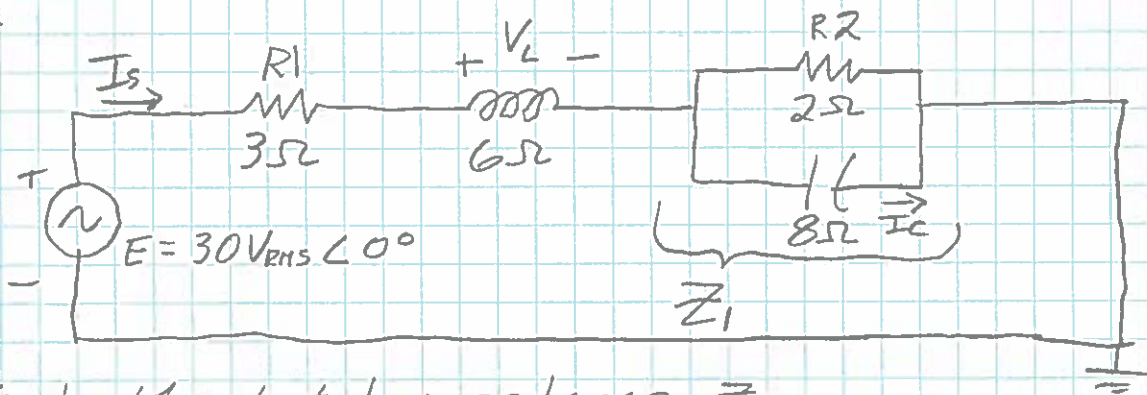

a) Find the total impedance  $Z_T$

$$Z_1 = 2 \Omega // 8 \Omega \angle 90 = \frac{2 \angle 0 \cdot 8 \angle 90}{2 + j8} = 1.94 \Omega \angle -14.04$$

$$Z_T = 3 \Omega \angle 0 + 6 \Omega \angle 90 + 1.94 \Omega \angle -14.04 = \boxed{7.38 \Omega \angle 48.56^\circ}$$

b) Find  $I_S$

$$I_S = \frac{E}{Z_T} = \frac{30 V_{RMS} \angle 0^\circ}{7.38 \Omega \angle 48.56^\circ} = \boxed{4.067 A \angle -48.56^\circ_{RMS}}$$

c) Find  $I_C$  using current divider


$$I_C = \frac{I_S \cdot R_2}{R_2 + Z_C} = 4.067 A \angle -48.56^\circ \left( \frac{2 \Omega \angle 0}{2 \Omega \angle 0 + 8 \Omega \angle 90} \right)$$

$$= \boxed{986.43 mA \angle -124.52^\circ_{RMS}}$$

d) Find  $V_L$  using voltage divider

$$V_L = \frac{E \cdot Z_L}{Z_T} = 30 V \angle 0^\circ \left( \frac{6 \Omega \angle 90}{7.38 \Omega \angle 48.56} \right) = \boxed{24.39 V_{RMS} \angle 41.44^\circ}$$

**Problem 17-5. For the network in Fig.17.42:**

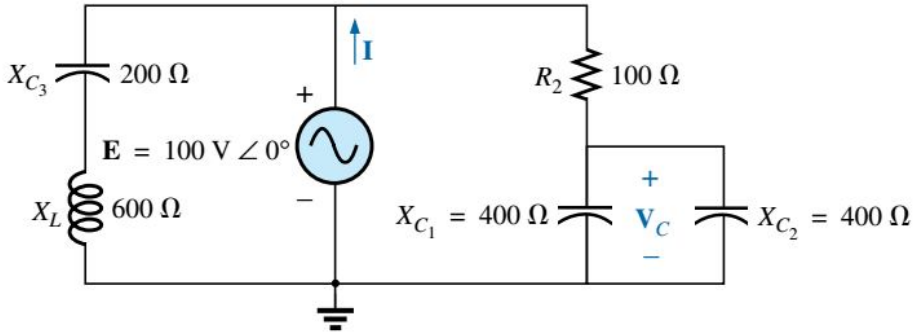

**FIG. 17.42**

*Problem 5.*


a.) Find the source current  $I$

Convert the elements to impedances and combine:

$$\begin{aligned}
 Z_1 &= Z_{R_2} + Z_{C_1} || Z_{C_2} \\
 &= 100 + (-j400) || (-j400) \\
 &= 100 - \frac{(j400)(j400)}{(j400) + (j400)} \\
 &= (100 - j200)\Omega = 223.6\Omega \angle -63.4^\circ
 \end{aligned}$$

$$\begin{aligned}
 Z_2 &= Z_{C_3} + Z_L \\
 &= -j400 + j600 \\
 &= j400\Omega = 400\Omega \angle 90^\circ
 \end{aligned}$$

The circuit can be redrawn as follows:

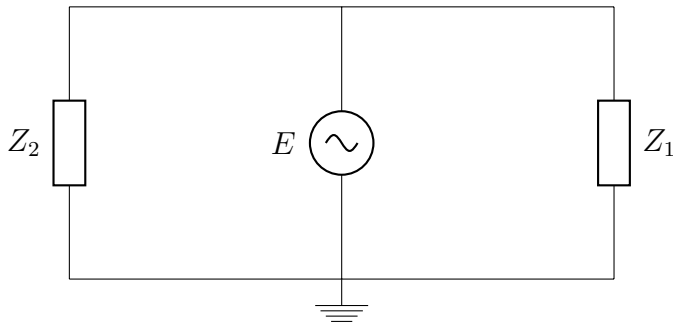

$$\begin{aligned}
\mathbf{Z}_T &= \mathbf{Z}_1 // \mathbf{Z}_2 \\
&= (223.6 \angle -63.4^\circ) + (400 \angle 90^\circ) \\
&= \frac{(223.6 \angle -63.4^\circ)(400 \angle 90^\circ)}{(223.6 \angle -63.4^\circ) + (400 \angle 90^\circ)} \\
&= 400 \angle -36.87^\circ
\end{aligned}$$

Therefore,  $\mathbf{I}$  can be calculated using ohms law as follows:

$$\begin{aligned}
\mathbf{I} &= \frac{\mathbf{E}}{\mathbf{Z}_T} \\
&= \frac{100 \text{ V}_{rms} \angle 0^\circ}{400 \angle -36.87^\circ} \\
&= 250 \text{ mA}_{rms} \angle 36.9^\circ
\end{aligned}$$

b.) Find the voltage  $\mathbf{V}_C$

$\mathbf{V}_C$  can be found using voltage divider between  $R_2$  and parallel combination of  $\mathbf{C}_1$  and  $\mathbf{C}_2$


$$\begin{aligned}
\mathbf{V}_C &= \mathbf{E} \cdot \frac{(\mathbf{Z}_{C_1} || \mathbf{Z}_{C_2})}{\mathbf{Z}_{R_2} + (\mathbf{Z}_{C_1} || \mathbf{Z}_{C_2})} \\
&= 100 \text{ V}_{rms} \angle 0^\circ \cdot \frac{(-j200)}{100 + (-j200)} \\
&= 89.44 \text{ V}_{rms} \angle -26.57^\circ = (80 - j40) \text{ V}_{rms}
\end{aligned}$$

c.) Find the average power delivered to the network

$$\begin{aligned}
P_{ave.} &= V_{rms} \cdot I_{rms} \cdot \cos(\theta_v - \theta_i) \\
&= 100 \cdot 250 \cdot \cos(-36.9^\circ) \\
&= 20 \text{ W}
\end{aligned}$$



**Problem 17-8.** For the network in Fig.17.45:

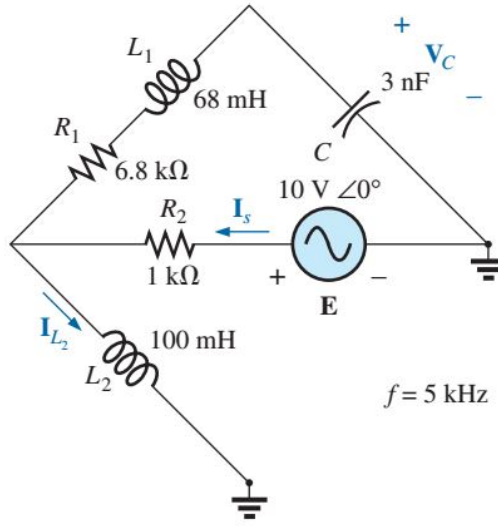

**FIG. 17.45**

*Problem 8.*

a.) Find the source current  $I_s$

Redraw the circuit before solving:


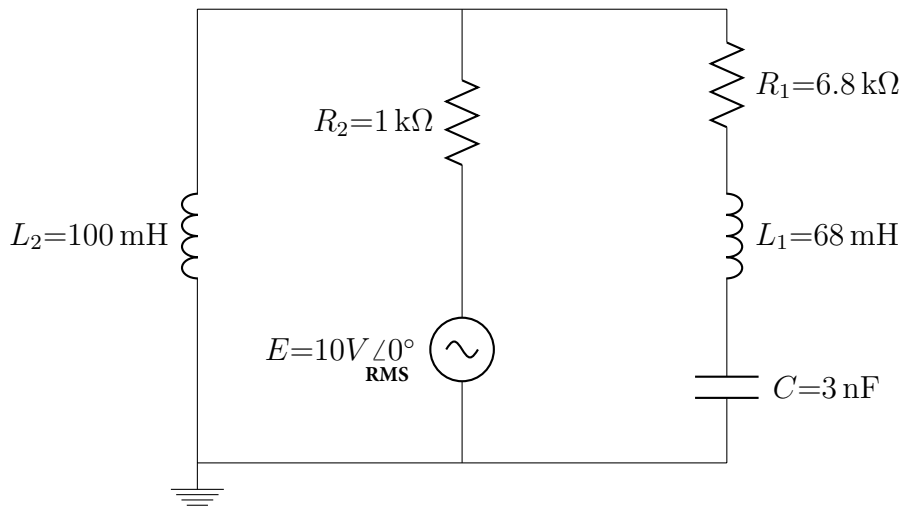


Figure 1: Parallel RLC circuit.

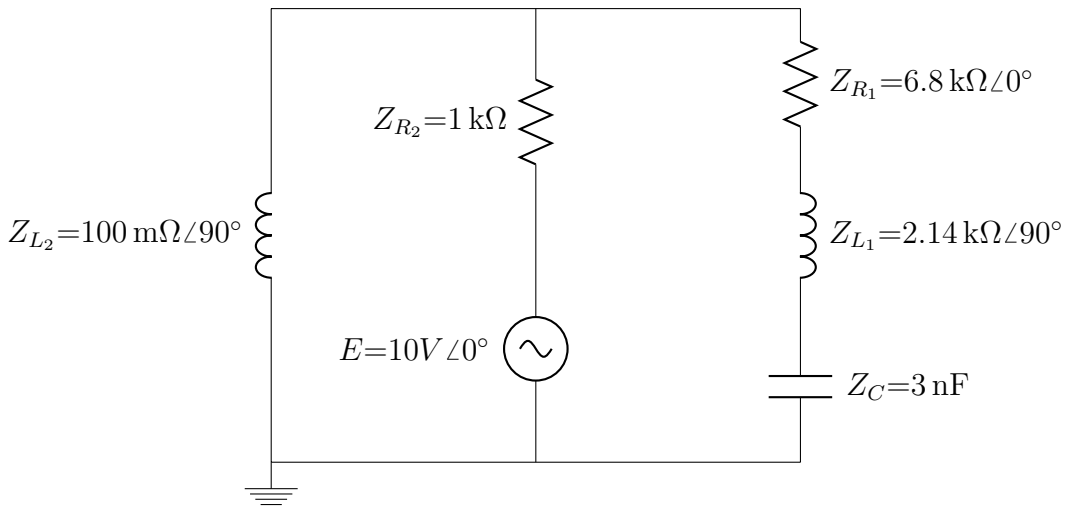Convert the elements to their respective impedances



$$\begin{aligned}
 \mathbf{Z}_{eq1} &= \mathbf{Z}_{R_1} + \mathbf{Z}_{L_1} + \mathbf{Z}_C \\
 &= 6.8 \text{ k}\Omega \angle 0^\circ + 2.14 \text{ k}\Omega \angle 90^\circ + 10.6 \text{ k}\Omega \angle -90^\circ \\
 &= 6.8 \text{ k}\Omega - j8.47 \text{ k}\Omega \\
 &= 10.86 \text{ k}\Omega \angle -51.24^\circ
 \end{aligned}$$

$$\mathbf{Z}_T = \mathbf{Z}_{R_1} + \mathbf{Z}_{L_2} \parallel \mathbf{Z}_{eq}$$

$$\begin{aligned}
 \mathbf{Z}_{eq2} = \mathbf{Z}_{L_2} \parallel \mathbf{Z}_{eq} &= \frac{(\mathbf{Z}_{L_2}) \cdot (\mathbf{Z}_{eq})}{\mathbf{Z}_{L_2} + \mathbf{Z}_{eq}} \\
 &= \frac{(3.14 \text{ k}\Omega \angle 90^\circ) \cdot (10.86 \text{ k}\Omega \angle -51.24^\circ)}{3.14 \text{ k}\Omega \angle 90^\circ + 10.86 \text{ k}\Omega \angle -51.24^\circ} \\
 &= 898.74 \Omega - j3.85 \text{ k}\Omega
 \end{aligned}$$

$$\begin{aligned}
 \mathbf{Z}_T &= 1 \text{ k}\Omega + \mathbf{Z}_{eq2} \\
 &= 1 \text{ k}\Omega + 898.74 \Omega - j3.85 \text{ k}\Omega \\
 &= 1898.74 \Omega + j3846.37 \Omega
 \end{aligned}$$

$$\begin{aligned}
 \mathbf{I}_S &= \frac{\mathbf{E}}{\mathbf{Z}_T} \\
 &= 1.03 \text{ mA}_{\text{RMS}} - j2.09 \text{ mA}_{\text{RMS}}
 \end{aligned}$$

b.) Find the voltage across the capacitor  $V_C$

Use current divider rule to find the current that flows through the capacitor  $I_C$ :

$$\begin{aligned} I_C &= \frac{Z_{L_2} I_s}{Z_{L_2} + (Z_{R_1} + Z_{L_1} + Z_C)} \\ &= \frac{(3.14 \text{ k}\Omega \angle 90^\circ)(1.03 \text{ mA} - j2.09 \text{ mA})_{\text{RMS}}}{(3.14 \text{ k}\Omega \angle 90^\circ) + (10.86 \text{ k}\Omega \angle -51.24^\circ)} \\ &= (0.848 \text{ mA} \angle 64.38^\circ)_{\text{RMS}} \end{aligned}$$

$$\begin{aligned} V_C &= I_C \cdot Z_C \\ &= (0.848 \text{ mA} \angle 64.38^\circ)_{\text{RMS}} \cdot (10.6 \text{ k}\Omega \angle -90^\circ) \\ &= (8.99 \text{ V} \angle -25.62^\circ)_{\text{RMS}} \end{aligned}$$

c.) Find the voltage  $V_{L_2}$


The voltage input voltage  $E$  is equal to the voltage drop over the resistor and the voltage drop over the parallel branch.

$$E = V_{R_2} + V_{L_2}$$

therefore

$$\begin{aligned} V_{L_2} &= E - V_{R_2} = E - I_S \cdot R_2 \\ &= 10 \text{ V} \angle 0^\circ_{\text{RMS}} - (1.03 \text{ mA} - j2.09 \text{ mA})_{\text{RMS}} \cdot 1 \text{ k}\Omega \\ &= 8.97 \text{ V} \angle \quad_{\text{RMS}} + j2.09 \text{ V} \quad_{\text{RMS}} \end{aligned}$$

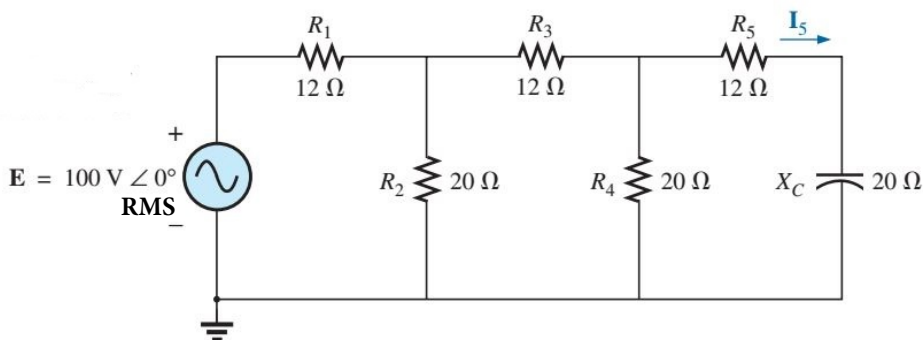**Problem 17-14.** Find the current  $I_5$  for the network in Fig.17.51. Note the effect of one reactive element on the resulting calculations.



Calculate the total impedance of the circuit  $Z_T$ :

$$\begin{aligned} Z_1 &= Z_{R_5} + Z_C \\ &= 12\Omega - j20\Omega = 23.38 \Omega \angle -59.04^\circ \end{aligned}$$

$$\begin{aligned} Z_2 &= Z_1 \parallel Z_{R_4} \\ &= \frac{Z_1 \cdot Z_{R_4}}{Z_1 + Z_{R_4}} = \frac{(23.38 \Omega \angle -59.04^\circ) \cdot (20\Omega)}{(23.38 \Omega \angle -59.04^\circ) + (20\Omega)} \\ &= 11.01 \Omega - j5.62 \Omega = 12.36 \Omega \angle -27.03^\circ \end{aligned}$$

$$\begin{aligned} Z_3 &= Z_2 + Z_{R_3} \\ &= 11.01 \Omega - j5.62 \Omega + 12\Omega \\ &= 23.01 \Omega - j5.62 \Omega = 23.69 \Omega \angle -13.72^\circ \end{aligned}$$

$$\begin{aligned} Z_4 &= Z_3 \parallel Z_{R_2} \\ &= \frac{(23.69 \Omega \angle -13.72^\circ) \cdot (20 \Omega)}{(23.69 \Omega \angle -13.72^\circ) + (20 \Omega)} \\ &= 10.86 \Omega - j1.19 \Omega = 10.92 \Omega \angle -6.28^\circ \end{aligned}$$

$$\begin{aligned} Z_T &= Z_4 + Z_{R_1} \\ &= 22.86 \Omega - j1.19 \Omega = 22.89 \Omega \angle -2.99^\circ \end{aligned}$$

The source current:


$$\begin{aligned} I_s &= \frac{E}{Z_T} \\ &= \frac{100 \text{ V} \angle 0^\circ}{22.89 \Omega \angle 2.99^\circ} \\ &= 4.37 \text{ A} \angle 2.991^\circ \end{aligned}$$

$$\begin{aligned}
 I_3 &= \frac{Z_{R_2} I_S}{Z_{R_2} + Z_3} \\
 &= 2.02 \text{ A} \angle 10.43^\circ \\
 &\quad \text{RMS}
 \end{aligned}$$


$$\begin{aligned}
 I_5 &= \frac{Z_{R_4} I_3}{Z_{R_4} + Z_1} \\
 &= 1.07 \text{ A} \angle 42.44^\circ \\
 &\quad \text{RMS}
 \end{aligned}$$

Because of the capacitor, the current leads the voltage. If the capacitor is replaced with an inductor, the current will lag the voltage.

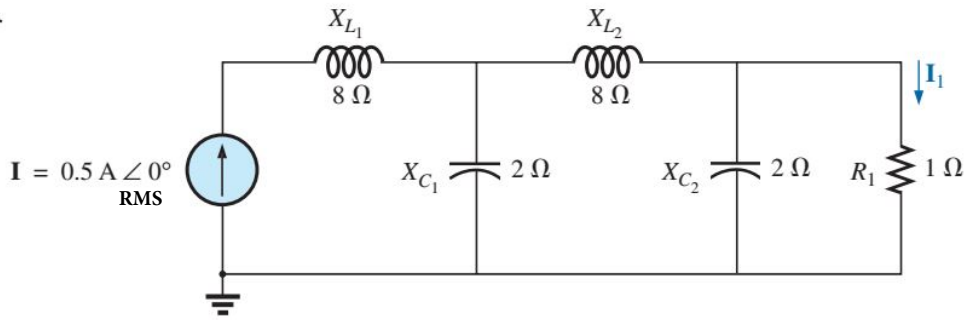
Problem 17-17.) Find the current  $I_1$  for the network in Fig. 17.54:



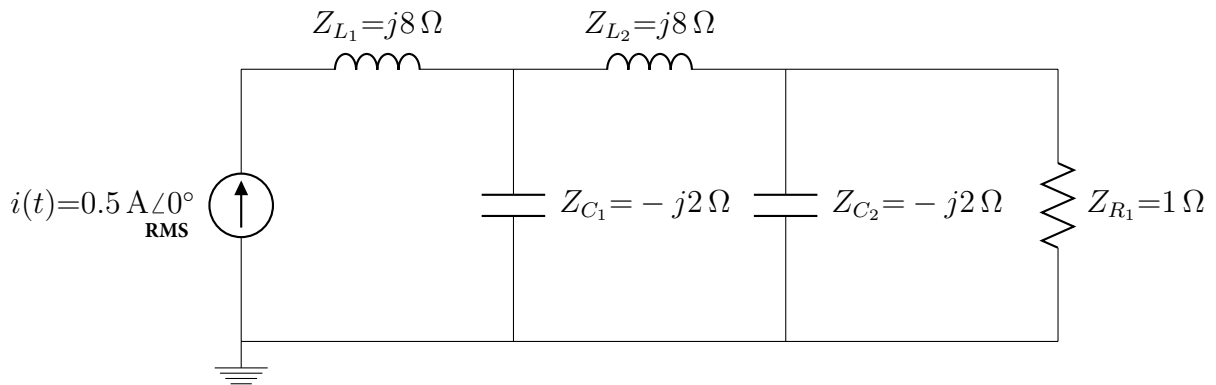Redraw the circuit replacing the circuit elements with their respective impedance



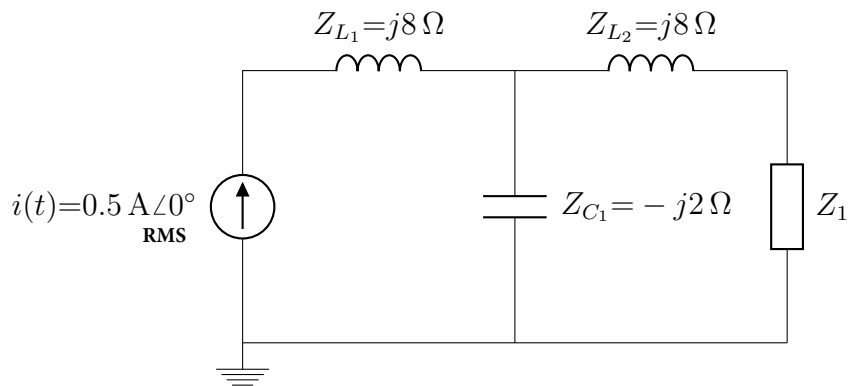Parallel combination of impedances  $Z_{R1}$  and  $Z_{C2}$  to get  $Z_1$



Series combination of  $Z_1$  and  $Z_{L2}$  to get  $Z_2$



$$\begin{aligned}\mathbf{Z}_1 &= \frac{(Z_{R_1})(Z_{C_2})}{(Z_{R_1}) + (Z_{C_2})} = \frac{(1\angle 0^\circ)(2\angle -90^\circ)}{(1\angle 0^\circ) + (2\angle -90^\circ)} \\ &= 0.8\Omega - j0.4\Omega = 0.894\Omega\angle -26.57^\circ\end{aligned}$$

$$\begin{aligned}\mathbf{Z}_2 &= Z_1 + Z_{L_2} = (0.8\Omega - j0.4\Omega) + (0 + j8) \\ &= 0.8\Omega + j7.6\Omega = 7.64\Omega\angle 83.99^\circ\end{aligned}$$

$$\begin{aligned}\mathbf{I}_{L_2} &= \frac{\mathbf{I}(\mathbf{Z}_{C_1})}{(\mathbf{Z}_{C_1}) + \mathbf{Z}_2} = \frac{(0.5\text{ A})(2\Omega\angle -90^\circ)}{(2\Omega\angle -90^\circ) + 7.64\Omega\angle 83.99^\circ} \\ &= -0.175\text{ A} - j0.025\text{ A} = 0.177\text{ A}\angle -171.87^\circ \\ &\quad \text{RMS}\end{aligned}$$

$$\begin{aligned}\mathbf{I}_1 &= \frac{\mathbf{I}_{L_2}(\mathbf{Z}_{C_2})}{(\mathbf{Z}_{C_2}) + \mathbf{Z}_{R_1}} = \frac{(0.177\text{ A}\angle -171.87^\circ)(2\Omega\angle -90^\circ)}{(2\Omega\angle -90^\circ) + 1\Omega\angle 0^\circ} \\ &= -0.15\text{ A} + j0.05\text{ A} = 158\text{ mA}\angle 161.57^\circ = 158\text{ mA}\angle -198.43^\circ \\ &\quad \text{RMS}\end{aligned}$$