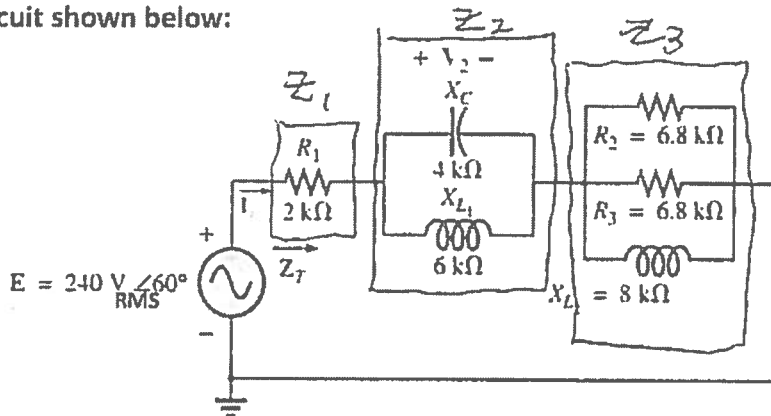


NAME (printed): SOLUTIONS Program: _____

This is a TIMED quiz – You have 15 minutes to complete. All 6 multiple-choice questions are equally weighted, there is no partial credit available – circle the most appropriate answer. Use your calculator and knowledge of AC circuits to answer the following questions about the circuit shown below:



$$Z_1 = 2K\Omega$$

$$Z_{3R} = \frac{(3.4K)(6.8K)}{3.4K + 6.8K}$$

$$Z_{3R} = (2.88K + j1.22K)$$

$$\frac{1}{Z_2} = \frac{1}{-j4K} + \frac{1}{j6K}$$

$$Z_{2R} = -j12K\Omega$$

1. Calculate Z_T in rectangular form:

- A) $(5.4K + j10.0K)\Omega$
 B) $(4.9K - j13.9K)\Omega$
 C) $(4.9K - j10.8K)\Omega$
 D) $(5.4K - j10.8K)\Omega$

$$Z_T = Z_1 + Z_2 + Z_3$$

$$Z_T = 4.9K\Omega - j10.8K\Omega$$

2. Determine Z_T in polar form (angle in degrees):

- A) $12.1K\Omega < 63^\circ$
 B) $11.4K\Omega < 62^\circ$
 C) $14.7K\Omega < 71^\circ$
 D) $11.8K\Omega < -66^\circ$

$$Z_T = 11.8K\Omega \angle -66^\circ$$

3. Find I_S in polar form (angle in radians):

- A) $20.3\text{ mArms} < 2.2\text{ rad}$
 B) $16.3\text{ mArms} < 0.02\text{ rad}$
 C) $19.8\text{ mArms} < 0.02\text{ rad}$
 D) $21.1\text{ mArms} < 2.2\text{ rad}$

$$I_S = \frac{240V_{RMS} \angle 60^\circ}{11.8K\Omega \angle -66^\circ} = 20.3\text{ mArms} \angle +126^\circ$$

$$I_S = 20.3\text{ mArms} \angle 2.2\text{ (rad)}$$

$$126^\circ = 2.2\text{ rad}$$

4. Calculate V_2 in polar form (angle in degrees):

- A) $238\text{ Vrms} < +36^\circ$
 B) $238\text{ Vrms} < -36^\circ$
 C) $33\text{ Vrms} < -36^\circ$
 D) $244\text{ Vrms} < 36^\circ$

$$\bar{V}_2 = \bar{I}_S Z_2 = (20.3\text{ mA} \angle 126^\circ)(12K \angle -90^\circ)$$

$$V_2 = 244V_{RMS} \angle +36^\circ$$

Problems 5 and 6 on the back →

5. Find the average power delivered to the network from the source:

A) 4.9 W

B) 3.5 W

C) 2.9 W

D) 2.0 W

$$P_A = V_{RMS} \cdot I_{RMS} \cdot \cos(\theta_V - \theta_I)$$
$$240 \cdot 20.3m \cdot 0.41$$

$$P_A = 2.0W$$

CHECK

$$P_A = I_R^2 R$$
$$= (20.3m)^2 \cdot 4.9K$$
$$= 2.0W \therefore$$

6. Find the power factor of the network:

A) 0.41 leading

B) 0.1 lagging

C) -0.1 leading

D) 0.40 lagging

CIRCUIT IS MOSTLY CAPACITIVE (ICE)

USING CURRENT AS A REFERENCE,
CURRENT LEADS VOLTAGE.