

Name (printed): \_\_\_\_\_ **Solutions** \_\_\_\_\_

Program: \_\_\_\_\_

All 6 questions are equally weighted, there is no partial credit. Circle the correct answer for each question.

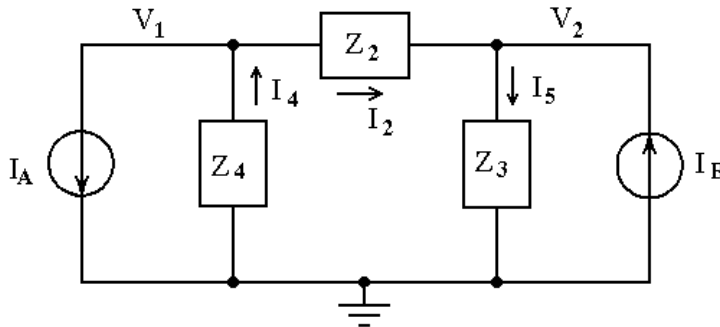



Figure 17.3

For the circuit shown above, answer the following questions:

- When setting up this circuit for nodal analysis, which one equation describes the application of KCL at node 1?
  - $I_2 = I_4 - I_5$
  - $I_A = I_4$
  - $I_5 = I_A + I_4$
  - $I_4 = I_A + I_2$
$$I_A + I_2 - I_4 = 0 \rightarrow I_A + I_2 = I_4$$
- Which one equation describes current  $I_2$ ?
  - $I_2 = -I_A$
  - $I_2 = (V_1 + V_2)/Z_2$
  - $I_2 = (V_1 - V_2)/Z_2$
  - $I_2 = I_4 + I_A$

Based on the direction of  $I_2$  indicated,  $I_2 = (V_1 - V_2)/Z_2$
- When setting up this circuit for nodal analysis, which one equation describes the application of KCL at node 2?
  - $I_2 = I_5 - I_B$
  - $I_A = I_4$
  - $I_5 = I_A + I_4$
  - $I_5 = I_2 - I_B$
$$-I_2 + I_5 - I_B = 0 \rightarrow I_2 = I_5 - I_B$$

Questions 4 through 6 on the back →

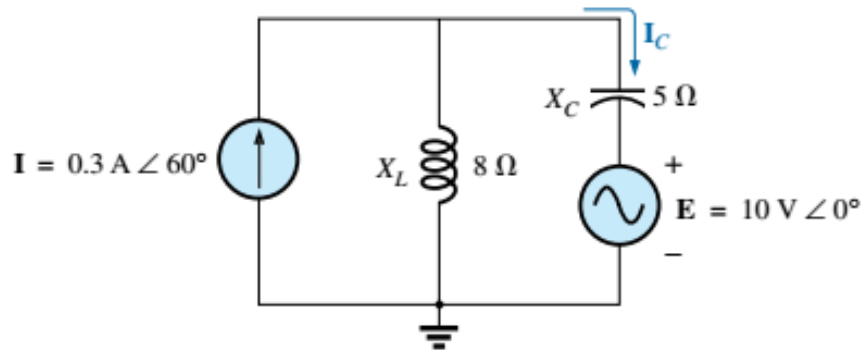

Note:  $I = 0.3 \text{ ARMS} \angle 60^\circ$ ,  $E = 10 \text{ VRMS} \angle 0^\circ$

For the circuit shown above, answer the following questions:

4. Find  $I_C$ , the current flowing through the capacitor (in the direction indicated):

- a.  $0.3 \text{ ARMS} \angle 60^\circ$
- b.  $1.26 \text{ ARMS} \angle -92.7^\circ$
- c.  $3.31 \text{ ARMS} \angle 92.7^\circ$
- d.  **$4.05 \text{ ARMS} \angle 84.3^\circ$**


See attached for details (P4, P5 and P6)

5. Determine the voltage across source I:


- a.  $26.9 \text{ VRMS} \angle -30^\circ$
- b.  **$30.2 \text{ VRMS} \angle -3.8^\circ$**
- c.  $4.3 \text{ VRMS} \angle 30^\circ$
- d.  $10 \text{ VRMS} \angle 180^\circ$

6. Find the voltage across the inductor due only to source E:

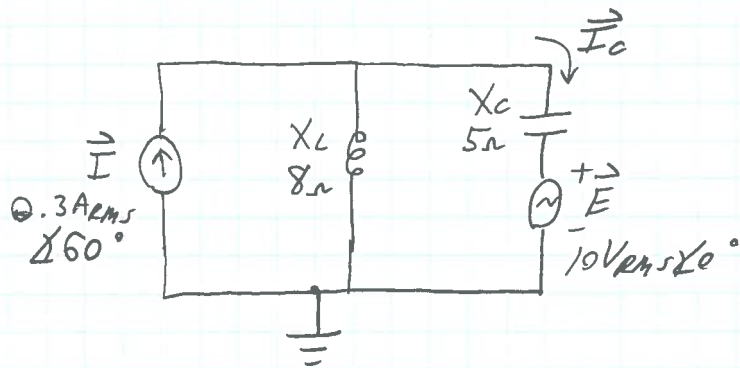- a.  $3.33 \text{ VRMS} \angle -56.6^\circ$
- b.  $4.00 \text{ VRMS} \angle -30^\circ$
- c.  **$26.7 \text{ VRMS} \angle 0^\circ$**
- d.  $32.1 \text{ VRMS} \angle 15.3^\circ$



$\vec{I}$  ACTIVE

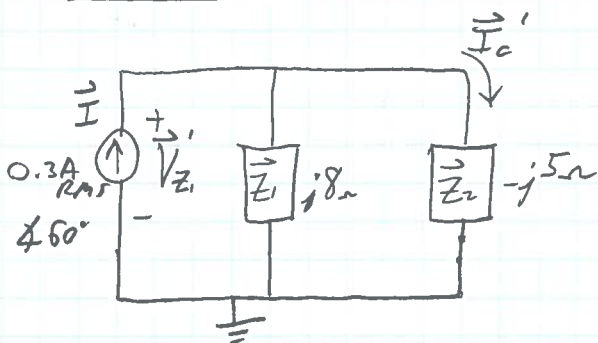

$$\vec{I}_C' = \vec{I} \cdot \frac{\vec{Z}_1 // \vec{Z}_2}{\vec{Z}_2}$$

$$= (0.3 A_{RMS} \angle 60^\circ) \left( \frac{-j13.33\Omega}{-j5\Omega} \right)$$


$$\vec{I}_C' = \boxed{0.8 A_{RMS} \angle 60^\circ}$$

$$\vec{V}_{Z_1}' = \vec{I}_C' \cdot \vec{Z}_2$$

$$= (0.8 A_{RMS} \angle 60^\circ) (-j5\Omega)$$

$$= \boxed{4 V_{RMS} \angle -30^\circ}$$

$\vec{E}$  ACTIVE

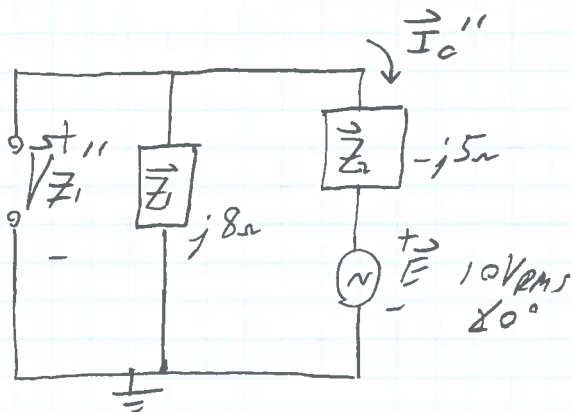

$$\vec{I}_C'' = \frac{-\vec{E}}{\vec{Z}_1 + \vec{Z}_2} = \frac{-10 V_{RMS} \angle 0^\circ}{j8\Omega + (-j5\Omega)}$$

$$\vec{I}_C'' = \boxed{3.33 A_{RMS} \angle 90^\circ}$$

$$\vec{V}_{Z_1}'' = (-\vec{I}_C'')(\vec{Z}_1)$$

$$= (3.33 A_{RMS} \angle 90^\circ)(j8\Omega)$$

$$\vec{V}_{Z_1}'' = \boxed{26.67 V_{RMS} \angle 0^\circ} \leftarrow \text{p\#6}$$

$$\vec{I}_C = \vec{I}_C' + \vec{I}_C'' = \boxed{4.05 A_{RMS} \angle 84.3^\circ} \leftarrow \text{p\#4}$$

$$\vec{V}_{Z_1} = \vec{V}_{Z_1}' + \vec{V}_{Z_1}'' = \boxed{30.2 V_{RMS} \angle -3.8^\circ} \leftarrow \text{p\#5}$$