

FULL NAME (Printed):

* SOLUTIONS *

RIT Program:

You have 50 minutes to complete this examination. You are allowed your calculator and the provided Formula Sheet from the text. If you brought a 3x5 card with additional formulas, please submit it with your exam.

- M/C Questions
 - Place the best alternative that answers the question in the blank space
 - NO partial credit will be awarded
- Work the Problem Questions
 - SHOW ALL your work in the space provided
 - BOX-IN your final answer
 - Partial credit may be awarded


1) What is the effective (or RMS) voltage for $v(t) = 10 \sin(\omega t - 50^\circ)$?1) A

A) 7.07 V

B) 20 V

C) 14.14 V

D) 10 V

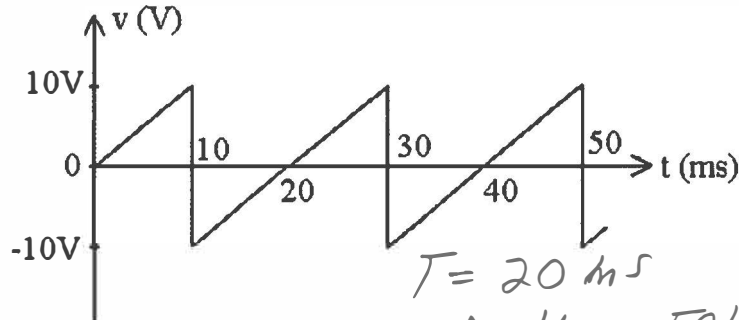

2) See Figure 13.1. What is the frequency of this waveform?

2) D

A) 33 Hz

B) 100 Hz

C) 20 Hz

D) 50 Hz

3) See Figure 13.1. What is the average value of this waveform?

3) D

A) +5 V

B) +10 V

C) +7.07 V

D) 0 V

4) See Figure 13.1. What is the period of this waveform?

4) D

A) 10 ms

B) 50 ms

C) 30 ms

D) 20 ms

5) What is the frequency of $v(t) = 35 \sin(5000t)$?

$$\omega = 5000 \text{ rad/s} = 2\pi f$$

$$f = \frac{5000}{2\pi} = 795.8 \text{ Hz}$$

5) A

A) 796 Hz

B) 35 r/s

C) 15,700 r/s

D) 5000 Hz

6) If $i(t) = 4 \sin(\omega t + 50^\circ)$ and $v(t) = 7 \sin(\omega t - 30^\circ)$, which one of these statements is TRUE?6) CA) i lags v by 80° .B) i lags v by 20° .C) i leads v by 80° . ✓D) i leads v by 20° .

$$50^\circ - (-30^\circ) = 80^\circ$$

- 7) Which one of the following phasor domain expressions is equivalent to the time domain expression $50 \sin(\omega t + 15^\circ)$? *PEAK* $50 \text{ Vpk} \angle 15^\circ$ or $35.4 \text{ VRMS} \angle 15^\circ$ 7) B
- A) $70.7 \text{ Vpk} \angle -15^\circ$ B) $50 \text{ Vpk} \angle 15^\circ$ C) $35 \text{ VRMS} \angle -15^\circ$ D) $70.7 \text{ VRMS} \angle 15^\circ$
- 8) Which one of the following polar values is equivalent to $30 + j40$? 8) B
- A) $70 \angle 36.9^\circ$ B) $50 \angle 53.1^\circ$ C) $70 \angle 53.1^\circ$ D) $50 \angle 36.9^\circ$
- 9) Which one of the following rectangular values is equivalent to the polar form $20 \angle 55^\circ$? 9) C
- A) $16.38 - j 11.47$ B) $16.38 + j 11.47$ C) $11.47 + j 16.38$ D) $11.17 - j 16.38$
- 10) The voltage across a 100 mH coil is $v(t) = 100 \sin 50t$. Which of these expressions describes the current? $I_m = \frac{V_m}{X_L} = \frac{100 \text{ V}}{\omega L} = \frac{100 \text{ V}}{(50 \text{ rad/s})(0.1 \text{ H})} = 20$ 10) A
- A) $20 \sin(50t - 90^\circ)$
 B) $20 \sin 50t$
 C) $2000 \sin(50t - 90^\circ)$
 D) $20 \sin(50t + 90^\circ)$
- 11) At what frequency does a $10 \mu\text{F}$ capacitor have a reactance of 100Ω ? $X_C = \frac{1}{\omega C}$ 11) B
- A) 1.59 kHz B) 159 Hz C) 1.59 MHz D) 15.9 kHz
- 12) What is the inductive reactance at 800 Hz of a 1 mH inductor with an internal resistance of 20Ω ? $f = \frac{1}{2\pi X_C C} = 159.2 \text{ Hz}$ 12) C
- A) 0.2Ω B) 12Ω C) 5.0Ω D) 20Ω
- 13) See Figure 14.2. What relationship exists between voltages v_1 and v_2 ? $X_L = 2\pi f L = 2\pi(800 \text{ Hz})(1 \text{ mH})$ 13) D

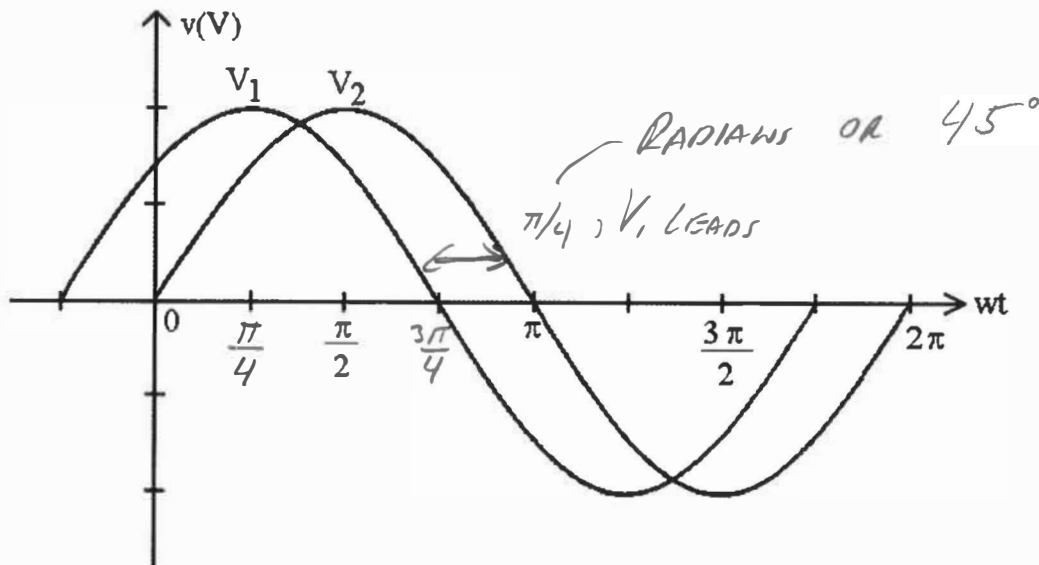


Figure 14.2

- A) v_1 leads v_2 by $(\pi/4)^\circ$. X
 B) v_1 lags v_2 by 45° .
 C) v_1 lags v_2 by $(\pi/4)^\circ$.
 D) v_1 leads v_2 by 45° . ✓

14) Which one of the following values is equivalent to $(5 - j3)(4 + j6)$?

14) C

A) $2 + j18$

B) $2 - j18$

C) $38 + j18$

D) $38 - j18$

15) What is the power factor in a system if $v(t) = 120 \sin(377t + 35^\circ)$ and $i(t) = 60 \sin(377t - 35^\circ)$?

15) D

A) 0.423 lagging

B) 1.0

C) 0.906 leading

D) 0.342 lagging

$$F = \cos(\theta_v - \theta_i) = \cos(35^\circ - (-35^\circ)) = \cos(70^\circ) = 0.342 \text{ LAGGING (I lags V)}$$

* Show your work and box in your answers for the remaining questions. Partial credit may be awarded *

16) See Figure 13.2. What is the average value of this waveform?

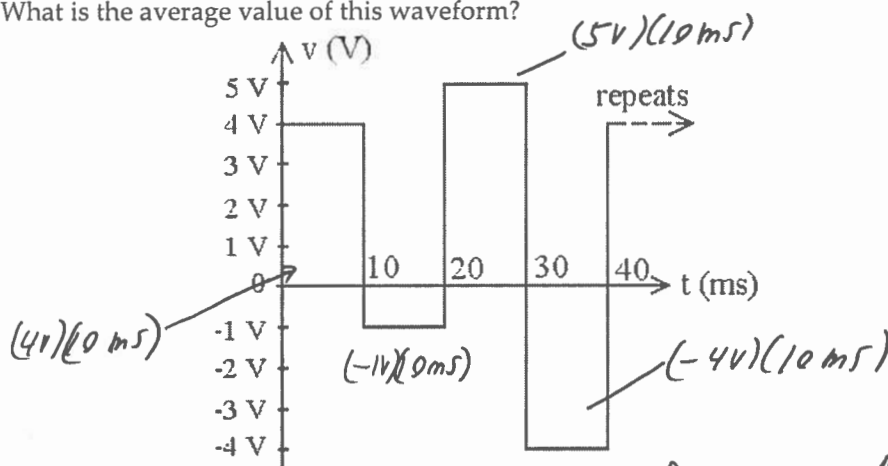


Figure 13.2

$$\text{Ave Value} = \frac{\text{Area Under Curve}}{\text{Length Under Curve}}$$

$$\begin{aligned} \text{Ave Value} &= \frac{(40 \text{ ms} \cdot \text{V}) + (-10 \text{ ms} \cdot \text{V}) + (50 \text{ ms} \cdot \text{V}) + (-40 \text{ ms} \cdot \text{V})}{40 \text{ ms}} \\ &= \frac{40 \text{ ms} \cdot \text{V}}{40 \text{ ms}} = \boxed{1 \text{ V}} \end{aligned}$$

17) Determine x in degrees if $(10 \angle x^\circ)(4 \angle -50^\circ) = 39.96 \angle 49.97^\circ$ R → P conv

$$(10)(4) \angle (x - 50)^\circ = 39.96 \angle 49.97^\circ$$

$$\therefore x - 50^\circ = 49.97^\circ$$

$$\text{OR} \\ x = 99.97 \sim \boxed{100^\circ}$$

18) Express $100 \sin(\omega t - 34^\circ)$ V in phasor form:

$$100V_{pk} \angle -34^\circ \quad \text{OR} \quad 70.71V_{RMS} \angle -34^\circ$$

19) How much power is dissipated by a resistor if the current through it is $i(t) = 12 \sin(\omega t + 30^\circ)$ and the voltage across it is $v(t) = 32 \sin(\omega t + 30^\circ)$?

$$P = V_{RMS} I_{RMS} \cos(\theta) = \left(\frac{32V}{\sqrt{2}}\right) \left(\frac{12V}{\sqrt{2}}\right) \cos(0^\circ)$$

$$192W$$

20) Find $v_a(t)$ in Figure 14.82 (below), given that $e_{in}(t) = 60 \sin(377t)$ and $v_b(t) = 20 \sin(377t - 45^\circ)$:

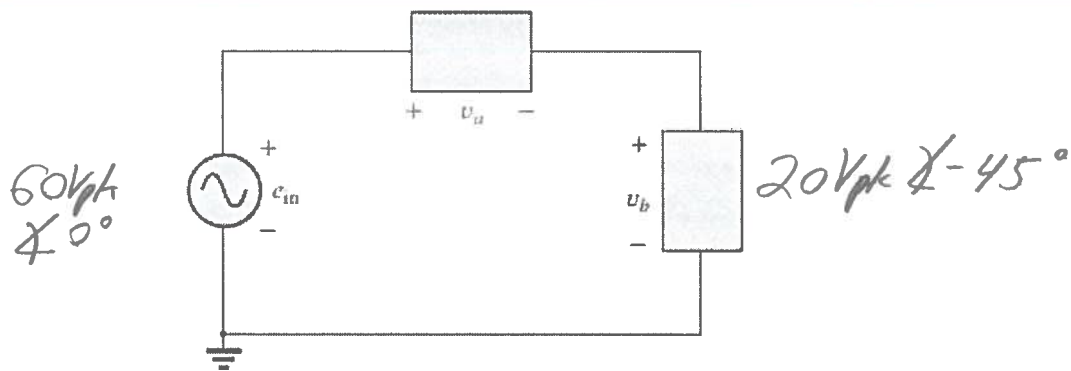


FIG. 14.82

$$\vec{E}_{in} = \vec{V}_a + \vec{V}_b, \text{ KVL}$$

$$\therefore \vec{V}_a = \vec{E}_{in} - \vec{V}_b$$

$$= 60V_{pk} \angle 0^\circ - 20V_{pk} \angle -45^\circ$$

$$\vec{V}_a = 47.99V_{pk} \angle 17.14^\circ$$

$$\therefore v_a(t) = 48 \sin(377t + 17.1^\circ) V$$