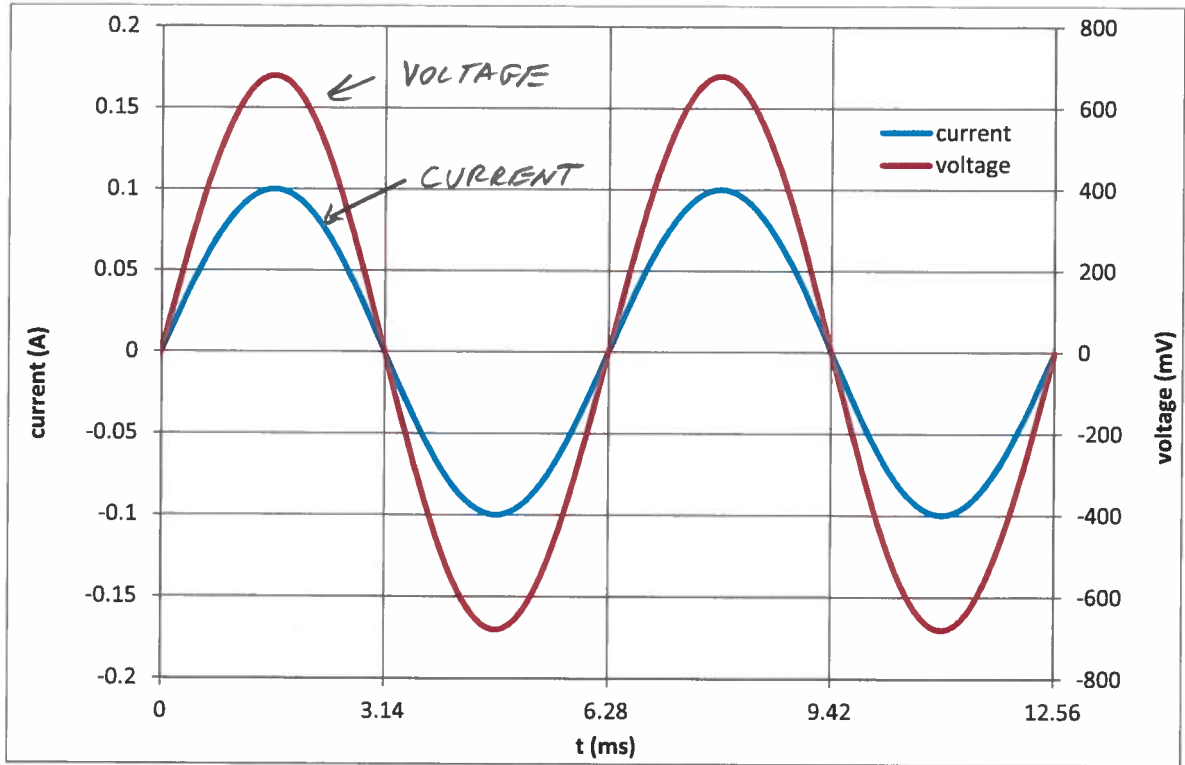


P14-5) The current through a $6.8 \text{ k}\Omega$ resistor is as indicated. Find the sinusoidal expression for the voltage. In addition, sketch the v and i sinusoidal waveforms on the same axis.

a.

$$i = 0.1 \sin(1000 t)$$

$$v = 680 \sin(1000 t)$$



7/24

P14-6

DETERMINE X_L (IN OHMS) For $L = 2\text{mH}$ +
 $f =$

a) DC

b) 60Hz

c) 4kHz

d) 1.2MHz

$$X_L = 2\pi fL$$

a) DC, $f = 0$ \therefore $X_L = 0\Omega$ s/c

b) $f = 60\text{Hz}$, $X_L = 2\pi(60\text{Hz})(2\text{mH})$
 $X_L = 0.754\Omega$

c) $f = 4\text{kHz}$, $X_L = 2\pi(4000\text{Hz})(2\text{mH})$
 $X_L = 50.27\Omega$

d) $f = 1.2\text{MHz}$, $X_L = 2\pi(1.2\text{E}6\text{Hz})(2\text{mH})$
 $X_L = 15,080\Omega$

P14-7

DETERMINE THE CLOSEST STANDARD VALUE
INDUCTANCE WITH:

a) $X_L = 2k\Omega$ @ $f = 14.47kHz$

b) $X_L = 40k\Omega$ @ $f = 5.3kHz$

$$X_L = 2\pi fL$$

$$\therefore L = \frac{X_L}{2\pi f}$$

a) $L = \frac{2000\Omega}{2\pi(14.47kHz)} = 21.998mH$

OR

$$\boxed{22mH}$$

b) $L = \frac{40,000\Omega}{2\pi(5.3kHz)} = 1.201H$

OR

$$\boxed{1.2H}$$

(MULTIPLE ONLINE REFERENCES
FOR "STANDARD" INDUCTOR VALUES)

P14-8

DETERMINE THE FREQUENCY FOR WHICH A
47 mH INDUCTOR HAS:

(a) $X_L = 10\Omega$

(b) $X_L = 4k\Omega$

(c) $X_L = 12k\Omega$

$$X_L = 2\pi fL$$

$$\therefore f = \frac{X_L}{2\pi L}$$


$$(a) f = \frac{10\Omega}{(2\pi)(47\text{mH})} = \boxed{33.86 \text{ Hz}}$$

$$(b) f = \frac{4k\Omega}{(2\pi)(47\text{mH})} = \boxed{13,545 \text{ Hz}}$$

$$(c) f = \frac{12k\Omega}{(2\pi)(47\text{mH})} = \boxed{40,635 \text{ Hz}}$$

P14-9) The current through a $20\ \Omega$ inductive reactance is given. What is the sinusoidal expression for the voltage? Sketch the v and i sinusoidal waveforms on the same axis.

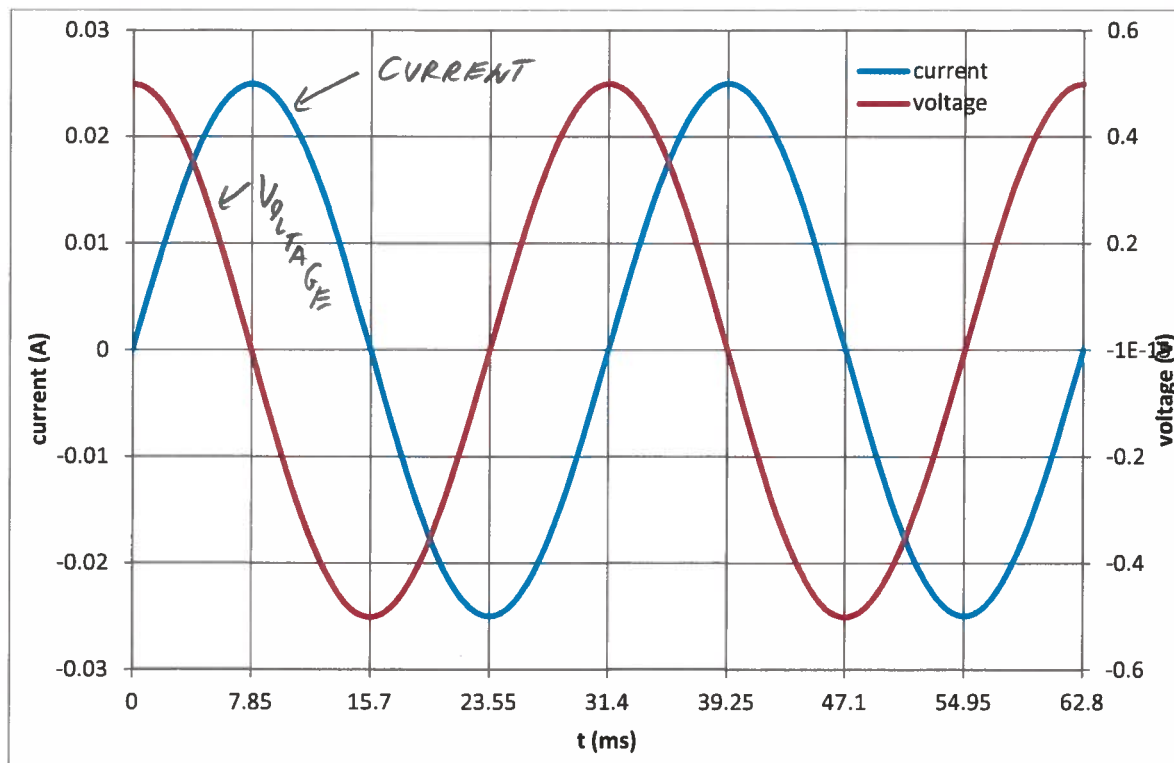a. $i = 25 \times 10^{-3} \sin(200t)$ $v = 0.5 \sin(200t + 90^\circ) = 0.5 \cos(200t)$




11/24

(P14-9)

(b)

$$i = 40 \times 10^{-3} \sin(\omega t + 60^\circ)$$
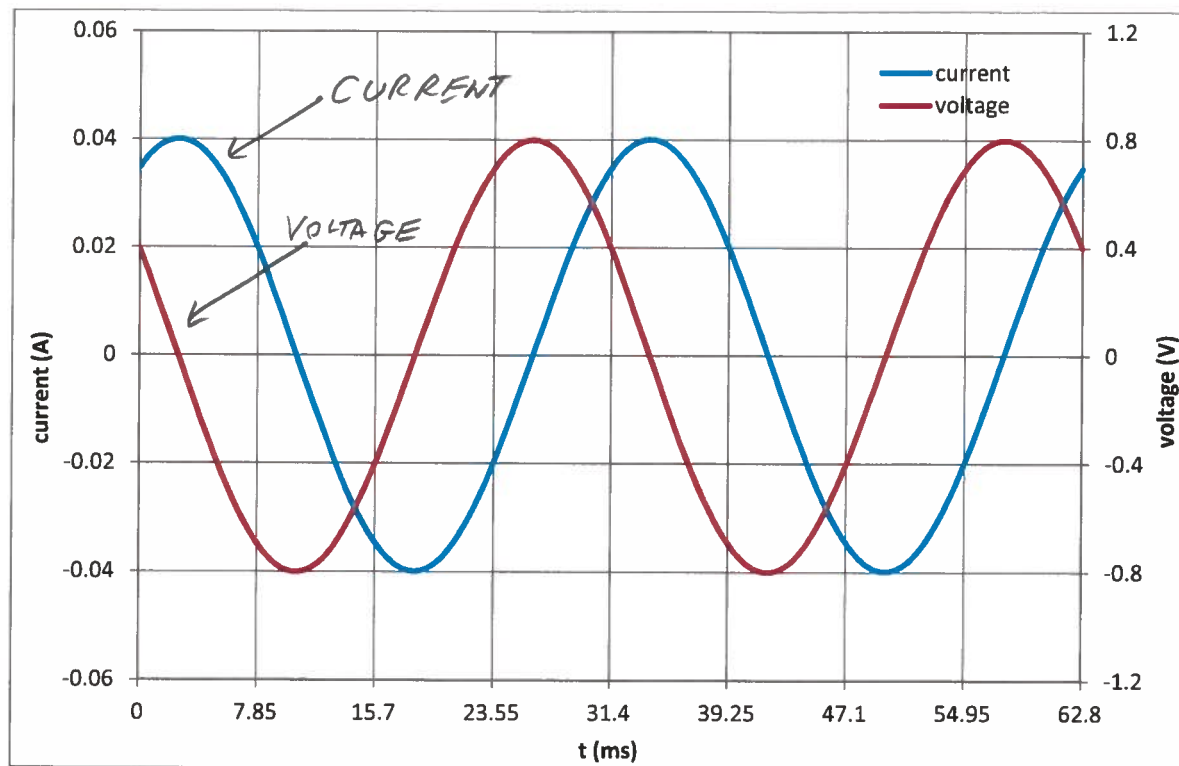
$$v = 0.8 \sin(\omega t + 150^\circ) = 0.8 \cos(\omega t + 60^\circ)$$



12/24

P14-13

FIND X_C , GIVEN $C = 0.2 \mu F$ +

(a) $f = 0 \text{ Hz}$ (DC)

(b) $f = 60 \text{ Hz}$

(c) $f = 2 \text{ kHz}$

(d) $f = 2 \text{ MHz}$

$$X_C = \frac{1}{2\pi f C}$$

∴ a) $f = 0 \text{ Hz}$, $X_C = \frac{1}{2\pi(0)(0.2 \mu F)} = \begin{matrix} \infty \Omega \\ \text{OR } \infty \\ 0/C \end{matrix}$

b) $f = 60 \text{ Hz}$, $X_C = \frac{1}{(2\pi)(60 \text{ Hz})(0.2 \mu F)}$
 $= 13,263 \Omega$

c) $f = 2 \text{ kHz}$, $X_C = \frac{1}{(2\pi)(2 \text{ kHz})(0.2 \mu F)}$
 $X_C = 397.9 \Omega$

d) $f = 2 \text{ MHz}$, $X_C = \frac{1}{(2\pi)(2 \text{ MHz})(0.2 \mu F)}$
 $X_C = 0.398 \Omega$

P14-15

DETERMINE THE FREQUENCY AT WHICH A $3.9\mu F$ CAPACITOR HAS:

(a) $X_c = 10\Omega$

(b) $X_c = 60k\Omega$

(c) $X_c = 0.1\Omega$

(d) $X_c = 2000\Omega$

$$X_c = \frac{1}{2\pi fC} \quad \therefore \quad f = \frac{1}{(2\pi)(X_c)(C)}$$

a) $X_c = 10\Omega$, $f = \frac{1}{(2\pi)(10\Omega)(3.9\mu F)} = \boxed{4,081 \text{ Hz}}$


b) $X_c = 60k\Omega$, $f = \frac{1}{(2\pi)(60k\Omega)(3.9\mu F)} = \boxed{0.680 \text{ Hz}}$

c) $X_c = 0.1\Omega$, $f = \frac{1}{(2\pi)(0.1\Omega)(3.9\mu F)} = \boxed{408.1 \text{ kHz}}$

d) $X_c = 2000\Omega$, $f = \frac{1}{(2\pi)(2000\Omega)(3.9\mu F)} = \boxed{20.4 \text{ Hz}}$

14/24

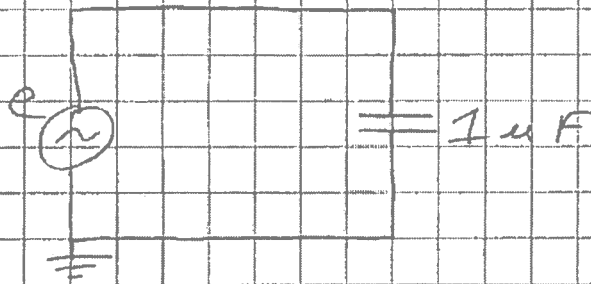14-17 The voltage across a $1\mu\text{F}$ capacitor is given. What is the sinusoidal expression for the current



a) $\overset{(30)}{30} \sin 200t$

$$X_C = \frac{1}{\omega C} = \frac{1}{200 \cdot 1\mu\text{F}} = 5\text{ k}\Omega$$

$$I_m = \frac{V_m}{X_C} = \frac{30\text{ V}}{5\text{ k}\Omega} = 6.0 \times 10^{-3}\text{ A}$$

i leads v , so $i = 6.0 \times 10^{-3} \sin(200t + 90^\circ)\text{ A}$

b) $60 \times 10^{-3} \sin 377t$

$$X_C = \frac{1}{\omega C} = \frac{1}{377 \cdot 1\mu\text{F}} = 2.653\text{ k}\Omega$$

$$I_m = \frac{V_m}{X_C} = \frac{0.060\text{ V}}{2.653\text{ k}\Omega} = 22.62\text{ }\mu\text{A}$$

$i = 22.62 \times 10^{-6} \sin(377t + 90^\circ)\text{ A}$

14-19 The current through a $0.56 \mu\text{F}$ capacitor is given. What is the sinusoidal expression for the voltage

a) $i = 0.20 \sin 300t$

$$X_C = \frac{1}{\omega C} = \frac{1}{300 \cdot 0.56 \mu\text{F}} = 5.952 \text{ k}\Omega$$

$$V_M = I_M X_C = 0.20 \cdot 5.952 \text{ k} = 1190.48 \text{ V}$$

v lags i, so $v = 1190.48 \sin(300t - 90^\circ)$ ✓

b) $i = 8 \times 10^3 \sin(377t - 30^\circ)$

$$X_C = \frac{1}{\omega C} = \frac{1}{377 \cdot 0.56 \mu\text{F}} = 4.737 \text{ k}\Omega$$

$$V_M = I_M X_C = 8 \text{ mA} \cdot 4.737 \text{ k} = 37.893 \text{ V}$$


$$-30^\circ - 90^\circ = -120^\circ$$

$v = 37.893 \sin(377t - 120^\circ)$ ✓

16/24

P14-20a

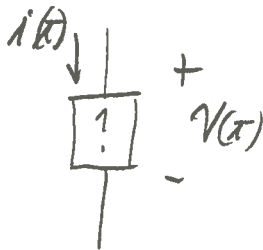INDICATE WHETHER THE ELEMENT INVOLVED IS A CAPACITOR, INDUCTOR OR RESISTOR + FIND ITS VALUE IF ENOUGH INFO IS PROVIDED:



$$V(t) = 550 \sin(377t + 50^\circ)$$

$$i(t) = 11 \sin(377t - 40^\circ)$$

V LEADS i BY $90^\circ \therefore ? = \boxed{\text{INDUCTOR}}$

VALUE : $X_L = 2\pi fL = \omega L$

$$\omega = 377 \text{ RAD/SEC}$$

$$\text{BUT } X_L = \frac{V_m}{I_m} = \frac{550 \text{ V}}{11 \text{ A}} = 50 \Omega$$

\therefore WE HAVE : $50 \Omega = (377 \text{ RAD/SEC})(L)$

$$\boxed{L = 132.6 \text{ mH}}$$

17/24

fx

=2*PI()*C5*\$D\$2

← *NOTE THE FORMULA FOR X_L

C

D

E

F

G

H

I

J

K

L

M

I

L

0.2
3.00E-03 (H)P14-22: Plot X_L versus frequency for a 3mH coil using a frequency range of zero to 100kHz on a linear scale

f (Hz)

X_L (Ohms)ANS
CELL

0

0.00

4000

75.40

8000

150.80

12000

226.19

16000

301.59

20000

376.99

24000

452.39

28000

527.79

32000

603.19

36000

678.58

40000

753.98

44000

829.38

48000

904.78

52000

980.18

56000

1055.58

60000

1130.97

64000

1206.37

68000

1281.77

72000

1357.17

76000

1432.57

80000

1507.96

84000

1583.36

88000

1658.76

92000


1734.16

96000

1809.56


100000

1884.96

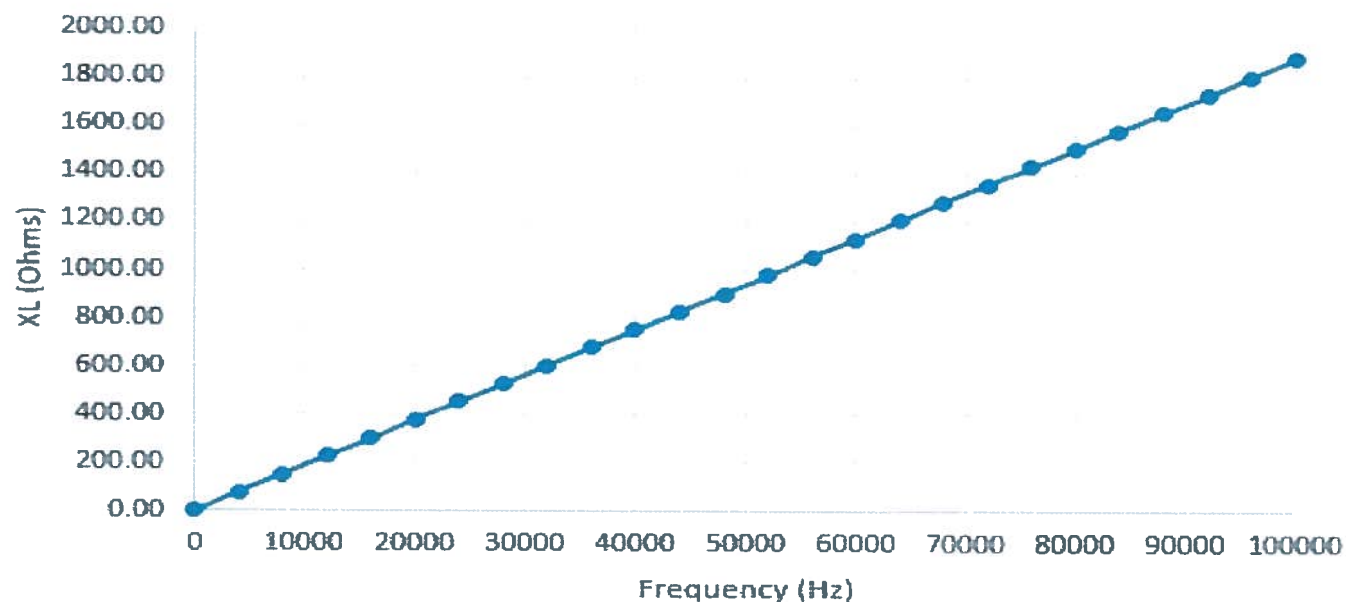Inductive Reactance as a Function of Frequency
(L=3mH)

18/24

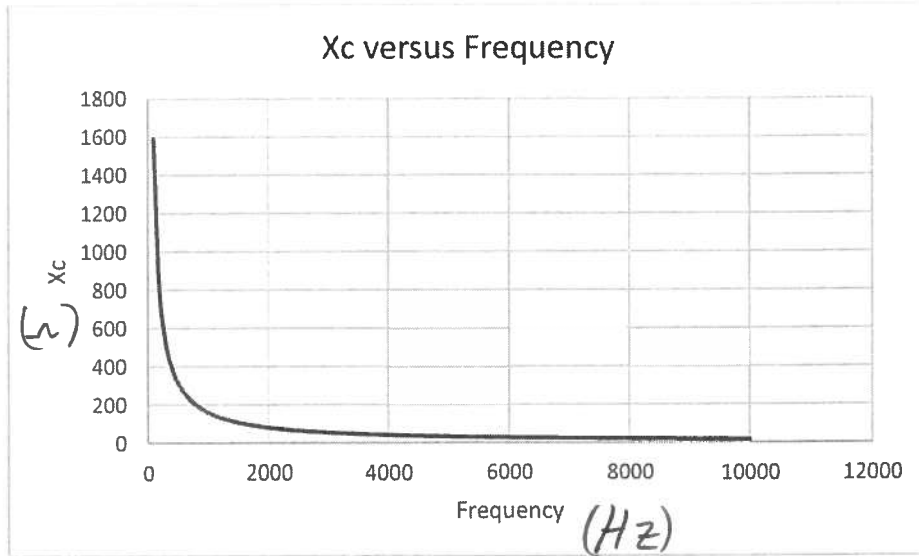14-23 Plot X_c versus frequency for a $1\mu\text{F}$ capacitor using a frequency range of zero to 10 kHz on a linear scale.



19/24

P14-25

THE REACTANCE OF A COIL EQUALS THE RESISTANCE OF A $10\text{ k}\Omega$ RESISTOR AT $f = 5\text{ kHz}$. DETERMINE THE INDUCTANCE OF THE COIL.

$$X_L = 10\text{ k}\Omega @ f = 5\text{ kHz}$$

$$\text{BUT } X_L = 2\pi fL$$

$$\therefore 10\text{ k}\Omega = (2\pi)(5\text{ kHz})(L)$$

$$\text{HENCE } \boxed{L = 318.3\text{ mH}}$$

P14-27

FIND C SUCH THAT $X_C = X_L$ FOR $L = 2\text{ mH}$
 $f = 50\text{ kHz}$

$$X_C = \frac{1}{2\pi fC}$$

$$X_L = 2\pi fL$$

EQUATING @ 50 kHz W/ $L = 2\text{ mH}$:

$$\frac{1}{(2\pi)(50\text{ kHz})(C)} = 2\pi(50\text{ kHz})(2\text{ mH})$$

$$\text{YIELDS } \boxed{C = 5.07\text{ nF}}$$

20/24

P14-28 (a+b)

FIND THE AVERAGE POWER LOSS + POWER FACTOR FOR EACH CIRCUIT WITH:

$i(x)$



(a) $V(x) = 60 \sin(\omega x + 30^\circ)$ V

$i(x) = 15 \sin(\omega x + 60^\circ)$ A

(b) $V(x) = -50 \sin(\omega x - 20^\circ)$ V

$i(x) = -2 \sin(\omega x - 20^\circ)$ A

$$P_{AVE} = \frac{V_m I_m}{2} \cos(\theta), \quad \theta = \theta_v - \theta_i$$

$$PF = \cos \theta$$

a) $P_{AVE} = \frac{(60V)(15A)}{2} \cos(30^\circ - 60^\circ)$

$$P_{AVE} = 389.7W$$

$$PF = \cos(-30^\circ) = 0.866$$

b) $P_{AVE} = \frac{(50V)(2A)}{2} \cos(-20^\circ - (-20^\circ))$

$$P_{AVE} = 50W$$

$$PF = \cos(0^\circ) = 1$$

21/24

14-29 If the current through and the voltage across an element are $i = 8 \sin(\omega t + 40^\circ)$ and $v = 48 \sin(\omega t + 40^\circ)$, compute the power by $I^2 R$, $(V_m I_m / 2) \cos \theta$, and $VI \cos \theta$, and compare answers.

$$R = \frac{V_m}{I_m} = \frac{48 \text{ V}}{8 \text{ A}} = 6 \Omega$$

$$P = I^2 R = \left(\frac{8 \text{ A}}{\sqrt{2}} \right)^2 \cdot 6 \Omega = \boxed{192 \text{ W}} \quad \text{*RMS Values}$$

$$P = \frac{V_m I_m}{2} \cos \theta = \frac{48 \text{ V} \cdot 8 \text{ A}}{2} \cdot \cos 0 = \boxed{192 \text{ W}}$$

$$P = VI \cos \theta = \left(\frac{48 \text{ V}}{\sqrt{2}} \right) \left(\frac{8 \text{ A}}{\sqrt{2}} \right) \cos 0 = \boxed{192 \text{ W}}$$

Same

22/24

P14-31

THE POWER FACTOR OF A CIRCUIT IS 0.5 LAGGING.
 $P_{\text{DELIVERED}} = 500\text{W}$.

GIVEN : $V_{iN}(x) = 50 \sin(\omega x + 10^\circ) \text{ V}$

FIND : $i_N(x)$

$$\text{PF} = \cos(\theta)$$

$$\therefore 0.5 = \cos(\theta) \quad , \quad \theta = |\theta_v - \theta_i| = \underline{60^\circ}$$

LAGGING PF \Rightarrow I LAGS V

$$P = 500\text{W} = \frac{V_m I_m}{2} \cos(\theta)$$

$$\text{OR } 500\text{W} = \frac{50\text{V}(I_m)}{2} (0.5)$$


$$\text{YIELDS : } \underline{I_m = 40\text{A}}$$

$$\text{HENCE } i(x) = 40 \sin(\omega x + 10^\circ - 60^\circ)$$

OR

$$\boxed{i(x) = 40 \sin(\omega x - 50^\circ) \text{ A}}$$

14-33

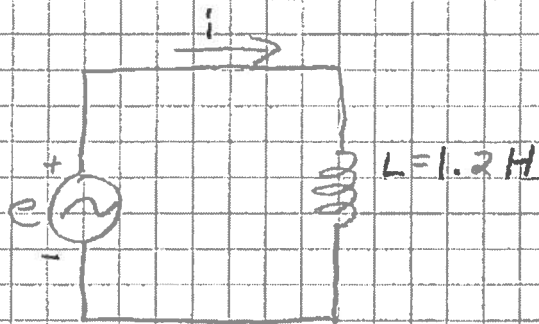

$$e = 220 \sin(1000t + 60^\circ)$$

a) Find the sinusoidal expression for i

$$X_L = \omega L = 1000 \cdot 1.2 \text{ H} = 1.2 \text{ k}\Omega$$

$$I_m = \frac{V_m}{X_L} = \frac{220 \text{ V}}{1.2 \text{ k}\Omega} = 183.33 \text{ mA}$$

For an inductor, i lags e by 90° , so the phase angle of i is $60^\circ - 90^\circ = -30^\circ$

$$i = 183.33 \times 10^{-3} \sin(1000t - 30^\circ)$$

A

b) Find the average power loss by the inductor

$$P = \frac{V_m I_m \cos \theta}{2}$$

$$\cos(90^\circ) = 0$$

$$P = 0 \text{ W}$$

24/24