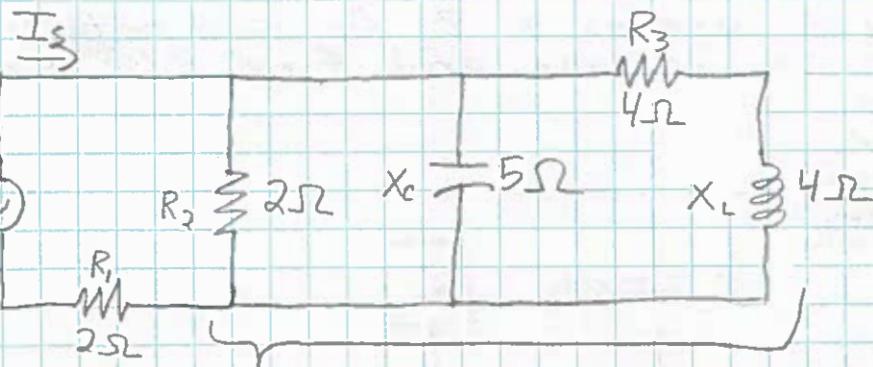


20-9

a) Find I_s

$$\begin{aligned} Z_T &= 2\Omega \angle 0^\circ + 2\Omega \angle 0^\circ // 5\Omega \angle -90^\circ // (4 + j4) \\ &= 2\Omega \angle 0^\circ + 1.589 \angle -6.843^\circ = 3.582\Omega \angle -3.029^\circ \end{aligned}$$

$$I_s = \frac{E}{Z_T} = \frac{20V_{RMS} \angle 0^\circ}{3.582\Omega \angle -3.029^\circ} = 5.58A_{RMS} \angle 3.03^\circ$$

b) Find the average power delivered to each element

$$P_{R1} = I_s^2 R_1 = 5.58A_{RMS}^2 \cdot 2\Omega = 62.27W$$

$$\begin{aligned} V_{R2} &= E - V_{R1} \\ &= E - I_s R_1 = 20V \angle 0^\circ - 5.58A \angle 3.03^\circ \cdot 2\Omega \angle 0^\circ \\ &= 20V \angle 0^\circ - 11.16 \angle 3.03^\circ \\ &= 8.88V_{RMS} \angle -3.81^\circ \end{aligned}$$

$$P_{R2} = \frac{V_{R2}^2}{R_2} = \frac{8.88V_{RMS}^2}{2\Omega} = 39.43W$$

$$I_{R3} = \frac{8.88V_{RMS} \angle -3.81^\circ}{4 + j4} = 1.57A_{RMS} \angle -48.81^\circ$$

$$P_{R3} = I_{R3}^2 \cdot R_3 = 1.57A_{RMS}^2 \cdot 4\Omega = 9.86W$$

c) Find the reactive power for each element

$$Q_{XC} = \frac{V_{R2}^2}{X_C} = \frac{8.88V_{RMS}^2}{5\Omega} = 15.771 \text{ VAR(C)}$$

$$Q_{XL} = I_{R3}^2 \cdot X_L = 1.57A_{RMS}^2 \cdot 4\Omega = 9.86 \text{ VAR(L)}$$

d) Find the apparent power for each element

| | |
|------------------|------------------------------------|
| R ₁ : | $S_T = P_{R1} = 62.27 \text{ VA}$ |
| R ₂ : | $S_T = P_{R2} = 39.43 \text{ VA}$ |
| R ₃ : | $S_T = P_{R3} = 9.86 \text{ VA}$ |
| C: | $S_T = Q_{XC} = 15.771 \text{ VA}$ |
| L: | $S_T = Q_{XL} = 9.86 \text{ VA}$ |

c) Find P_T , Q_T , S_T , and F_p for the system

$$P_T = P_{R1} + P_{R2} + P_{R3} = 62.27W + 39.43W + 9.86W$$

$$= 111.56W$$

$$Q_T = Q_{xc} - Q_{xL} = 15.771 \text{ VAR}(C) - 9.86 \text{ VAR}(L)$$

$$= 5.911 \text{ VAR}(C)$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \sqrt{111.56^2 + 5.911^2} = 111.716 \text{ VA}$$

$$F_p = \frac{P_T}{S_T} = \frac{111.56}{111.716} = 0.999 \text{ leading}$$

f) Sketch the power triangle



20-12 An electrical system is rated 10kVA, 200V at a 0.5 leading power factor.

a) Find the impedance of the system in rectangular coordinates

$$I_s = \frac{S_T}{E} = \frac{10\text{kVA}}{200\text{V RMS}} = 50\text{A RMS}$$

$$F_p = 0.5 \\ \cos \theta = 0.5$$


$$\theta = \cos^{-1} 0.5 = 60^\circ \quad I_s \text{ leads } E \text{ by } 60^\circ \\ \therefore I_s = 50\text{A L } 60^\circ$$

$$Z_T = \frac{E}{I_s} = \frac{200\text{V L } 0^\circ}{50\text{A L } 60^\circ} = \boxed{2 - j 3.464} \text{ Ohms}$$

b) Find the average power delivered to the system

$$F_p = \frac{P_T}{S_T} \Rightarrow P_T = F_p S_T = 0.5 \cdot 10\text{kVA} = \boxed{5\text{KW}}$$

(14) For the system:

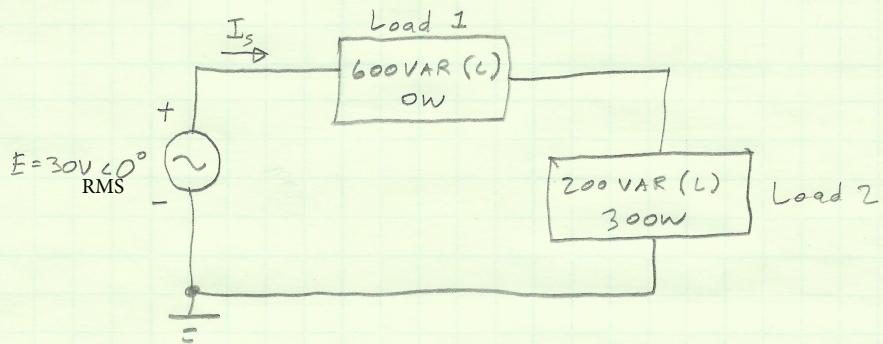

a) Find P_T , Q_T , S_T , and F_p

$$P_T = 0W + 300W = \boxed{300W}$$

$$Q_T = 600 \text{ VAR (c)} + 200 \text{ VAR (L)} = \boxed{400 \text{ VAR (c)}}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \boxed{500 \text{ VA}}$$

$$F_p = \frac{P_T}{S_T} = \frac{300 \text{ W}}{500 \text{ VA}} = \boxed{0.6 \text{ leading}}$$


b) Find I_s

$$E \cdot I_s \cdot F_p = P_T \quad |I_s| = \frac{P_T}{E \cdot F_p} = \frac{300 \text{ W}}{(30 \text{ V}) (0.6)} = 16.7 \text{ A}$$

$$\theta_I = \theta_E + \cos^{-1}(F_p) = 0^\circ + \cos^{-1}(0.6) = 53.1^\circ$$

$$I_s = \boxed{16.7 \text{ A} < 53.1^\circ \text{ RMS}}$$

c) Draw the power triangle

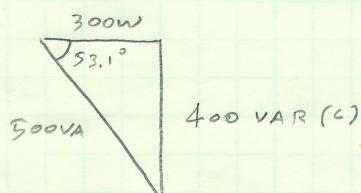

d) Find the types of elements and their impedance within each load

Load 1

$$600 \text{ VAR} (C) \rightarrow \frac{1}{\square}$$

$$Z_C = \frac{Q}{I_s^2} = \frac{600 \text{ VAR}}{(16.67 A)^2_{\text{RMS}}} = \boxed{2.16 \Omega \angle -90^\circ}$$

Load 2

$$200 \text{ VAR} (L) \rightarrow \square$$

$$300 \text{ W} \rightarrow \square$$

$$Z_L = \frac{Q}{I_s^2} = \frac{200 \text{ VAR}}{(16.67 A)^2_{\text{RMS}}} = \boxed{0.7197 \Omega \angle 90^\circ}$$

$$R = \frac{P}{I_s^2} = \frac{300 \text{ W}}{(16.67 A)^2_{\text{RMS}}} = \boxed{1.079 \Omega \angle 0^\circ}$$

e) Verify that the result of part b is correct by calculating I_s using only E and the values from part d.

$$Z_T = (2.16 \Omega \angle -90^\circ) + (0.7197 \Omega \angle 90^\circ) + (1.079 \Omega \angle 0^\circ) = (1.8 \Omega \angle -53.2^\circ)$$

$$I_s = \frac{E}{Z_T} = \frac{(30 V_{\text{RMS}} \angle 0^\circ)}{(1.8 \Omega \angle -53.2^\circ)} = \boxed{(16.67 A \angle 53.2^\circ)_{\text{RMS}}}$$

(19) The load on a 120V, 60Hz supply is 5kW (resistive), 8kVAR (inductive), and 2kVAR (capacitive).

a) Find S_T

$$Q_T = 8 \text{ kVAR (L)} + 2 \text{ kVAR (C)} = 6 \text{ kVAR (L)}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \sqrt{(5 \text{ kW})^2 + (6 \text{ kVAR})^2} = \boxed{7.81 \text{ kVA}}$$

b) Find F_p

$$F_p = \frac{P_T}{S_T} = \frac{5 \text{ kW}}{7.81 \text{ kVA}} = \boxed{0.64 \text{ lagging}}$$

c) Find I_T

$$|I_T| = \frac{P_T}{E \cdot F_p} = \frac{5 \text{ kW}}{(120 \text{ V})_{\text{RMS}} (0.64)} = 65 \text{ A}$$

$$\theta_I = \theta_E - \cos^{-1}(F_p) = 0^\circ - \cos^{-1}(0.64) = 50.2^\circ$$

$$\boxed{I_T = (65 \text{ A})_{\text{RMS}} \angle -50.2^\circ}$$

d. $X_C = \frac{1}{2\pi f C}, Q_C = I^2 X_C = \frac{E^2}{X_C} = \frac{(120 \text{ V})_{\text{RMS}}^2}{X_C}$

and $X_C = \frac{(120 \text{ V})_{\text{RMS}}^2}{Q_C} = \frac{14,400}{6000} = 2.4 \Omega$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{(2\pi)(60 \text{ Hz})(2.4 \Omega)} = \boxed{1105 \mu\text{F}}$$

e) Calculate I_T^* at unity power factor

$$S_T^* = \sqrt{P_T^2 + 0} = 5 \text{ kVA}$$

$$I_T^* = \frac{S_T^*}{E} = \frac{5 \text{ kVA}}{120 \text{ V}} = \boxed{41.67 \text{ A}}_{\text{RMS}}$$

21-1 Find the resonant ω_s and f_s for the series circuit with the following parameters:

a) $R = 10\Omega$ $L = 1H$ $C = 16\mu F$

$$\omega_s = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{1H \cdot 16\mu F}} = \boxed{250 \text{ rad/s}}$$

$$f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{1H \cdot 16\mu F}} = \boxed{39.789 \text{ Hz}}$$

b) $R = 300\Omega$ $L = 0.51H$ $C = 0.16\mu F$

$$\omega_s = \frac{1}{\sqrt{0.51H \cdot 0.16\mu F}} = \boxed{3501 \text{ rad/s}}$$


$$f_s = \frac{1}{2\pi\sqrt{0.51H \cdot 0.16\mu F}} = \boxed{557.154 \text{ Hz}}$$

c) $R = 20\Omega$ $L = 27mH$ $C = 7.5\mu F$

$$\omega_s = \frac{1}{\sqrt{270H \cdot 7.5\mu F}} = \boxed{22.222 \text{ rad/s}}$$

$$f_s = \frac{1}{2\pi\sqrt{270H \cdot 7.5\mu F}} = \boxed{3.537 \text{ Hz}}$$

③ For the circuit:

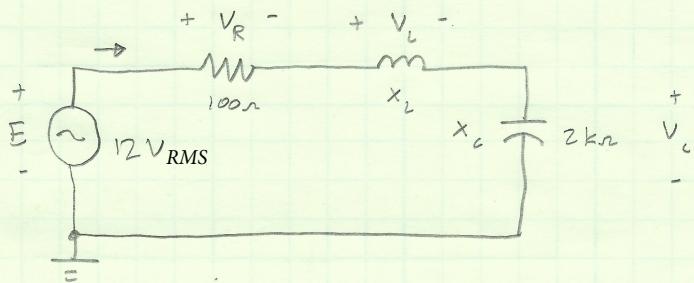

a) Find the value of X_L for resonance

$$X_L = 2\text{k}\Omega \angle 90^\circ$$

b) Calculate I at resonance

$$Z_T = (100\Omega \angle 0^\circ) + (2\text{k}\Omega \angle 90^\circ) + (2\text{k}\Omega \angle -90^\circ) = 100\Omega \angle 0^\circ$$

$$I = \frac{E}{Z_T} = \frac{12\text{ V}_{\text{RMS}} \angle 0^\circ}{100\Omega \angle 0^\circ} = 120\text{ mA}_{\text{RMS}} \angle 0^\circ$$

c) Calculate V_R , V_L , V_C at resonance

$$V_R = Z_R \cdot I = (100\Omega \angle 0^\circ)(120\text{ mA} \angle 0^\circ) = 12\text{ V}_{\text{RMS}} \angle 0^\circ$$

$$V_L = Z_L \cdot I = (2\text{k}\Omega \angle 90^\circ)(120\text{ mA} \angle 0^\circ) = 240\text{ V}_{\text{RMS}} \angle 90^\circ$$

$$V_C = Z_C \cdot I = (2\text{k}\Omega \angle -90^\circ)(120\text{ mA} \angle 0^\circ) = 240\text{ V}_{\text{RMS}} \angle -90^\circ$$

d) Determine the Q-factor of the circuit

$$Q = \frac{X_L}{R} = \frac{2\text{k}\Omega}{100\Omega} = 20$$

e) If the frequency is 5 kHz, determine the values of L and C

$$\omega = 2\pi f = 2\pi(5 \text{ kHz}) = 31.42 \frac{\text{kr}}{\text{s}}$$

$$X_L = 2\text{k}\Omega = \omega L \quad L = \frac{X_L}{\omega} = \frac{2 \text{ k}\Omega}{31.42 \frac{\text{kr}}{\text{s}}} = \boxed{63.7 \text{ mH}}$$

$$X_C = \frac{1}{\omega C} \quad C = \frac{1}{\omega X_C} = \frac{1}{(2 \text{ k}\Omega)(31.42 \frac{\text{kr}}{\text{s}})} = \boxed{15.9 \text{ nF}}$$

f) Find the bandwidth of the response if the resonant frequency is 5 kHz

$$BW = \frac{f_R}{Q} = \frac{5 \text{ kHz}}{20} = \boxed{250 \text{ Hz}}$$

g) What are the low and high cut-off frequencies?

$$f_L, f_H = f_R \pm \frac{BW}{2} = 5 \text{ kHz} \pm 125 \text{ Hz} = \boxed{4.875 \text{ kHz}, 5.125 \text{ kHz}}$$