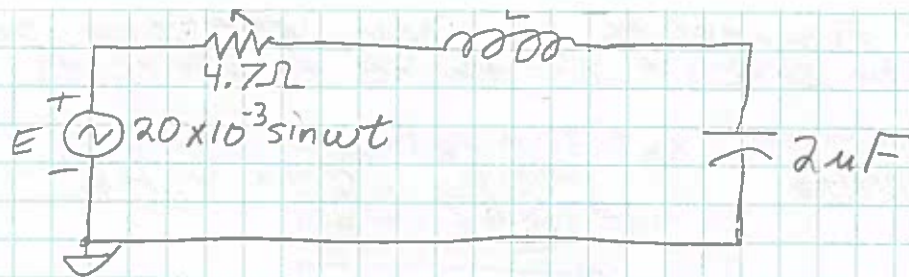


21-4



- a) Find the value of  $L$  in millihenries if the resonant frequency is  $1800 \text{ Hz}$ .

$$f_s = \frac{1}{2\pi\sqrt{LC}} \Rightarrow L = \frac{1}{(2\pi f_s)^2 \cdot C} = \frac{1}{2\pi \cdot 1.8 \text{ kHz} \cdot 2 \mu\text{F}} = \boxed{3.91 \text{ mH}}$$

- b) Calculate and compare  $X_C + X_L$

$$X_C = \frac{1}{2\pi \cdot 1.8 \text{ kHz} \cdot 2 \mu\text{F}} = \boxed{44.2 \Omega}$$

$$X_L = 2\pi \cdot 1.8 \text{ kHz} \cdot 3.91 \text{ mH} = \boxed{44.2 \Omega} \quad \text{Same}$$

- c)  $E_{\text{RMS}} = 0.707 \cdot 20 \times 10^{-3} \text{ V} = 14.14 \text{ mV}_{\text{RMS}} \angle 0^\circ$

$$I_{\text{RMS}} = \frac{14.14 \text{ mV}_{\text{RMS}} \angle 0^\circ}{4.7 \Omega + j44.2 - j44.2} = \boxed{3.009 \text{ mA}_{\text{RMS}} \angle 0^\circ}$$

- d) Find the power dissipated by the circuit at resonance

$$P = I^2 R = (3.009 \text{ mA})^2 \cdot 4.7 \Omega = \boxed{42.54 \mu\text{W}}$$

- e) What is the apparent power delivered to the system at resonance?

$$S_T = P_T = \boxed{42.54 \mu\text{VA}}$$

- f) What is the power factor of the circuit at resonance?

$$F_p = \frac{P_T}{S_T} = \frac{42.54 \mu\text{W}}{42.54 \mu\text{VA}} = \boxed{1}$$

- g) Calculate the  $Q$  of the circuit and the resulting bandwidth

$$Q = \frac{X_L}{R} = \frac{44.2 \Omega}{4.7 \Omega} = \boxed{9.4} \quad \text{BW} = \frac{f_s}{Q_s} = \frac{1800 \text{ Hz}}{9.4} = \boxed{191.49 \text{ Hz}}$$



h) Find the cutoff frequencies, and calculate the power dissipated by the circuit at these frequencies

$$\begin{aligned}f_1 &= f_s - \frac{1}{2} BW \\&= 1800 \text{ Hz} - 0.5 \cdot 191.49 \text{ Hz} \\&= 1.7 \text{ kHz}\end{aligned}$$

$$\begin{aligned}f_2 &= f_s + \frac{1}{2} BW \\&= 1800 \text{ Hz} + 0.5 \cdot 191.49 \text{ Hz} \\&= 1.896 \text{ kHz}\end{aligned}$$

$$P_{HPF} = \frac{1}{2} P_{MAX} = \frac{1}{2} \cdot 42.54 \mu W = 21.27 \mu W$$



- ⑤ a) Find the bandwidth of a series resonant circuit having a resonant frequency of 6000 Hz and a  $Q_s$  of 15.

$$BW = \frac{f_r}{Q_s} = \frac{6000}{15} = \boxed{400 \text{ Hz}}$$

- b) Find the cutoff frequencies

$$f_1 = f_r - \frac{BW}{2} = 6000 \text{ Hz} - \frac{400 \text{ Hz}}{2} = \boxed{5800 \text{ Hz}}$$

$$f_2 = f_r + \frac{BW}{2} = 6000 \text{ Hz} + \frac{400 \text{ Hz}}{2} = \boxed{6200 \text{ Hz}}$$

- c) If the resistance of the circuit at resonance is  $3 \Omega$ , what are the values of  $X_L$  and  $X_C$  in ohms?

$$Q_s = \frac{X_L}{R} \rightarrow X_L = Q_s R = (15)(3 \Omega) = \boxed{45 \Omega}$$

$$X_L = X_C \text{ @ } f = f_r, \text{ so } X_C = \boxed{45 \Omega}$$

- d) What is the power dissipated at the half-power frequencies if the maximum current flowing through the circuit is 0.5 A?


\* assumed to  
mean  $0.5 A_p$

$$P_{\max} = I^2 R = (0.5 A_p)^2 (3 \Omega) = 750 \text{ mW}$$

$$P_{\text{HPF}} = \frac{1}{2} P_{\max} = \frac{1}{2} (750 \text{ mW}) = \boxed{375 \text{ mW}}$$



P21.9

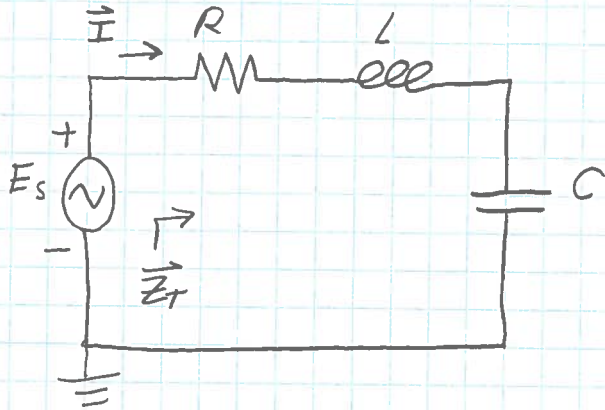

$$\vec{E}_s = 5V_{pk} \angle 0^\circ$$

$$I_{PEAK} = 500\text{mA} (@ f_s)$$

$$BW = 120\text{Hz}$$

$$f_s = 8400\text{Hz}$$

FIND

(a)  $R, L, C$

$$I_{PEAK} = \frac{E_s}{R} = \frac{5V_{pk} \angle 0^\circ}{R} = 500\text{mA}$$

$$\therefore R = \frac{5V_{pk} \angle 0^\circ}{500\text{mA}_{pk}} = \boxed{10\Omega}$$

$$BW = \frac{f_s}{Q_s} \quad \therefore Q_s = \frac{f_s}{BW} = \frac{8400\text{Hz}}{120\text{Hz}}$$

$$\underline{Q_s = 70}$$

$$\text{But } Q_s = \frac{X_L}{R}$$

$$\therefore X_L = (Q_s)(R) = (70)(10\Omega) = \underline{700\Omega}$$

$$X_L = 2\pi fL$$

$$\therefore L = \frac{X_L}{2\pi f} = \frac{700\Omega}{(2\pi)(8400\text{Hz})}$$

$$\boxed{L = 13.3\text{mH}}$$

$$X_C = \frac{1}{2\pi fC}$$

$$\therefore C = \frac{1}{2\pi fX_C} = \frac{1}{(2\pi)(8400\text{Hz})(700\Omega)}$$

$$\boxed{C = 27.1\text{nF}}$$

(b)  $f_1, f_2$ 

$$f_2 = \frac{1}{2\pi} \left[ \frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right]$$

$$f_2 = 8.44 \text{ kHz}$$

$$f_1 = \frac{1}{2\pi} \left[ -\frac{R}{2L} + \frac{1}{2} \sqrt{\left(\frac{R}{L}\right)^2 + \frac{4}{LC}} \right]$$

$$f_1 = 8.32 \text{ kHz}$$

OR


$$f_2 = f_s + \frac{BW}{2} = 8400 \text{ Hz} + \frac{120 \text{ Hz}}{2}$$

$$f_2 = 8.46 \text{ kHz}$$

$$+ \quad f_1 = f_s - \frac{BW}{2} = 8400 \text{ Hz} - \frac{120 \text{ Hz}}{2}$$

$$f_1 = 8.34 \text{ kHz}$$

**Problem 21-14.** For the parallel resonant network in Fig. 21.55:

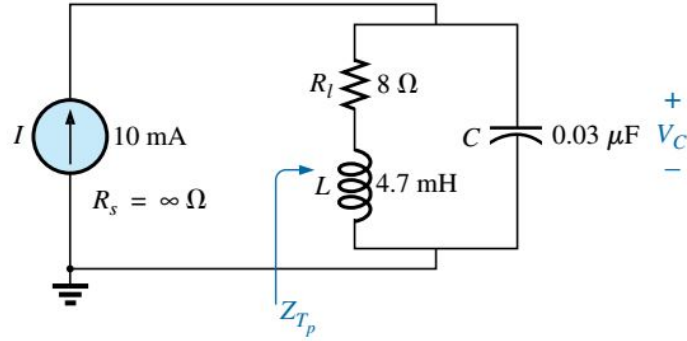

**FIG. 21.55**

*Problem 14.*

(a) Calculate  $f_s$ .

$$f_s = \frac{1}{2 \cdot \pi \cdot \sqrt{LC}}$$

$$= \boxed{13.4 \text{ kHz}}$$

(b) Determine  $Q_l$  using  $f = f_s$ . Can the approximate approach be applied?

$$Q_l = \frac{X_L}{R_l}$$

$$= \frac{2 \cdot \pi \cdot f_s \cdot L}{R_l} = \frac{2 \cdot \pi \cdot 13.4 \text{ kHz} \cdot 4.7 \cdot 10^{-3}}{8}$$

$$= \boxed{49.5}$$

(c) Determine  $f_p$  and  $f_m$  Given that  $Q_l > 10$ ,

$$f_p = f_s = f_m = \boxed{13.4 \text{ kHz}}$$

(d) Calculate  $X_L$  and  $X_C$  using  $f_p$ . How do they compare?

$$X_L = 2 \cdot \pi \cdot f_s \cdot L$$

$$= 2 \cdot \pi \cdot 13.4 \text{ kHz} \cdot 4.7 \cdot 10^{-3}$$

$$= \boxed{398.8 \Omega}$$

$$X_C = \frac{1}{2 \cdot \pi \cdot f_s \cdot C}$$

$$= \frac{1}{2 \cdot \pi \cdot 13.4 \text{ kHz} \cdot 0.03 \cdot 10^{-6}}$$

$$= \boxed{398.8 \Omega}$$

$X_L$  is equal to  $X_C$

(e) Find the total impedance at resonance ( $f_p$ ).

$$Z_{T_P} = R_S || Q_l^2 R_l$$

where:  $R_S = \infty \Omega$ . Therefore

$$\begin{aligned} Z_{T_P} &= Q_l^2 \cdot R_l \\ &= 49.5^2 \cdot 8 \Omega \\ &= \boxed{19.58 \text{ k}\Omega} \end{aligned}$$

(f) Calculate  $V_C$  at resonance ( $f_p$ ).

$$\begin{aligned} V_C &= I \cdot Z_{T_P} \\ &= 10 \text{ mA} \cdot 19.58 \text{ k}\Omega \\ &= \boxed{195.8 \text{ V}} \end{aligned}$$

(g) Determine  $Q_p$  and the BW using


$$\begin{aligned} Q_p &= \frac{Z_{T_P}}{X_L} = \frac{Z_{T_P}}{X_C} \\ &= \frac{19.58 \text{ k}\Omega}{398.8 \Omega} \\ &= \boxed{49.48} \end{aligned}$$

$$\begin{aligned} BW &= \frac{f_p}{Q_p} = \frac{f_s}{Q_p} \\ &= \frac{f_p}{Q_p} = \frac{13.4 \text{ kHz}}{49.48} \\ &= \boxed{270.9 \text{ Hz}} \end{aligned}$$

(h) Calculate  $I_L$  and  $I_C$  at  $f_p$ .

$$\begin{aligned} I_L &= I_C = Q_l \cdot I_T \\ I_L &= 49.5 \cdot 10 \text{ mA} \\ I_L &= \boxed{494.8 \text{ mA}} \end{aligned}$$

**Problem 21-18. For the network in Fig. 21.59:**

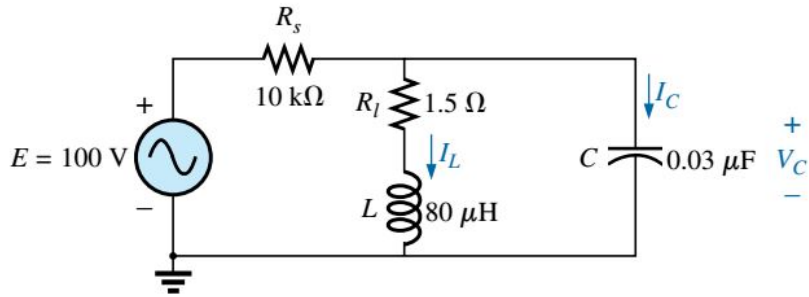

**FIG. 21.59**  
Problem 18.

- (a) Find the resonant frequencies  $f_s$ ,  $f_p$  and  $f_m$ . What do the results suggest about the  $Q_p$  of the network?

$$\begin{aligned} f_s &= \frac{1}{2 \cdot \pi \cdot \sqrt{LC}} \\ &= \frac{1}{2 \cdot \pi \cdot \sqrt{(80 \mu\text{H})(0.03 \mu\text{F})}} \\ &= \boxed{102.73 \text{ kHz}} \end{aligned}$$

$$\begin{aligned} f_p &= f_s \sqrt{1 - \frac{R_l^2 C}{L}} \\ &= 102.7 \text{ kHz} \sqrt{1 - \frac{1.5^2 (0.03 \mu\text{F})}{(80 \mu\text{H})}} \\ &= \boxed{102.71 \text{ kHz}} \end{aligned}$$

$$\begin{aligned} f_m &= f_s \sqrt{1 - \frac{1}{4} \left[ \frac{R_l^2 C}{L} \right]} \\ &= 102.7 \text{ kHz} \sqrt{1 - \frac{1}{4} \left[ \frac{1.5^2 (0.03 \mu\text{F})}{(80 \mu\text{H})} \right]} \\ &= \boxed{102.73 \text{ kHz}} \end{aligned}$$

Given that  $f_s \approx f_p \approx f_m$ ,  $Q_l$  of the network is greater than or equal to 10.

- (b) Find the values of  $X_L$  and  $X_C$  at resonance ( $f_p$ ). How do they compare?

$$\begin{aligned} X_L &= 2 \cdot \pi \cdot f_s \cdot L \\ &= 2 \cdot \pi \cdot 102.73 \text{ kHz} \cdot 80 \cdot 10^{-6} \\ &= \boxed{51.64 \Omega} \end{aligned}$$



$$\begin{aligned}
X_C &= \frac{1}{2 \cdot \pi \cdot f_s \cdot C} \\
&= \frac{1}{2 \cdot \pi \cdot 102.73 \text{ kHz} \cdot 0.03 \cdot 10^{-6}} \\
&= \boxed{51.64 \Omega}
\end{aligned}$$

$$X_L \approx X_C \text{ at resonance } (f_p)$$

(c) Find the impedance  $Z_{TP}$  at resonance ( $f_p$ ).

$$\begin{aligned}
Z_{TP} &= R_s \parallel Q_l^2 \cdot R_l \\
&= 10 \text{ k}\Omega \parallel 34.4^2 \cdot 1.5 \Omega \\
&= \frac{10 \text{ k}\Omega \cdot [34.4^2 \cdot 1.5 \Omega]}{10 \text{ k}\Omega + [34.4^2 \cdot 1.5 \Omega]} \\
&= \boxed{1.51 \text{ k}\Omega}
\end{aligned}$$

where

$$\begin{aligned}
Q_l &= \frac{X_L}{R_l} = \frac{51.64 \Omega}{1.5 \Omega} \\
&= \boxed{34.4}
\end{aligned}$$

(d) Calculate  $Q_P$  and the BW.

$$\begin{aligned}
Q_p &= \frac{Z_{TP}}{X_L} = \frac{Z_{TP}}{X_C} \\
&= \frac{1.51 \text{ k}\Omega}{51.64 \Omega} \\
&= \boxed{29.2}
\end{aligned}$$

$$\begin{aligned}
BW &= \frac{f_p}{Q_p} = \frac{f_s}{Q_p} \\
&= \frac{f_p}{Q_p} = \frac{102.73 \text{ kHz}}{29.2} \\
&= \boxed{3.52 \text{ kHz}}
\end{aligned}$$

(e) Find the magnitude of current  $I_L$  and  $I_C$  at resonance ( $f_p$ ).

Use source conversion to convert the voltage source "E" to current source "I"

$$\begin{aligned}
I &= \frac{E}{R_s} = \frac{100}{10 \text{ k}\Omega} \\
&= 10 \text{ mA}
\end{aligned}$$

And the parallel resistance  $R_s = R_p = 10 \text{ k}\Omega$ . Using current divider

$$\begin{aligned}
I_T &= I \cdot \frac{R_s}{R_s + Q_l^2 \cdot R_l} \\
&= 10 \text{ mA} \cdot \frac{10 \text{ k}\Omega}{10 \text{ k}\Omega + 34.4^2 \cdot 1.5} \\
&= 8.49 \text{ mA}
\end{aligned}$$

$$\begin{aligned}
I_L = I_C &= Q_L \cdot I_T \\
&= 34.4 \cdot 8.49 \text{ mA} \\
&= \boxed{292.3 \text{ mA}}
\end{aligned}$$

(f) Calculate the voltage  $V_C$  at resonance ( $f_p$ )

$$\begin{aligned}
V_C &= I_C \cdot Z_{T_p} \\
&= 292.3 \text{ mA} \cdot 1.51 \text{ k}\Omega \\
&= \boxed{15.1 \text{ V}}
\end{aligned}$$


26) Design the network below to have the following characteristics:

$$BW = 500 \text{ Hz}$$

$$Q_p = 30$$

$$V_{C_{\max}} = 1.8 \text{ V}$$

\* Voltages and currents are in peak \*

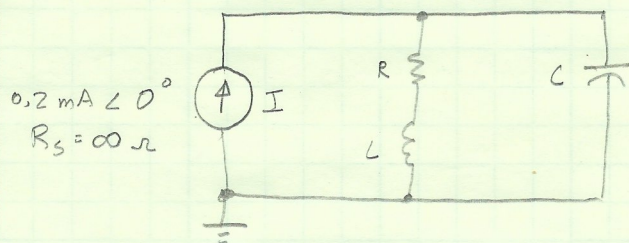

$$Z_{Tp} = \frac{V_{C_{\max}}}{I} = \frac{1.8 \text{ V}}{0.2 \text{ mA}} = 9 \text{ k}\Omega$$

$$Q_p = \frac{R}{X_L} = \frac{R_p}{X_L} \rightarrow X_L = \frac{R_p}{Q_p} = \frac{Z_{Tp}}{Q_p} = \frac{9 \text{ k}\Omega}{30} = 300 \Omega = X_L$$

$$BW = \frac{f_p}{Q_p} \rightarrow f_p = (BW)(Q_p) = (500 \text{ Hz})(30) = \boxed{15 \text{ kHz}}$$

$$L = \frac{X_L}{2\pi f} = \frac{300 \Omega}{2\pi (15 \text{ kHz})} = \boxed{3.18 \text{ mH}}$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi (15 \text{ kHz}) (300 \Omega)} = \boxed{35.37 \text{ nF}}$$

$$Q_p = \frac{X_L}{R_L} \rightarrow R_L = \frac{X_L}{Q_p} = \frac{300 \Omega}{30} = \boxed{10 \Omega}$$



## Problem 21-28.

Verify the results in Example 21.8. That is, show that the resonant frequency is 40 kHz, the cutoff frequencies are as calculated, and the bandwidth is 1.85 kHz.

The circuit simulated in Multisim, the resulting magnitude and phase response curves are shown below. The resonant frequency from Multisim is in agreement with the resonant frequency from Example 21.8 in the text. Where


$$f_{p_{Multisim}} = 40.01 \text{ kHz}$$

$$f_{p_{Text}} = 40.01 \text{ kHz}$$

Similarly the bandwidth from Multisim is in agreement with the bandwidth from the text. Where



$$BW_{Multisim} = 40.94 \text{ kHz} - 39.11 \text{ kHz} = 1.83 \text{ kHz}$$

$$BW_{Text} = 1.85 \text{ kHz}$$

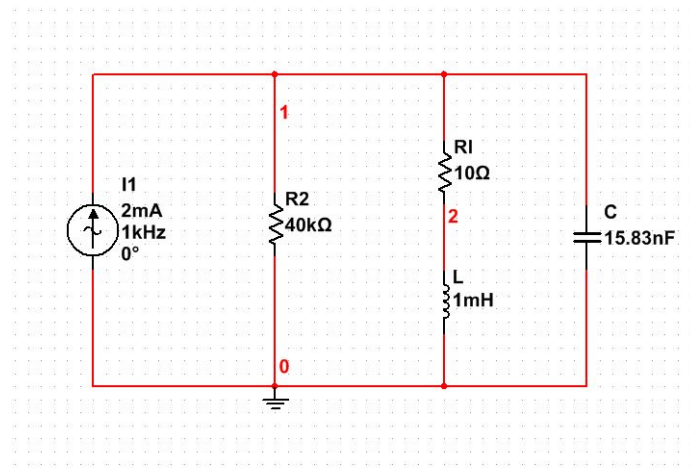
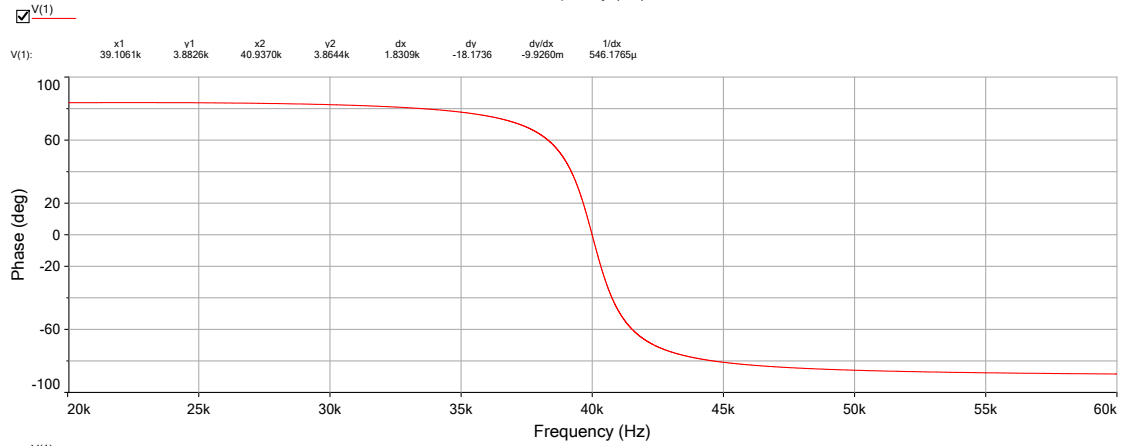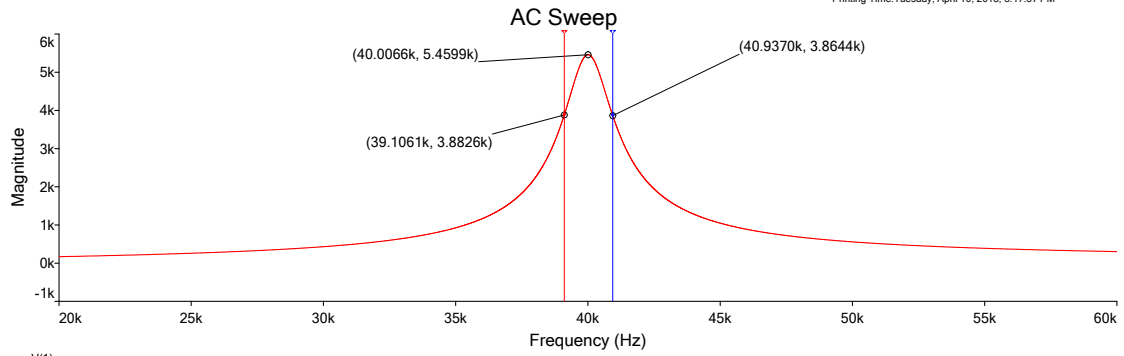
# Problem 21-28

Printing Time: Tuesday, April 10, 2018, 3:17:57 PM



22-5 Given  $N = \log_{10} X$ , determine  $X$  for each value of  $N$ .

$$X = 10^N$$

a)  $N = 3$       $x = 1000$

b)  $N = 12$       $x = 10^{12}$

c)  $N = 0.2$       $x = 1.585$

d)  $N = 0.04$       $x = 1.096$

e)  $N = 10$       $x = 10^{10}$

f)  $N = 3.18$       $x = 1.51 \times 10^3$

g)  $N = 1.001$       $x = 10.023$

h)  $N = 6.1$       $x = 1.259 \times 10^6$



⑧ Find  $\log_{10}(3)^3$  and compare with  $3 \log_{10} 3$ .

Assumption:  $\log_{10}(3)^3 = \log_{10}(3^3)$  and  $\log_{10}(3)^3 \neq [\log_{10}(3)]^3$

$$\log_{10}(3^3) = \log_{10}(27) = \boxed{1.43}$$

$$3 \log_{10} 3 = 3(0.4771) = \boxed{1.43}$$

$\therefore$  They are equal, as expected.

**Problem 22-10.**

A power level of 100 W is 6 dB above what power level?

$$\begin{aligned}dB &= 10 \cdot \log \frac{P_o}{P_i} \\6 \text{ dB} &= 10 \cdot \log \frac{100 \text{ W}}{P_i} \\\frac{6}{10} &= \log \frac{100 \text{ W}}{P_i} \\10^{\frac{6}{10}} &= \frac{100 \text{ W}}{P_i} \\P_i &= \frac{100 \text{ W}}{10^{\frac{6}{10}}} \\&= \boxed{25.12 \text{ mW}}\end{aligned}$$



⑫ Determine the  $\text{dB}_m$  level for an output power of  $120\text{mW}$ .

$$10 \log_{10} \left( \frac{120\text{mW}}{1\text{mW}} \right) = \boxed{20.8 \text{ dB}_m}$$



**Problem 22-13.**

Find the  $dB_v$  gain of an amplifier that raises the voltage level from 0.1 mV to 8.4 mV.

$$\begin{aligned} dB_v &= 20 \cdot \frac{8.4 \text{ mV}}{0.1 \text{ mV}} \\ &= 20 \cdot 84 \\ &= 20 \cdot 1.92 \\ &= \boxed{38.49} \end{aligned}$$

**Problem 22-14.**

Find the output voltage of an amplifier if the applied voltage is 20 mV and a  $dB_v$  gain of 22 dB is attained.

$$\begin{aligned}dB_v &= 20 \cdot \log \frac{V_o}{V_i} \\22 \text{ dB}_v &= 20 \cdot \log \frac{V_o}{20 \text{ mV}} \\ \frac{22}{20} &= \log \frac{V_o}{20 \text{ mV}} \\10^{\frac{22}{20}} &= \frac{V_o}{20 \text{ mV}} \\V_o &= 20 \text{ mV} \cdot 10^{\frac{22}{20}} \\&= \boxed{251.8 \text{ mV}}\end{aligned}$$