

FULL NAME (Printed):

\* SOLUTIONS \*

RIT Program:

Choose the one alternative that best completes the statement or answers the question. No partial credit will be awarded so choose carefully.

- 1) What is the total impedance,  $Z_T$  of a series network consisting of a  $5\ \Omega$  resistor, an inductor having  $10\ \Omega$  reactance, and a capacitor with  $15\ \Omega$  reactance?

A)  $(5 - j5)\ \Omega$ B)  $(5 - j25)\ \Omega$ C)  $(5 + j25)\ \Omega$ D)  $(5 + j5)\ \Omega$ 1) A

$$\vec{Z}_T = 5\ \Omega + j10\ \Omega - j15\ \Omega = \underline{(5 - j5)\ \Omega}$$

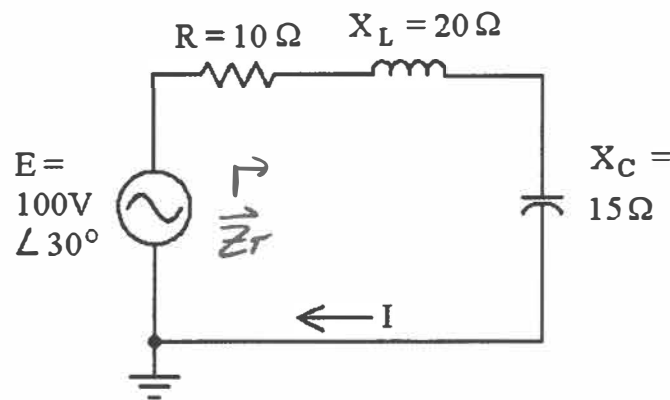


Figure 15.3

- 2) See Figure 15.3. The total impedance of this circuit may be made purely resistive by
- A) increasing  $R$  to  $35\ \Omega$ .  
 B) increasing  $R$  to  $5\ \Omega$ .  
 C) decreasing the signal frequency.  
 D) increasing the signal frequency.

2) C

$$\begin{aligned}\vec{Z}_T &= 10 + j20 - j15 \\ &= 10 + jX_L - jX_C \\ &= 10 + j\omega L - j\frac{1}{\omega C} \\ &\quad \text{IF } \omega \downarrow, X_L \downarrow, X_C \uparrow\end{aligned}$$

- 3) See Figure 15.3. What is  $Z_T$  (the total series circuit impedance) in polar form?

A)  $5\ \Omega \angle 10^\circ$ B)  $10\ \Omega \angle 5^\circ$ C)  $11.18\ \Omega \angle 26.6^\circ$ D)  $11.18\ \Omega \angle 63.43^\circ$ 3) C

$$\vec{Z}_T = (10 + j5)\ \Omega = \underline{11.18\ \Omega \angle 26.6^\circ}$$

4) What is the impedance,  $Z_T$  of a series R-C circuit made up of a  $56\text{ k}\Omega$  resistor and a  $0.033\text{ }\mu\text{F}$  capacitor at a signal frequency of  $450\text{ Hz}$ ?


4) D

A)  $10,730\text{ }\Omega\angle-90^\circ$


B)  $66,730\text{ }\Omega\angle10.8^\circ$

C)  $57,070\text{ }\Omega\angle-33^\circ$

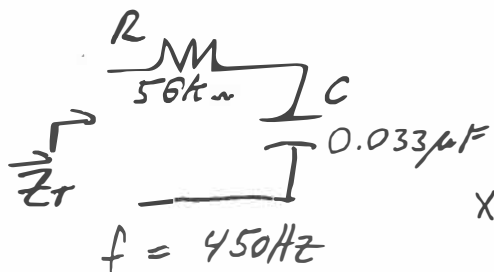D)  $57,016\text{ }\Omega\angle-10.8^\circ$


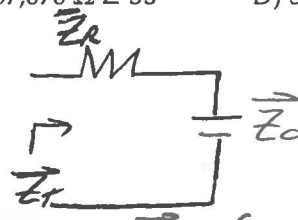
$$X_C = \frac{1}{2\pi fC} = 10,718\text{ }\Omega$$



$$\vec{Z}_T = (56,000 - j10,718)\text{ }\Omega$$

$$= 57,016\text{ }\Omega\angle-10.8^\circ$$

5) See Figure 15.4. Determine  $Z_T$  expressed in rectangular form.

5) B

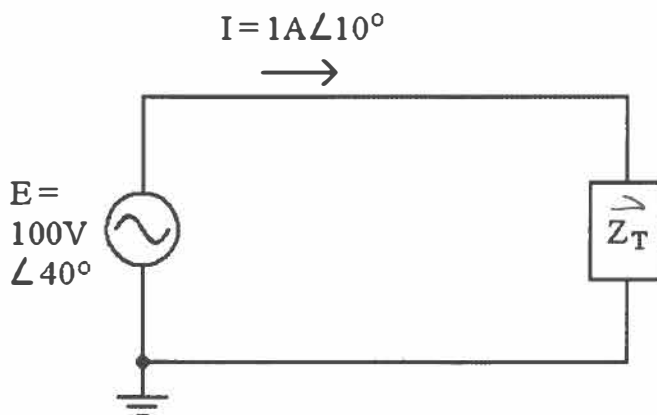


Figure 15.4

$$\vec{Z}_T = \frac{\vec{E}}{\vec{I}}$$

$$= \frac{100\text{ V}\angle40^\circ}{1\text{ A}\angle10^\circ}$$

$$\vec{Z}_T = 100\text{ }\Omega\angle30^\circ$$

$$\text{OR}$$

$$(86.6 + j50)\text{ }\Omega$$

A)  $(64.3 + j76.6)\text{ }\Omega$

B)  $(86.6 + j50)\text{ }\Omega$

C)  $(100 + j50)\text{ }\Omega$

D)  $(100 + j30)\text{ }\Omega$