

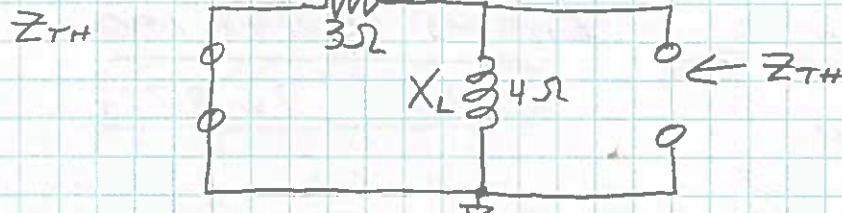


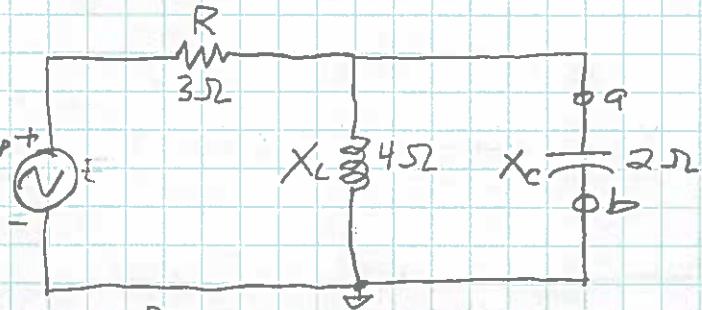19-15 Find the Thevenin equivalent circuit for the portion of the network below external to the elements between points a and b



$$Z_{TH} = 3\Omega \angle 0^\circ // 4\Omega \angle 90^\circ$$


$$= 2.4\Omega \angle 36.87^\circ$$

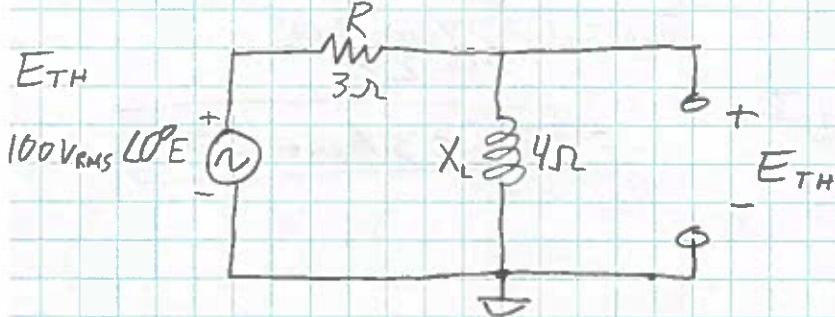


$$E_{TH} = 100 \text{ V RMS } \angle 0^\circ \left( \frac{4\Omega \angle 90^\circ}{3 + j4} \right)$$

$$= 80 \text{ V RMS } \angle 36.87^\circ$$

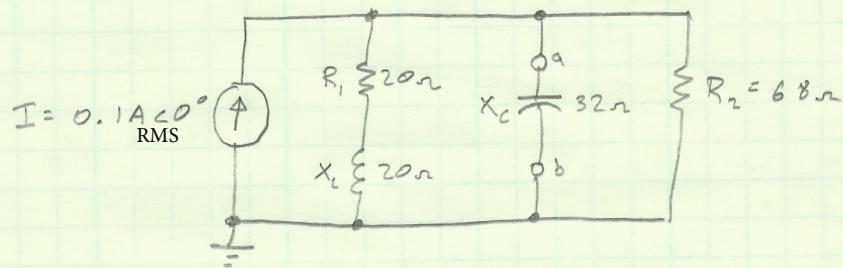
(17) Find the Thévenin equivalent circuit for the portion of the network below external to the points a, b:


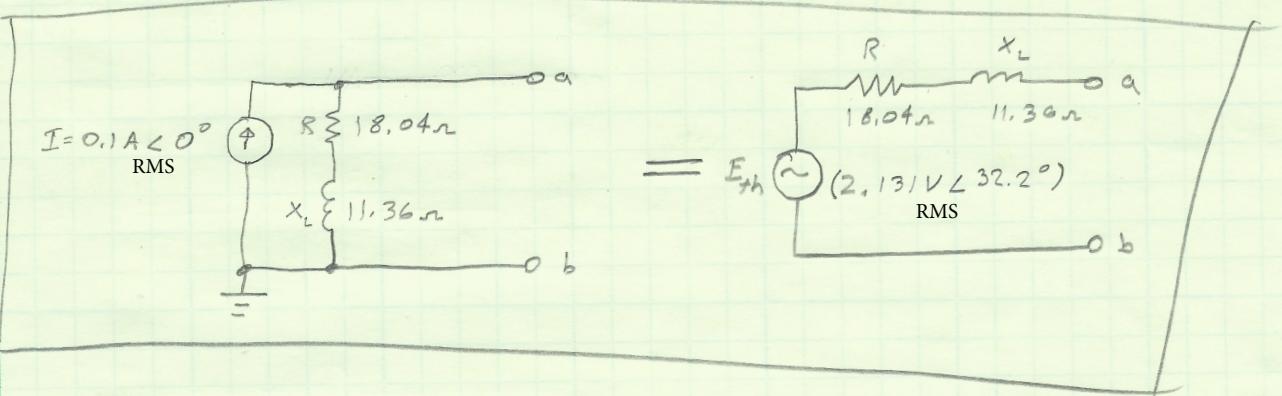
$$Z_T = R_2 \parallel (R_1 + X_L) = 68 \Omega \parallel (20 \Omega + j20 \Omega) = (18.04 + j11.36) \Omega$$



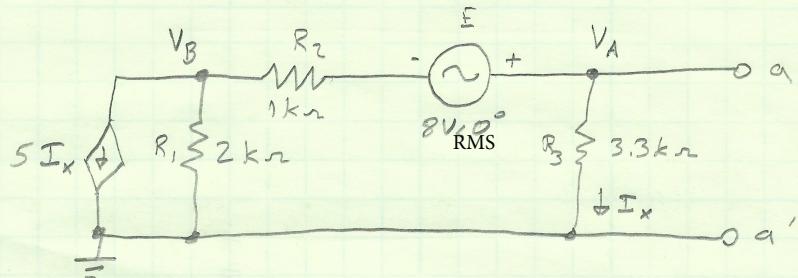(33) Find the Thévenin equivalent circuit equivalent to the network external to the points a-a':



$$I_x = \frac{V_A}{R_3}$$

Nodal

$$0 = 5 \frac{V_A}{R_3} + \frac{V_B}{R_1} + \frac{V_B + E - V_A}{R_2}$$


$$\textcircled{1} \quad -\frac{E}{R_2} = V_A \left[ \frac{5}{R_3} - \frac{1}{R_2} \right] + V_B \left[ \frac{1}{R_1} + \frac{1}{R_2} \right]$$

$$\frac{V_B + E - V_A}{R_2} = \frac{V_A}{R_3}$$


$$\textcircled{2} \quad \frac{E}{R_2} = V_A \left[ \frac{1}{R_3} + \frac{1}{R_2} \right] + V_B \left[ -\frac{1}{R_2} \right]$$

$$V_A = 1.62 V \angle 0^\circ = V_a \quad V_{a'} = 0 V$$

$$V_B = -5.89 V \angle 0^\circ$$

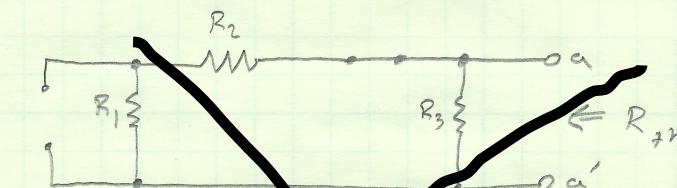

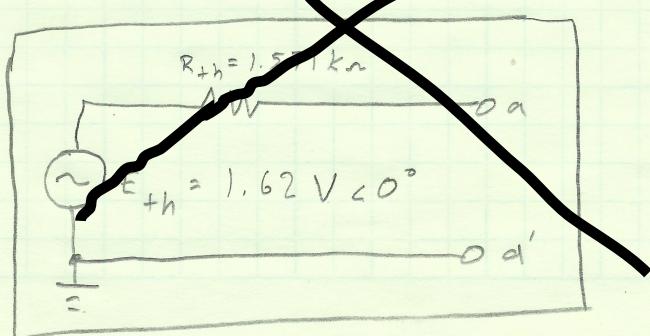
$$R_{th} = R_3 \parallel (R_1 + R_2) \\ = 1.571 k\Omega \angle 0^\circ$$



Must use an alternate method to find Zth since the dependent source is controlled in-network. Use a test source or the following:

33.  $E_{oc}$ :  
 $(E_{Th})$

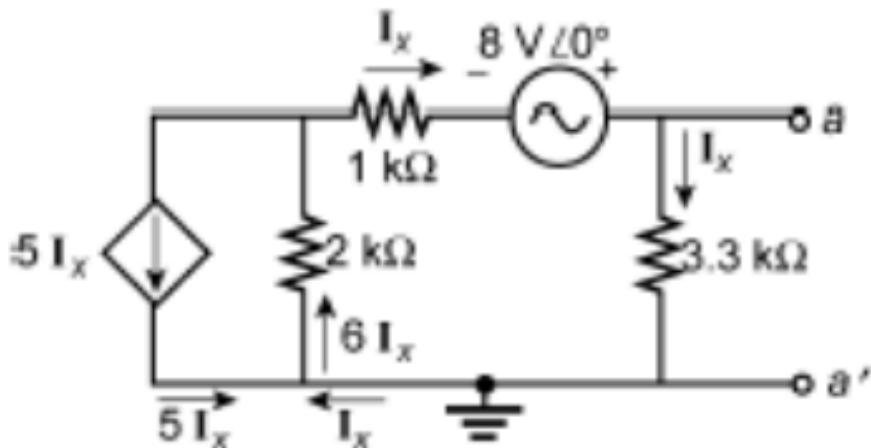


$$\text{KVL: } -6 I_x (2 \text{ k}\Omega) - I_x (1 \text{ k}\Omega) + 8 \text{ V} \angle 0^\circ - I_x (3.3 \text{ k}\Omega) = 0$$

$$I_x = \frac{8 \text{ V} \angle 0^\circ}{16.3 \text{ k}\Omega} = 0.491 \text{ mA} \angle 0^\circ$$


$$E_{oc} = E_{Th} = I_x (3.3 \text{ k}\Omega) = 1.62 \text{ V} \angle 0^\circ$$

$I_{sc}$ :


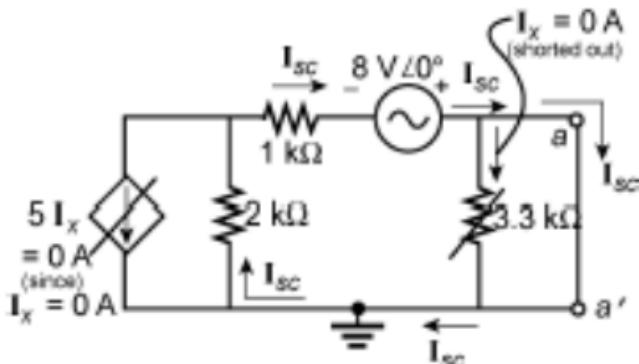


$$I_{sc} = \frac{8 \text{ V}}{3 \text{ k}\Omega} = 2.667 \text{ mA} \angle 0^\circ$$
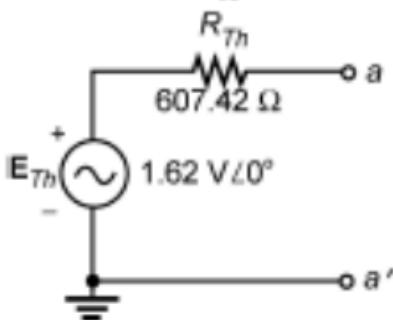
$$Z_{Th} = \frac{E_{oc}}{I_{sc}} = \frac{1.62 \text{ V} \angle 0^\circ}{2.667 \text{ mA} \angle 0^\circ} = 607.42 \text{ } \Omega \angle 0^\circ$$




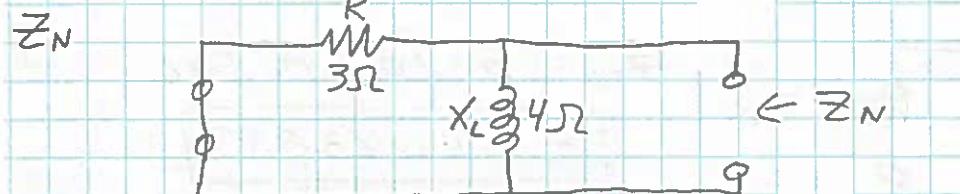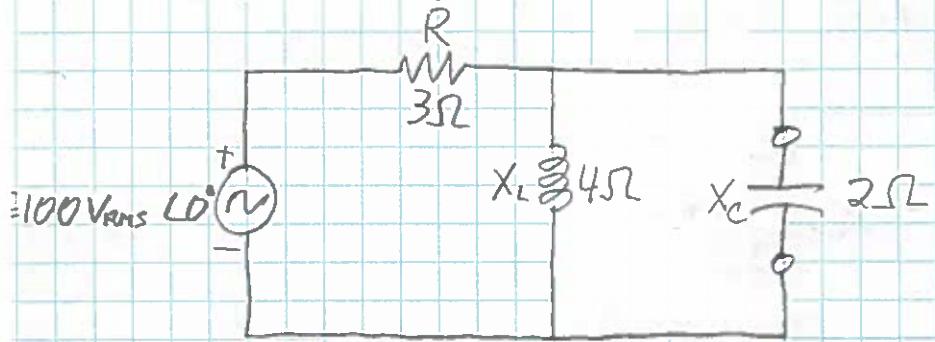19-34 Find the Norton equivalent circuit for the network external to the elements a and b.



$$Z_N = 3\Omega \angle 0^\circ // 4\Omega \angle 90^\circ$$


$$= 2.4\Omega \angle 36.87^\circ$$

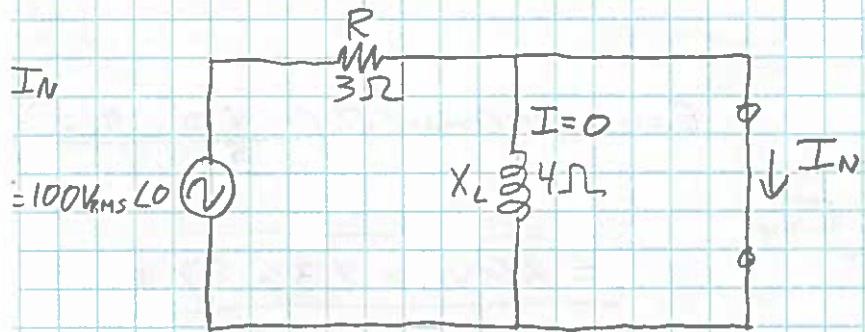

$$I_N = \frac{100 \text{V RMS } 60^\circ}{3\Omega \angle 0^\circ}$$

$$= 33.33 \text{ A RMS } 60^\circ$$

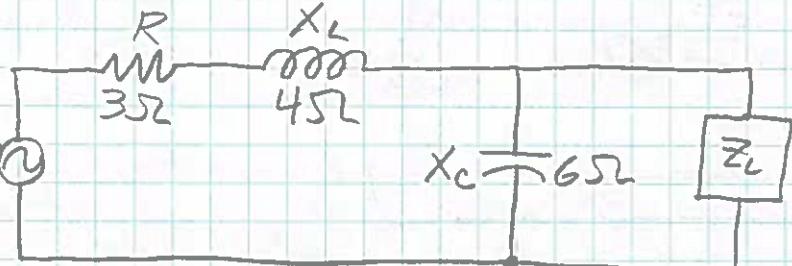19-48 Find the load impedance  $Z_L$  for the network for maximum power to the load, and find the maximum power to the load.



$$Z_{TH} = \frac{(3\Omega \angle 0^\circ + 4\Omega \angle 90^\circ) \parallel 6\Omega \angle -90^\circ}{(3\Omega \angle 0^\circ + 4\Omega \angle 90^\circ)} = 8.32 \Omega \angle -3.18^\circ$$


$$Z_L = 8.32 \angle 3.18^\circ$$

$$E_{TH} = 120V \angle 0^\circ \left( \frac{6\Omega \angle -90^\circ}{3\Omega \angle 0^\circ + j4 \Omega \angle 90^\circ} \right)$$

$$E_{TH} = 199.7V_{RMS} \angle -56.31^\circ$$

$$P_{max} = \frac{E_{TH}^2}{4R_{TH}} = \frac{(199.7V)^2}{4 \cdot 8.32 \Omega} = 1198W$$

④ For the system below:

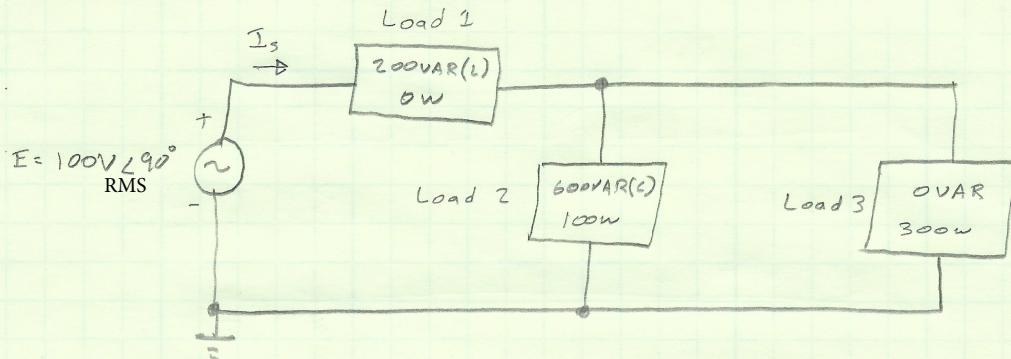

a) Determine total watts, total VAR, total VA, and  $F_p$


$$P_T = 100W + 300W = \boxed{400W}$$

$$Q_T = 200\text{VAR}(L) + 600\text{VAR}(C) = \boxed{400\text{VAR}(C)}$$

$$S_T = \sqrt{P_T^2 + Q_T^2} = \boxed{565.7 \text{ VA}}$$

$$F_p = \frac{P_T}{S_T} = \frac{400W}{565.7 \text{ VA}} = \boxed{0.707 \text{ (leading)}} \rightarrow 45^\circ$$

b) Draw the power triangle

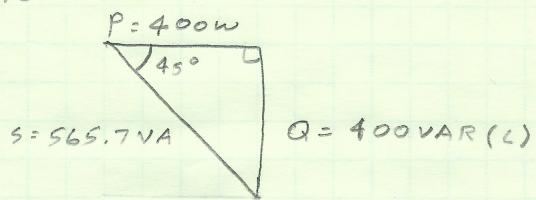

c) Find the current  $I_s$

$$P_T = E \cdot I_s \cdot F_p \quad |I_s| = \frac{P_T}{E \cdot F_p} = \frac{400W}{(100V)(0.707)} = 5.66A_{\text{RMS}}$$

$$\theta_I = \theta_E + \cos^{-1}(F_p) = 90^\circ + 45^\circ = 135^\circ$$

$$I_s = (5.66A \angle 135^\circ)_{\text{RMS}}$$