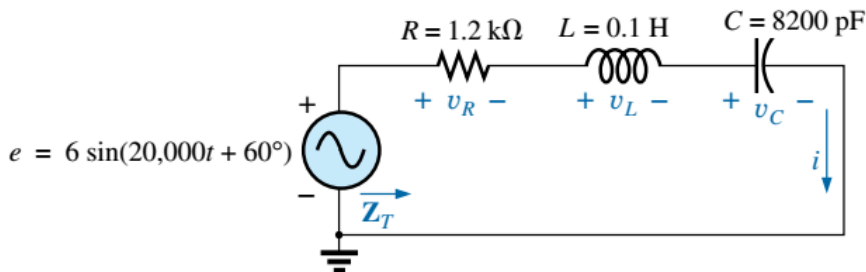


TEAM NAME (printed): _____ **SOLUTIONS** _____

Team members **PRESENT** (printed full names): _____

All 7 questions are equally weighted. Show your work and **BOX-IN** your final answer for credit.



For the circuit shown above, answer the following questions:

1. Determine Z_T

$$Z_T = R + jX_L - jX_C$$


$$Z_T = 1.2\text{K} + j 2.0\text{K} - j 6.1\text{K}$$

$$Z_T = 1.2\text{K} - j 4.1\text{K} \quad (\text{circuit is mostly capacitive})$$

$$Z_T = 4.27\text{K } \Omega < -73.7^\circ$$

$Z_T = 4.3\text{K } \Omega < -74^\circ$

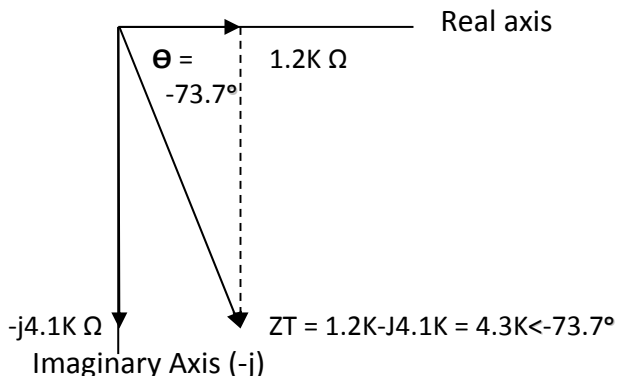2. Draw the impedance diagram (titled and labeled, angles shown)




3. Find the current I , in phasor form

$$E = 4.2\text{V}_{\text{rms}} < +60^\circ$$

$$I = E / Z_T = (4.2\text{V}_{\text{rms}} < +60^\circ) / (Z_T = 4.27\text{K} < -73.7^\circ) =$$

$1.0\text{mA}_{\text{rms}} < 134^\circ$

✓ ICE man

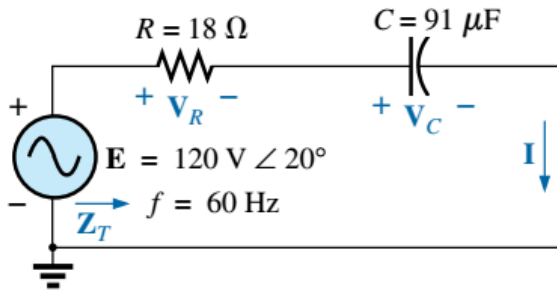

Note: $E = 120 \text{ V}_{\text{RMS}} \angle 20^\circ$

For the circuit shown above, answer the following questions:

4. Determine Z_T

$$Z_T = R - jX_C$$

$$Z_T = 18 \Omega - j29.1 \Omega$$

$$Z_T = 34.2 \Omega \angle -58.3^\circ$$

$$Z_T = 34 \Omega \angle -58^\circ$$

5. Find V_C in phasor form

$$\text{Need: } X_C = 1 / (2 \pi f C) = 29.1 \Omega \angle -90^\circ$$

Will use Vdivider to find V_C

$$V_C = V_S (-jX_C / Z_T) = (120 \text{ V}_{\text{rms}} \angle +20^\circ) / (29.1 \Omega \angle -90^\circ / 34.2 \Omega \angle -58.3^\circ)$$

$$V_C = (120 \text{ V}_{\text{rms}} \angle +20^\circ) / (0.85 \Omega \angle -32^\circ) = (102.1 \text{ V}_{\text{rms}} \angle -11.7^\circ)$$

$$102 \text{ V}_{\text{rms}} \angle -12^\circ$$

$$\text{Check KVL: } V_r = (120 \text{ V}_{\text{rms}} \angle +20^\circ) / (18 \Omega \angle 0^\circ / 34.2 \Omega \angle -58.3^\circ) = (63.2 \text{ V}_{\text{rms}} \angle +78.3^\circ)$$

$$\text{Does } V_S = V_C + V_r? \quad (102.1 \text{ V}_{\text{rms}} \angle -11.7^\circ) + (63.2 \text{ V}_{\text{rms}} \angle +78.3^\circ)$$

✓ $V_S = (120.1 \text{ V}_{\text{rms}} \angle +20.1^\circ)$ (good enough, it checks!)

6. Find the average power delivered to the circuit

$$P_{\text{avg}} = V_{\text{rms}} * I_{\text{rms}} * \cos(\Theta_V - \Theta_I) \quad (\text{don't have } I_{\text{rms}})$$

$$I_{\text{rms}} = V_{\text{rms}} / Z_T = (120 \text{ V}_{\text{rms}} \angle +20^\circ) / (34.2 \Omega \angle -58.3^\circ) = 3.51 \text{ A}_{\text{rms}} \angle 78.3^\circ$$

$$P_{\text{avg}} = V_{\text{rms}} * I_{\text{rms}} * \cos(\Theta_V - \Theta_I) = 120 \text{ V}_{\text{rms}} * 3.51 \text{ A}_{\text{rms}} * \cos(20^\circ - 78.3^\circ) = 221 \text{ Watts}$$

Check this:

$$✓ P_{\text{avg}} = V_{\text{rms}}^2 / R = (63.2 \text{ V}_{\text{rms}})^2 / 18 \Omega = 222 \text{ watts (rounding?)}$$

$$221 \text{ Watts}$$

7. Is the power factor for this circuit leading or lagging? Explain.

The voltage is at $+20^\circ$ and the current is at $+78.3^\circ$. Therefore, the current **leads** the voltage.