

TEAM NAME


** SOLUTIONS **

Team member

All 5 questions are equally weighted. Show your work and BOX-IN your final answer for credit.

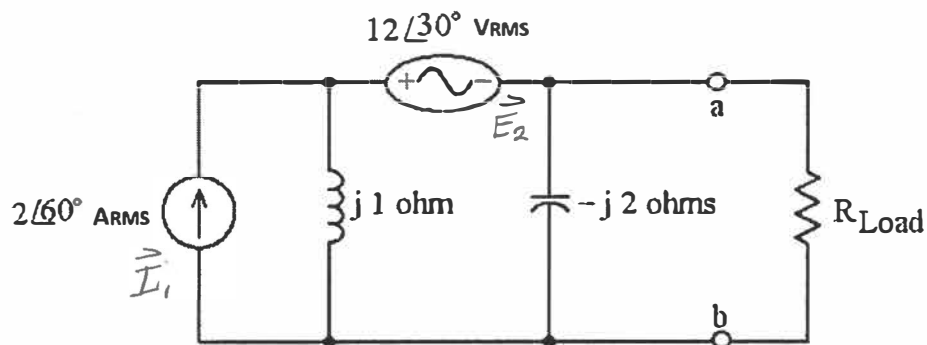
1. If $Z_{TH} = (10 - j30) \Omega$ for a specific circuit, what must the load impedance be for maximum power transfer to occur from that circuit to the load?

$$\vec{Z}_L = \vec{Z}_{TH}^* = \boxed{(10 + j30) \Omega}$$





For the circuit shown above, answer the following 2 questions:

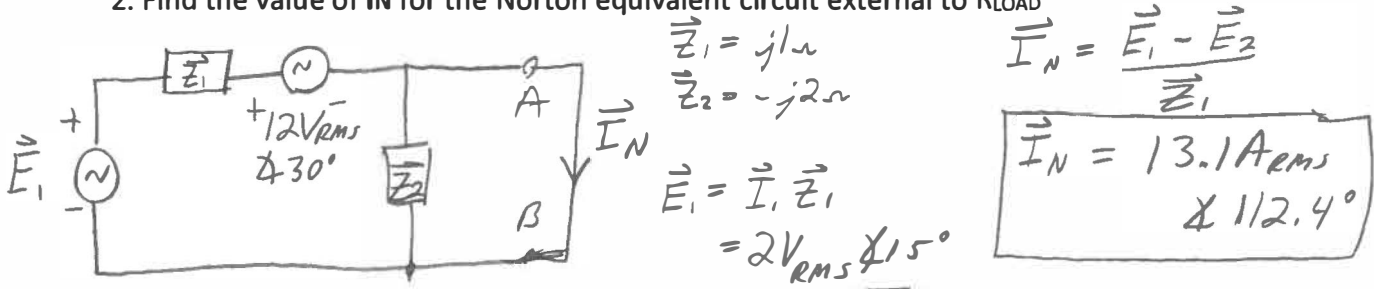2. Find the value of I_N for the Norton equivalent circuit external to R_{LOAD}



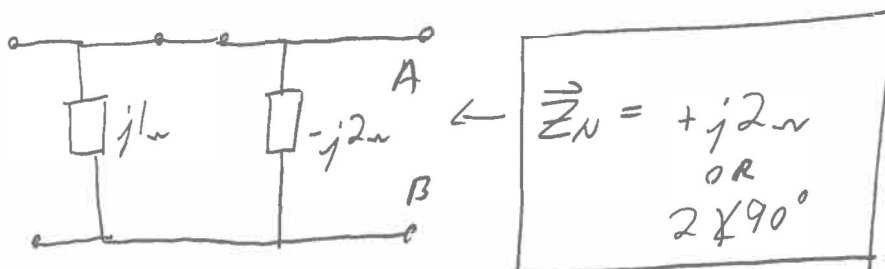
3. Find the value of Z_N for the Norton equivalent circuit external to R_{LOAD}



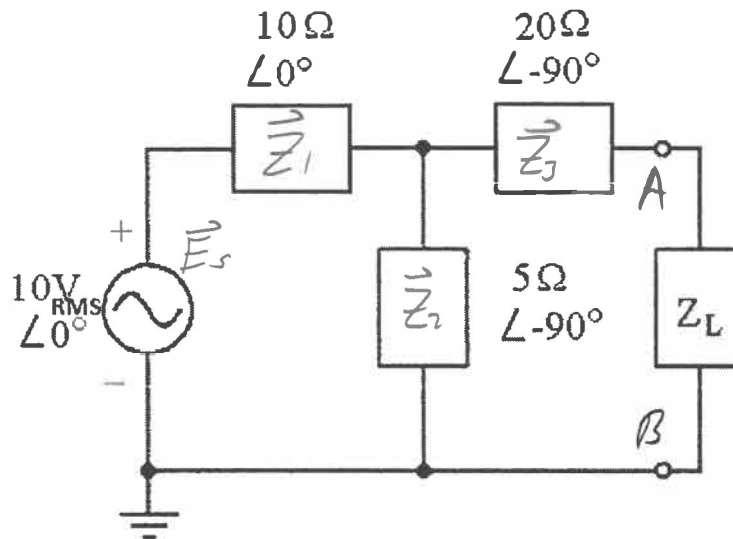

For the circuit shown above, answer the following 2 questions:

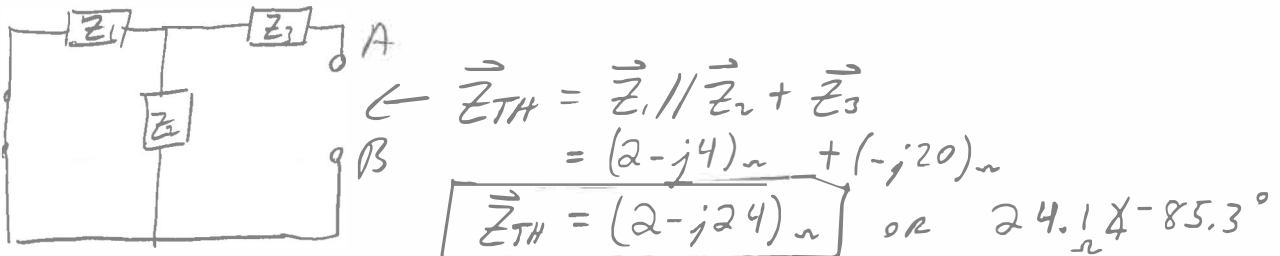4. What is the Thevenin impedance, Z_{TH} , external to Z_L ?



5. What is the Thevenin voltage, V_{TH} , external to Z_L ?

