
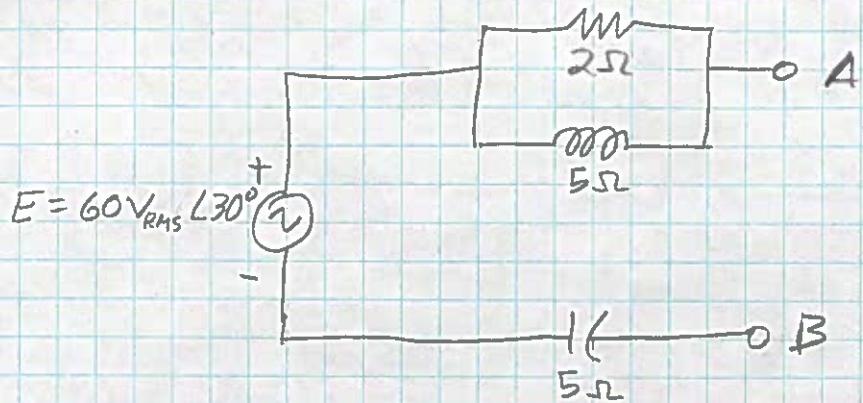


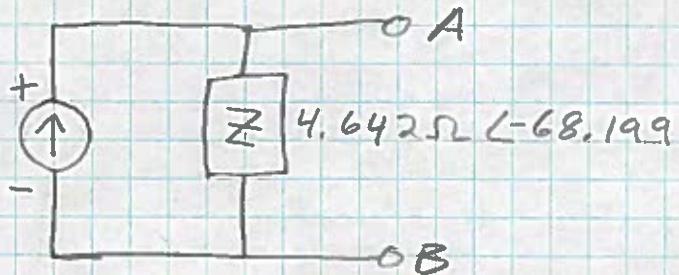18-2 Convert the voltage source to a current source




$$\begin{aligned} Z &= 5\Omega \angle -90^\circ + 2\Omega \angle 0^\circ // 5\Omega \angle 90^\circ \\ &= 5\Omega \angle -90^\circ + 1.857\Omega \angle 21.8^\circ = 4.642\Omega \angle -68.199^\circ \end{aligned}$$


$$I = \frac{E}{Z} = \frac{60\text{V}_{\text{RMS}} \angle 30^\circ}{4.642\Omega \angle -68.199^\circ} = 12.924\text{A} \angle 98.199^\circ$$


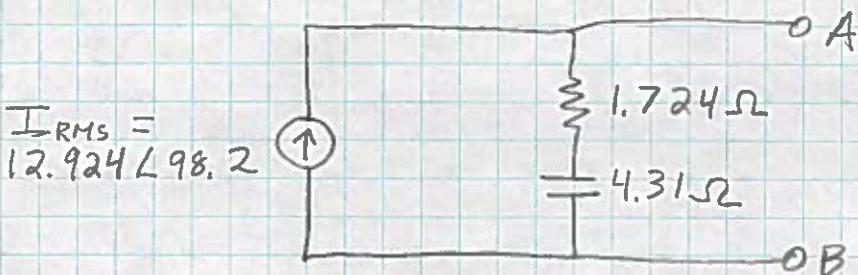
$$Z = 4.642\Omega \angle -68.199^\circ = (1.724 - j 4.31)\Omega$$




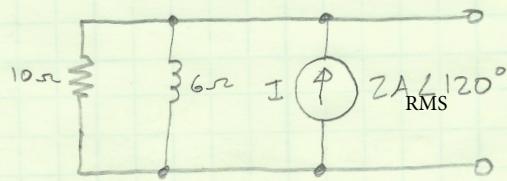
③ Convert the current source to a voltage source



$$Z_T = 10\Omega \parallel j6\Omega = (2.647 + j4.412)\Omega$$
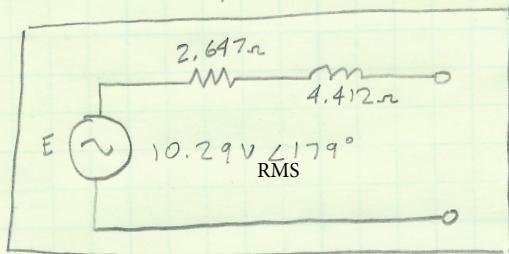
$$E_{th} = I \cdot Z_T = (2.647 + j4.412)\Omega \cdot (2A L 120^\circ)_{RMS} = (10.29V L 179^\circ)_{RMS}$$



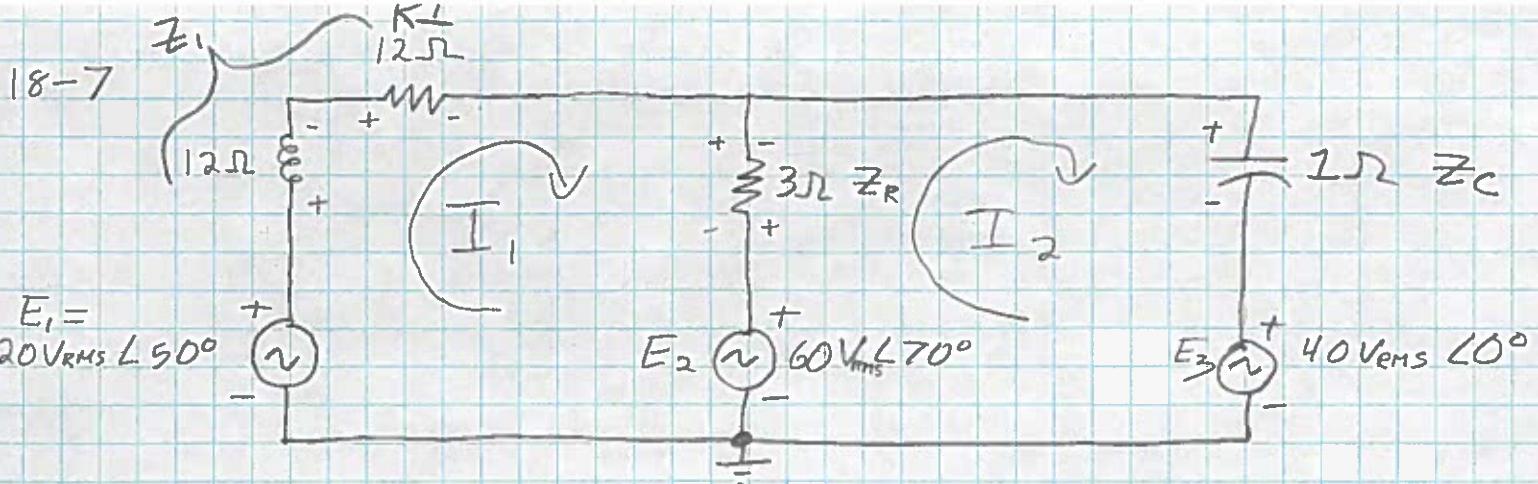

Write the mesh equations and determine the current through  $R_1$ .

$$I_1) 0 = E_1 - I_1 Z_1 - I_1 Z_R + I_2 Z_R - E_2$$

$$-E_1 + E_2 = -I_1 (Z_1 + Z_R) + I_2 Z_R$$

$$-20V_{RMS} \angle 50^\circ + 60V_{RMS} \angle 70^\circ = +I_1 (-15 - j12) + I_2 (3)$$

$$41.77V_{RMS} \angle 79.425^\circ$$

$$I_2) 0 = E_2 - I_2 Z_R + I_1 Z_R - I_2 Z_C - E_3$$

$$-E_2 + E_3 = I_1 Z_R - I_2 (Z_R + Z_C)$$

$$-60V_{RMS} \angle 70^\circ + 40V_{RMS} \angle 0^\circ = I_1 (3) + I_2 (-3 + j1)$$

$$59.652V_{RMS} \angle -70.941^\circ$$


$$I_1 = \begin{vmatrix} 41.77V \angle 79.425 & 3 \angle 0 \\ 59.652V \angle -70.941 & -3 + j1 \\ -15 - j12 & 3 \angle 0 \\ 3 & -3 + j1 \end{vmatrix}$$

$$= (41.77V \angle 79.425)(-3 + j1) - (59.652V \angle -70.941)(3 \angle 0)$$

$$(-15 - j12)(-3 + j1) - (3)(3 \angle 0)$$

$$= \frac{133.72 \angle 156.355}{52.393 \angle 23.629} = \boxed{2.55A_{RMS} \angle 132.73^\circ}$$

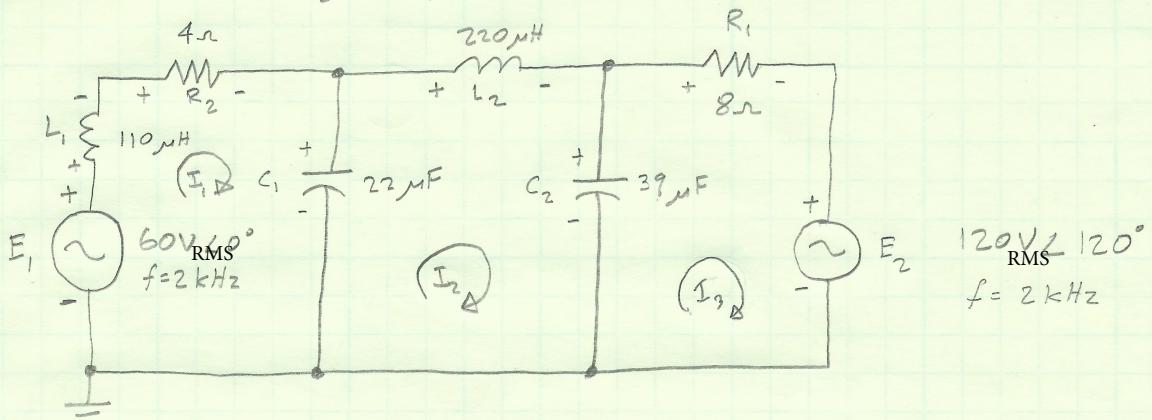⑧ Write the mesh equations for the network below. Find the current through  $R_1$ .



$$E_1 = V_{L_1} + V_{E_2} + V_{C_1} = I_1 X_{L_1} + I_1 R_2 + (I_1 - I_2) X_{C_1}$$

$$0 = -V_{C_1} + V_{L_2} + V_{C_2} = -(I_1 - I_2) X_{C_1} + I_2 X_{L_2} + (I_2 - I_3) X_{C_2}$$

$$-E_2 = -V_{C_2} + V_{R_1} = I_3 R_1 - (I_2 - I_3) X_{C_2}$$

$$E_1 = (X_{L_1} + R_2 + X_{C_1}) I_1 + (-X_{C_1}) I_2 + 0 I_3$$

$$0 = (-X_{C_1}) I_1 + (X_{C_1} + X_{L_2} + X_{C_2}) I_2 + (-X_{C_2}) I_3$$

$$-E_2 = 0 I_1 + (-X_{C_2}) I_2 + (X_{C_2} + R_1) I_3$$

$$X_{L_1} = 1.382 \Omega \quad X_{C_1} = 3.617 \Omega \quad X_{L_2} = 2.765 \Omega \quad X_{C_2} = 2.04 \Omega$$


... and then a miracle happens...

$$I_1 = 6.667 A \angle -63.1^\circ$$


$$I_2 = 18.91 A \angle -63.5^\circ$$

$$I_3 = 14.99 A \angle -63.82^\circ = I_{R_1}$$

18-13

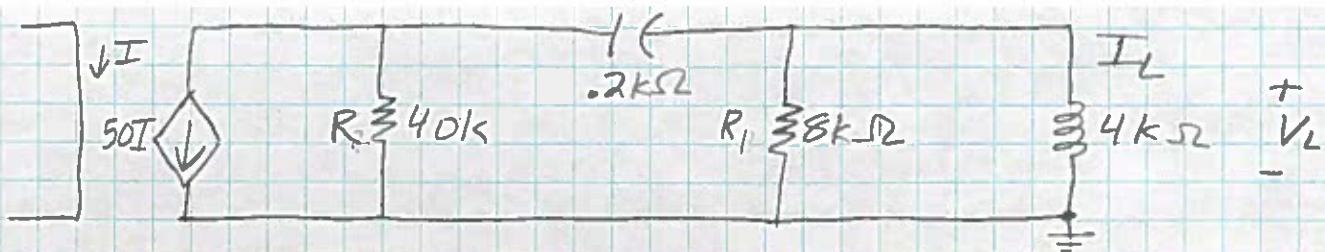

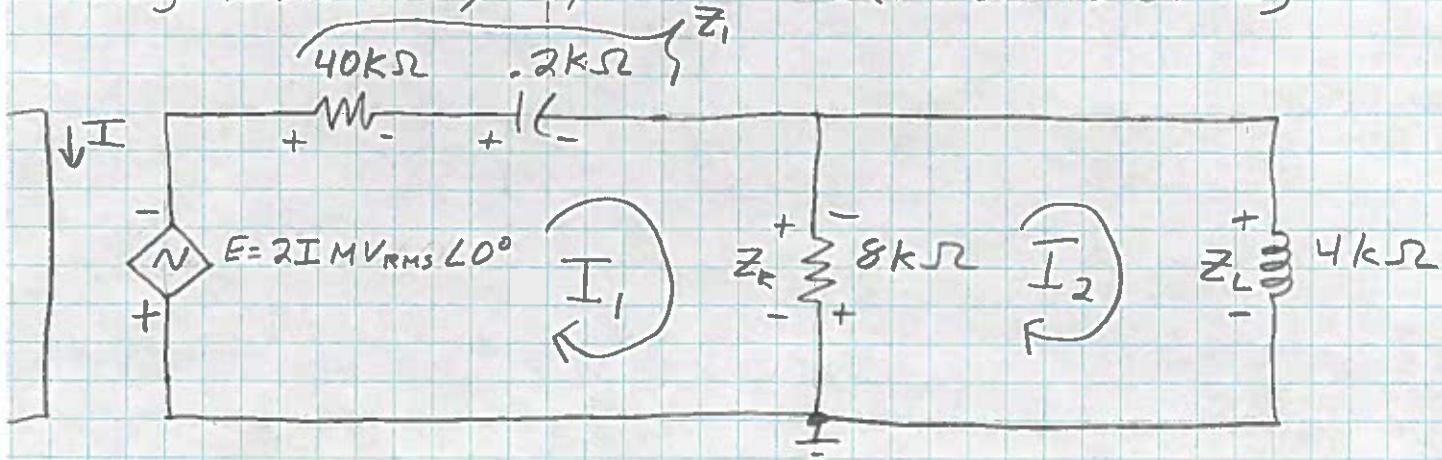Using mesh analysis, find  $I_L$  (in terms of  $I$ )



$$E = 50I \cdot 40k\Omega = 2IMV_{RMS} \angle 0^\circ$$

$$I_1) 0 = -E - I_1 z_1 - I_1 z_R + I_2 z_2$$

$$E = I_1 (-z_1 - z_R) + I_2 z_2$$

$$2IMV \angle 0^\circ = I_1 (-48k + j200) + I_2 (8k)$$

$$I_2) 0 = -I_2 (z_R) + I_1 (z_R) - I_2 (z_L)$$

$$0 = I_1 (z_R) + I_2 (-z_R - z_L)$$

$$0 = I_1 (8k) + I_2 (-8k - j4k)$$

$$I_2 = \frac{-48k + j200}{8k} \quad \frac{2IMV \angle 0^\circ}{-48k + j200}$$


$$\frac{8k}{8k} \quad \frac{0}{-8k - j4k}$$

$$= \frac{(-48k + j200)(0) - (2IMV \angle 0^\circ)(8k)}{(-48k + j200)(-8k - j4k) - (8k)(8k)}$$

$$= \frac{16 \times 10^9 \cdot I}{320.8 \times 10^6 + j190.4 \times 10^6} = \boxed{42.89 I A_{RMS} \angle -30.69^\circ}$$

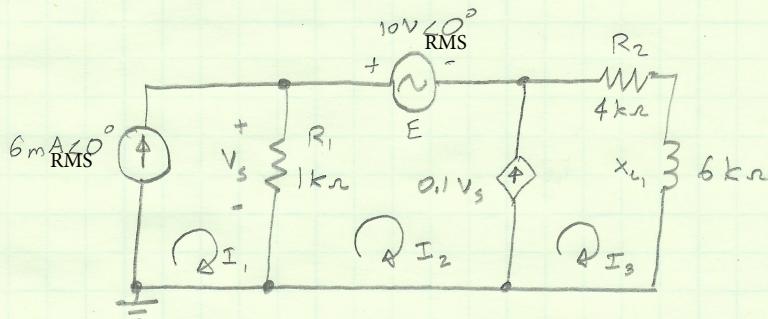(16) Write the mesh equations for the network below.

Determine the current through the inductive element.



$$Z_1 = R_1 + jx_{L1} = (4k\Omega + j6k\Omega)$$

$$I_1 = 6 \text{ mA} \angle 0^\circ$$

$$V_s = (I_1 - I_2)R_1$$

$$\boxed{\textcircled{1}} \quad -V_s + E - I_3 Z_1 = 0$$

$$\boxed{\textcircled{2}} \quad 0.1V_s = I_3 - I_2$$

$$-(I_1 - I_2)R_1 + E - I_3 Z_1 = 0$$


$$I_3 = I_2 + 0.1R_1(I_1 - I_2)$$

$$-R_1 I_1 + R_1 I_2 + E - I_3 Z_1 = 0$$

$$I_3 = I_2 + 0.1R_1 I_1 - 0.1R_1 I_2$$

$$E = R_1 I_1 - R_1 I_2 + I_3 Z_1$$

$$I_3 = 0.1R_1 I_1 + (1 - 0.1R_1) I_2$$

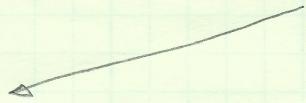

$$E = R_1 I_1 - R_1 I_2 + Z_1 [0.1R_1 I_1 + (1 - 0.1R_1) I_2]$$

$$E = R_1 I_1 - R_1 I_2 + 0.1Z_1 R_1 I_1 + Z_1 (1 - 0.1R_1) I_2$$

$$Z_1 (1 - 0.1R_1) I_2 - R_1 I_2 = E - R_1 I_1 - 0.1Z_1 R_1 I_1$$

$$I_2 = \frac{E - R_1 I_1 - 0.1Z_1 R_1 I_1}{Z_1 (1 - 0.1R_1) - R_1} = 6.053 \text{ mA} \angle 0.111^\circ$$

$$I_{X_{L1}} = I_3 = 0.1R_1(I_1 - I_2) + I_2 = \boxed{1.394 \text{ mA} \angle -56.24^\circ \text{ RMS}}$$