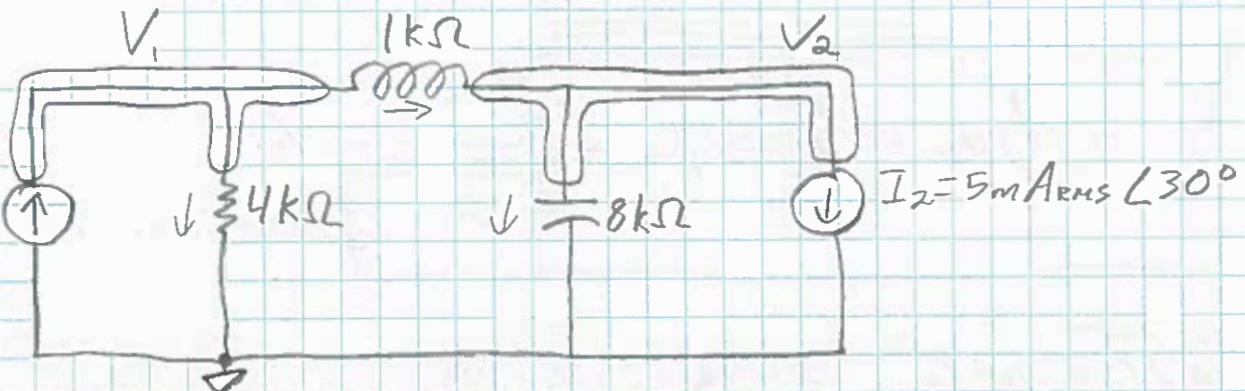


18-17 Determine the nodal voltages



$$I_1 = 3 \text{ mA RMS} \angle 0^\circ$$

$$I_2 = 5 \text{ mA RMS} \angle 30^\circ$$

$$V_1: \frac{I_N = 0}{I_1} = \frac{V_1 - 0}{4k\Omega} + \frac{V_1 - V_2}{1k\Omega \angle 90^\circ}$$

$$3 \text{ mA} \angle 0^\circ = V_1 \left( \frac{1}{4k\Omega} + \frac{1}{1k\Omega \angle 90^\circ} \right) + V_2 \left( \frac{-1}{1k\Omega \angle 90^\circ} \right)$$

$$V_2: \frac{I_N = 0}{V_1 - V_2} = \frac{V_2 - 0}{8k\Omega \angle -90^\circ} + I_2$$

$$\frac{V_1 - V_2}{8k\Omega \angle -90^\circ} = \frac{V_2 - 0}{8k\Omega \angle -90^\circ} + 5 \text{ mA} \angle 30^\circ$$

$$5 \text{ mA} \angle 30^\circ = V_1 \left( \frac{1}{1k\Omega \angle 90^\circ} \right) + V_2 \left( \frac{-1}{1k\Omega \angle 90^\circ} + \frac{-1}{8k\Omega \angle -90^\circ} \right)$$

$$V_1 = \frac{\begin{vmatrix} 3 \text{ mA} \angle 0^\circ & \frac{-1}{1k\Omega \angle 90^\circ} \\ 5 \text{ mA} \angle 30^\circ & \frac{-1}{1k\Omega \angle 90^\circ} + \frac{-1}{8k\Omega \angle -90^\circ} \end{vmatrix}}{\begin{vmatrix} \frac{1}{4k\Omega} + \frac{1}{1k\Omega \angle 90^\circ} & \frac{-1}{1k\Omega \angle 90^\circ} \\ \frac{1}{1k\Omega \angle 90^\circ} & \frac{-1}{1k\Omega \angle 90^\circ} + \frac{-1}{8k\Omega \angle -90^\circ} \end{vmatrix}}$$

$$= \frac{\begin{vmatrix} 3 \text{ mA} \angle 0^\circ & .001 \angle 90^\circ \\ 5 \text{ mA} \angle 30^\circ & 875 \mu\Omega \angle 90^\circ \end{vmatrix}}{\begin{vmatrix} .002 \angle 90^\circ & .001 \angle 90^\circ \\ .001 \angle -90^\circ & 875 \mu\Omega \angle 90^\circ \end{vmatrix}}$$

$$= \frac{3 \text{ mA} \angle 0^\circ \cdot 875 \mu\Omega \angle 90^\circ - 5 \text{ mA} \angle 30^\circ \cdot .001 \angle 90^\circ}{.002 \angle 90^\circ \cdot 875 \mu\Omega \angle 90^\circ - .001 \angle 90^\circ \cdot .001 \angle -90^\circ} = 4.035 \text{ V}_{\text{rms}} \angle -34.3^\circ$$

$$3 \text{ mA} \angle 0^\circ = 4.035 \text{ V}_{\text{rms}} \angle -34.3^\circ \left( \frac{1}{1k\Omega} + \frac{1}{1k\Omega \angle 90^\circ} \right) + V_2 \left( \frac{-1}{1k\Omega \angle 90^\circ} \right)$$

$$V_2 = 10.07 \text{ V}_{\text{rms}} \angle -48.55^\circ$$

20. Determine the nodal voltages for the network of Fig. 18.80.


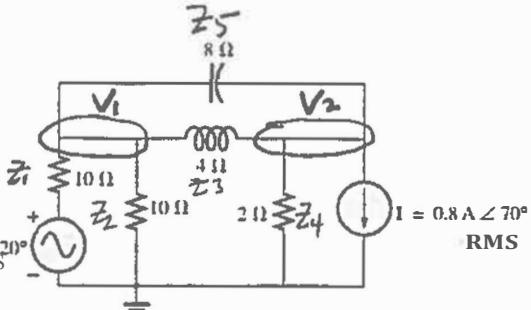


FIG. 18.80  
Problem 20.

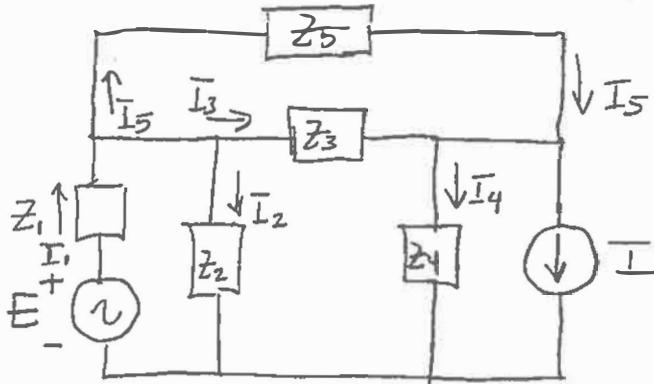

Node V<sub>1</sub>:

$$I_1 = \bar{I}_2 + \bar{I}_3 + \bar{I}_5$$

$$\frac{E - V_1}{Z_1} = \frac{V_1}{Z_2} + \frac{V_1 - V_2}{Z_3} + \frac{V_1 - V_2}{Z_5}$$

$$\therefore V_1 \left[ \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \frac{1}{Z_5} \right] - V_2 \left[ \frac{1}{Z_3} + \frac{1}{Z_5} \right] = \frac{E}{Z_1}$$

Node V<sub>2</sub>:

$$\bar{I} + \bar{I}_3 + \bar{I}_4 + \bar{I}_5 = 0$$

$$\bar{I}_3 + \bar{I}_4 + \bar{I}_5 = -\bar{I}$$

$$\frac{V_2 - V_1}{Z_3} + \frac{V_2}{Z_4} + \frac{V_2 - V_1}{Z_5} = -\bar{I}$$

$$\therefore -V_1 \left[ \frac{1}{Z_3} + \frac{1}{Z_5} \right] + V_2 \left[ \frac{1}{Z_3} + \frac{1}{Z_4} + \frac{1}{Z_5} \right] = -\bar{I}$$

$$\textcircled{1} V_1 [0.200 - 0.125j] - V_2 [-0.125j] = -2.5 + 4.330j$$

$$\textcircled{2} -V_1 [-0.125j] + V_2 [0.5 - 0.125j] = -0.8 \text{ Arms } \angle 70^\circ$$

$$-0.274 - 0.752j$$

$$Z_1 = 10 \Omega + 0j$$

$$Z_2 = " "$$

$$Z_3 = 4 \Omega + j$$

$$Z_4 = 2 \Omega + \theta j$$

$$Z_5 = 8 \Omega - j$$


$$\bar{I} = 0.8 \text{ A } \angle 70^\circ$$

$$E = 50 \text{ V } \angle 120^\circ$$

$$V_1 = (-16.994 + 10.248j) V_{rms}$$
$$= 19.85 V_{rms} \angle 148.9^\circ$$

$$V_2 = (1.250 + 3.057j) V_{rms}$$
$$= 3.3 V_{rms} \angle 67.8^\circ$$

17-24 Determine the nodal voltages

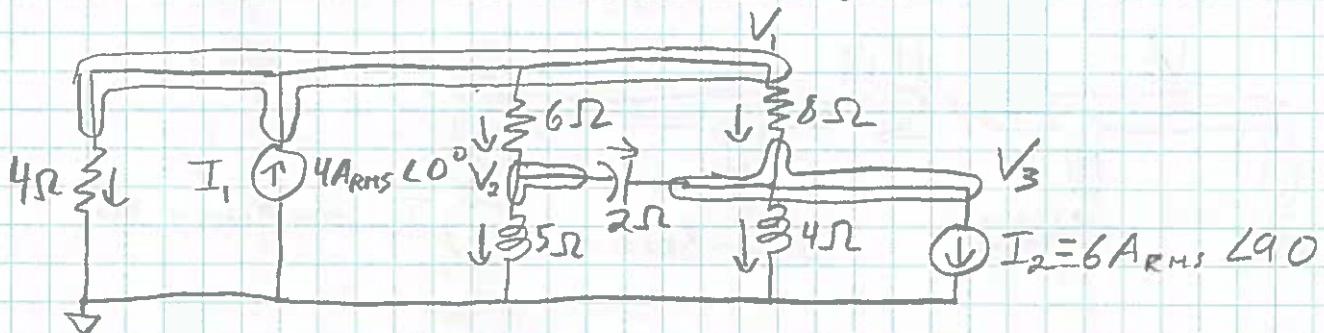

$$1: IN = OUT$$

$$4A \angle 0^\circ = \frac{V_1 - 0}{4\Omega} + \frac{V_1 - V_2}{6\Omega} + \frac{V_1 - V_3}{8\Omega}$$

$$4A \angle 0^\circ = V_1 \left( \frac{1}{4\Omega} + \frac{1}{6\Omega} + \frac{1}{8\Omega} \right) + V_2 \left( \frac{-1}{6\Omega} \right) + V_3 \left( \frac{-1}{8\Omega} \right)$$

$$2: IN = OUT$$

$$\frac{V_1 - V_2}{6\Omega} = \frac{V_2 - 0}{5\Omega \angle 90^\circ} + \frac{V_2 - V_3}{2\Omega \angle -90^\circ}$$

$$0 = V_1 \left( \frac{-1}{6\Omega} \right) + V_2 \left( \frac{1}{5\Omega \angle 90^\circ} + \frac{1}{2\Omega \angle -90^\circ} \right) + V_3 \left( \frac{-1}{2\Omega \angle -90^\circ} \right)$$

$$3: IN = OUT$$

$$\frac{V_1 - V_3}{8\Omega} + \frac{V_2 - V_3}{2\Omega \angle 90^\circ} = \frac{V_3 - 0}{4\Omega \angle 90^\circ} + 6A \angle 90^\circ$$

$$6A \angle 90^\circ = V_1 \left( \frac{1}{8\Omega} \right) + V_2 \left( \frac{1}{2\Omega \angle 90^\circ} \right) + V_3 \left( \frac{-1}{8\Omega} + \frac{-1}{2\Omega \angle -90^\circ} + \frac{-1}{4\Omega \angle -90^\circ} \right)$$


$$X = \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$A = \begin{bmatrix} \frac{1}{4\Omega} + \frac{1}{6\Omega} + \frac{1}{8\Omega} & \frac{-1}{6\Omega} & \frac{-1}{8\Omega} \\ \frac{-1}{6\Omega} & \frac{1}{5\Omega \angle 90^\circ} + \frac{1}{2\Omega \angle -90^\circ} & \frac{-1}{2\Omega \angle -90^\circ} \\ \frac{1}{8\Omega} & \frac{-1}{8\Omega} + \frac{-1}{2\Omega \angle -90^\circ} + \frac{-1}{4\Omega \angle -90^\circ} & \end{bmatrix}$$

$$B = \begin{bmatrix} 4A \angle 0^\circ \\ 0 \\ 6A \angle 90^\circ \end{bmatrix}$$

$$X = A^{-1} \cdot B = \begin{bmatrix} 22.96V \angle -35.75^\circ \\ 39.81V \angle -45.68^\circ \\ 23.28V \angle -59.93^\circ \end{bmatrix}_{RMS}$$

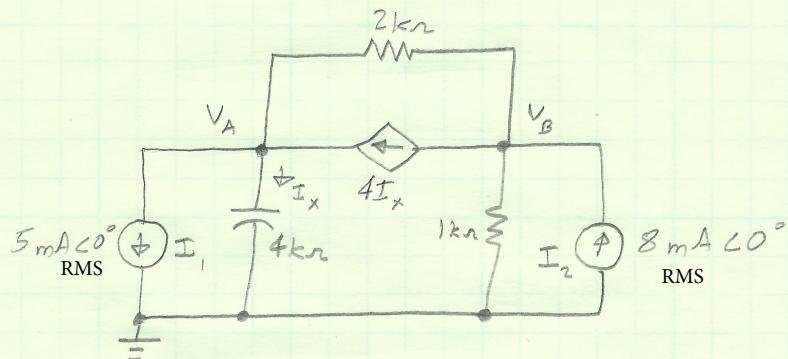(25) Find the nodal voltages for the network below, and determine the voltage across the  $1\text{k}\Omega$  resistor



$$I_x = \frac{V_A}{-j4k\Omega}$$

$$\textcircled{1} \quad 4I_x = I_1 + \frac{V_A}{-j4k\Omega} + \frac{V_A - V_B}{2k\Omega}$$

$$\frac{4V_A}{-j4k\Omega}$$


$$-I_1 = V_A \left[ -\frac{4}{-j4k\Omega} + \frac{1}{-j4k\Omega} + \frac{1}{2k\Omega} \right] + V_B \left[ -\frac{1}{2k\Omega} \right]$$

$$\textcircled{2} \quad I_2 + \frac{V_A - V_B}{2k\Omega} = \frac{4V_A}{-j4k\Omega} + \frac{V_B}{1k\Omega}$$

$$I_2 = V_A \left[ -\frac{1}{2k\Omega} + \frac{4}{-j4k\Omega} \right] + V_B \left[ \frac{1}{2k\Omega} + \frac{1}{1k\Omega} \right]$$

$$\therefore \boxed{\begin{aligned} V_A &= 4.373V \angle -128.7^\circ \text{ RMS} \\ V_B &= 2.252V \angle 17.65^\circ \text{ RMS} \end{aligned}}$$

19-1 Using superposition, find  $I_L$

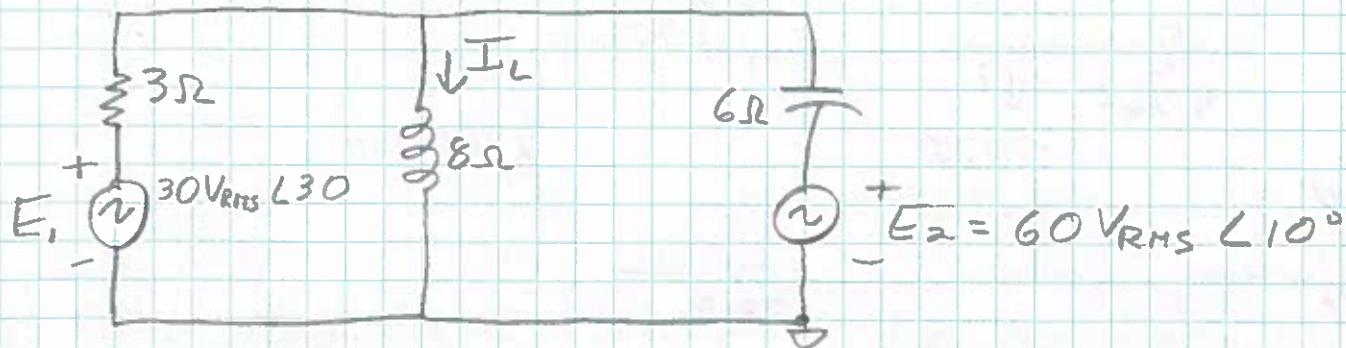

$$I_1 = \frac{30V L 30}{3\Omega + 8L90 / 6L - 90}$$

$$= \frac{30V L 30}{3 - j24}$$

$$= 1.24 A L 112.875$$

$$I_L' = 1.24 A L 112.875 \left( \frac{6L - 90}{8L90 + 6L - 90} \right)$$

$$= 3.72 A L -67.125$$

$$I_2 = \frac{60V L 10}{6\Omega L - 90 + 3L0 / 8L90}$$

$$= \frac{60V L 10}{5.662 A L -62.319}$$

$$= 10.598 A L 72.319$$

$$I_L'' = 10.598 A L 72.319 \left( \frac{3L0}{3L0 + 8L90} \right)$$


$$= 3.721 A L 2.875$$

$$I_L = I_L' + I_L''$$


$$= 3.72 A L -67.125 + 3.721 A L 2.875$$

$$= 6.095 A_{RMS} L -32.119$$

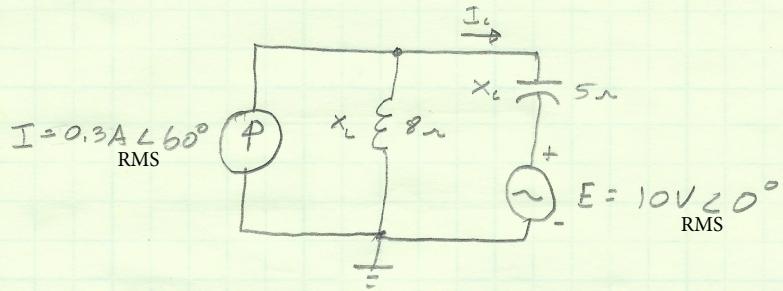
② Using superposition, determine  $I_c$  in the network:



$$I_c = I_c' + I_c''$$

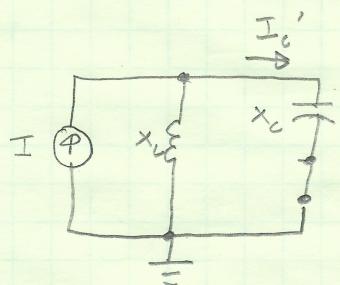

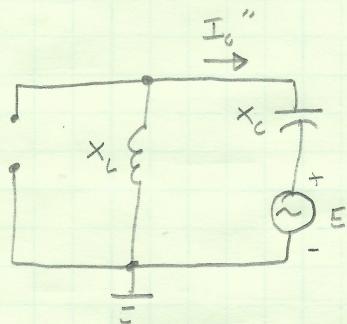
$$I_c' = \frac{X_c}{X_L + X_c} \cdot I = 0.8 \text{ A} \angle 60^\circ$$



$$I_c'' = \frac{-E}{X_c + X_L} = 3.33 \text{ A} \angle 90^\circ$$

$$I_c = (0.8 \text{ A} \angle 60^\circ) + (3.33 \text{ A} \angle 90^\circ) = \boxed{4.05 \text{ A} \angle 84.3^\circ \text{ RMS}}$$

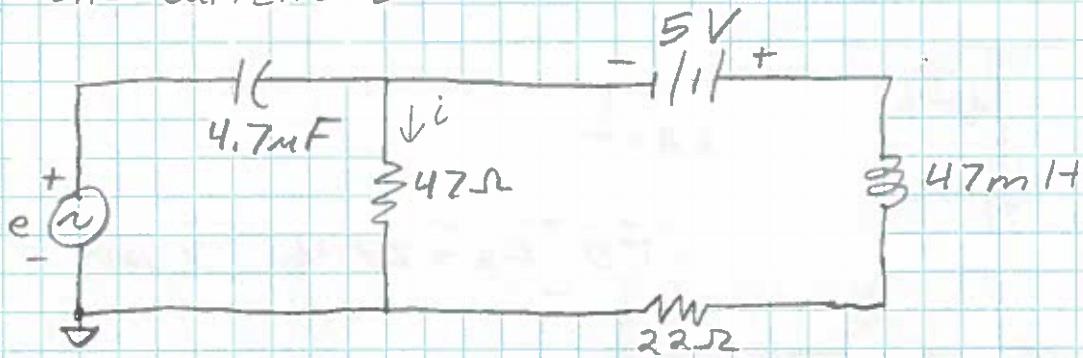
19-6 Using superposition, find the sinusoidal expression for the current  $i$



$$e = 20 \sin(1000t + 60^\circ)$$


$$E = 20 V_{PK} \angle 60^\circ$$
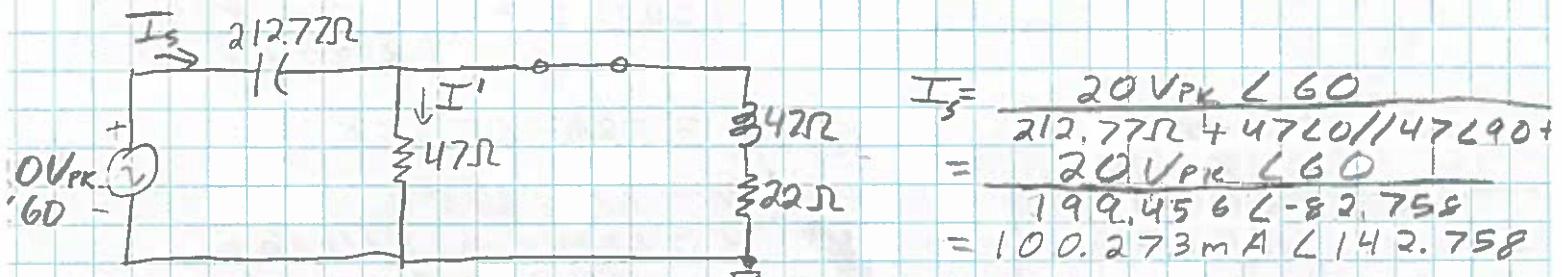
$$X_C = \frac{1}{1000 \cdot 4.7 \mu F} = 212.77 \Omega \quad X_L = 1000 \cdot 47 mH = 47 \Omega$$





$$I' = I_s \left( \frac{22 + j47}{22 + j47 + 47} \right) = 62.328 \text{ mA} \angle 173.413^\circ$$
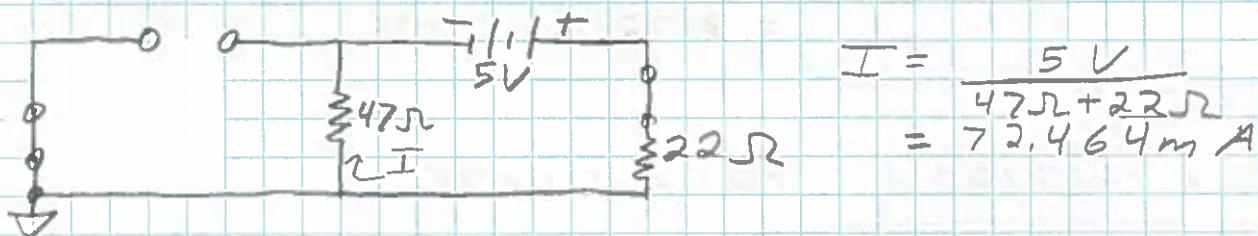
$$i = 62.328 \times 10^{-3} \sin(1000t + 173.413^\circ)$$




$$i = -72.464 \text{ mA} + 62.328 \times 10^{-3} \sin(1000t + 173.413^\circ)$$

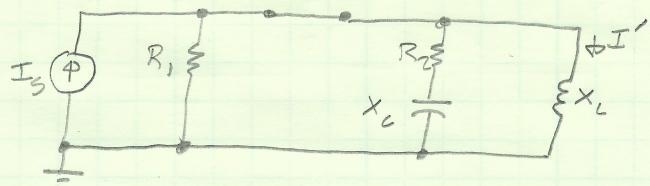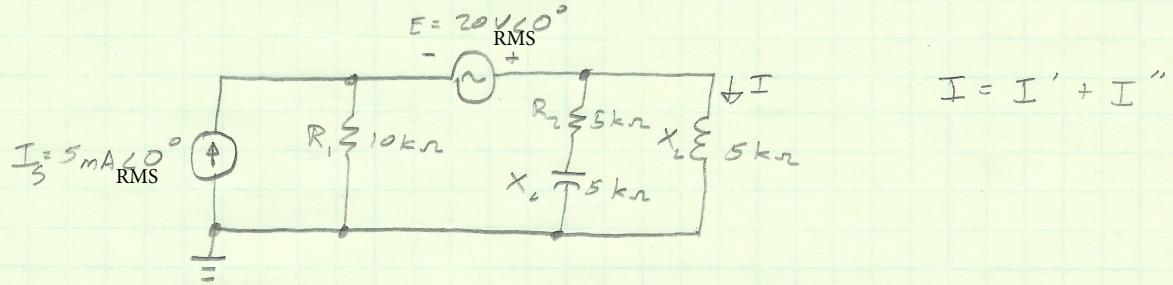⑧ Using superposition, find  $I$  for the network below:


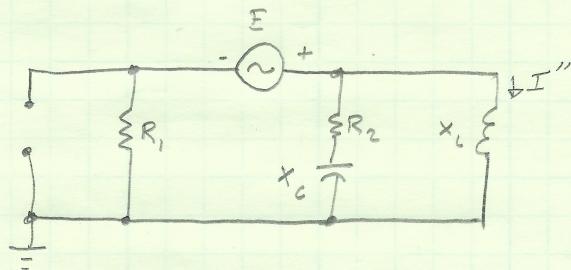
$$I' = \frac{R_1 // (R_2 + X_C)}{Z_L + (R_1 // (R_2 + X_C))} \cdot I_s = (4.472 \text{ mA RMS} \angle -63.43^\circ)$$



$$I'' = E \cdot \frac{X_L // (R_2 + X_C)}{[X_L // (R_2 + X_C)] + R_1} \cdot \frac{1}{X_L} = (1.789 \text{ mA} \angle -63.43^\circ)$$

$$I = I' + I'' = \boxed{(6.26 \text{ mA RMS} \angle -63.43^\circ)}$$